

UNIT: 2 AMPLIFIERS AT HIGH FREQUENCIES

Low frequency analysis:

- All external capacitances (C_e, C_b, C_c) show their effect in low frequency region. Hence they cannot be neglected.
- All internal capacitances behave as open circuit in low frequency regions. Hence they need not be considered.
- The approximate BJT should be replaced with its approx. h-parameter model during analysis. (For FET low frequency model)


Mid frequency analysis:

- All external capacitances behave as short circuit.
- All junction capacitances behave as open circuit.
- BJT is to be replaced with approx. h-parameter model.

High frequency analysis:

- All external capacitances behave as short circuit.
- All junction capacitances show their effect in high frequency region, hence cannot be neglected.
- BJT should be replaced with hybrid- π model during analysis. (For FET, high frequency model)

LOW FREQUENCY ANALYSIS :

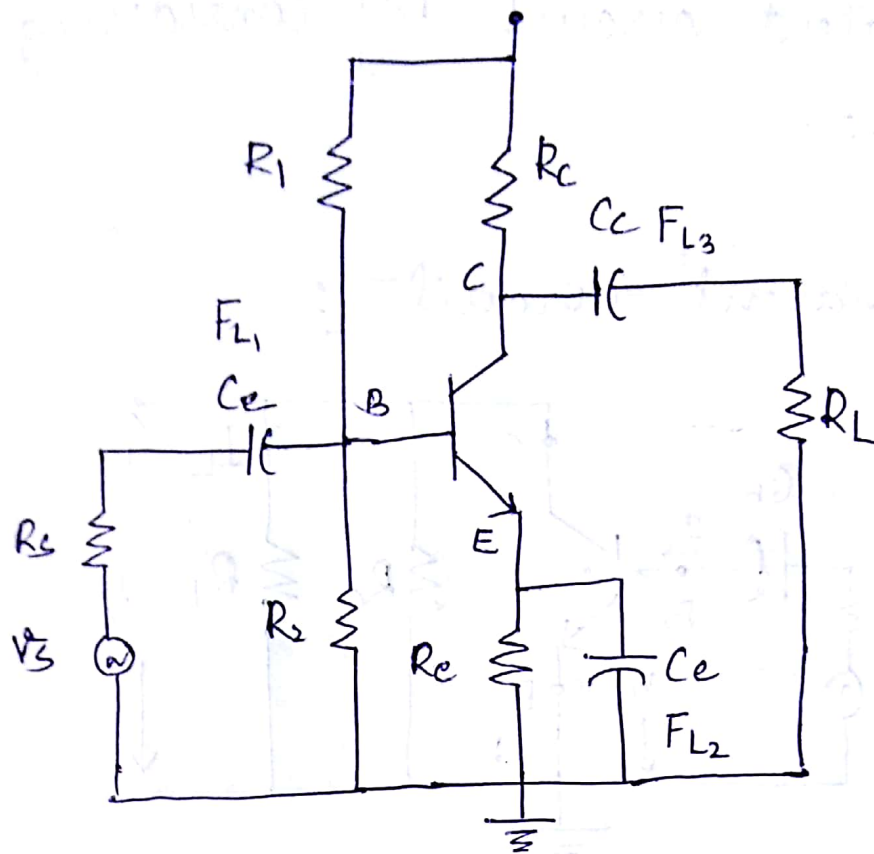


* Assumptions :

1. Neglect the biasing resistances R_1 & R_2 (Open R_1 & R_2)
2. Neglect the stabilisation resistance as $|R_e| \gg \left| \frac{1}{j\omega C_e} \right|$
3. Use approx. h-parameter model for BJT.
4. When C_b is considered, short circuit C_e & C_c .
 " C_e " " " " C_b & C_c
 " C_c " " " " C_e & C_b


Analysis :

Ac equivalent circuit by considering C_b alone.

Ac equivalent circuit :

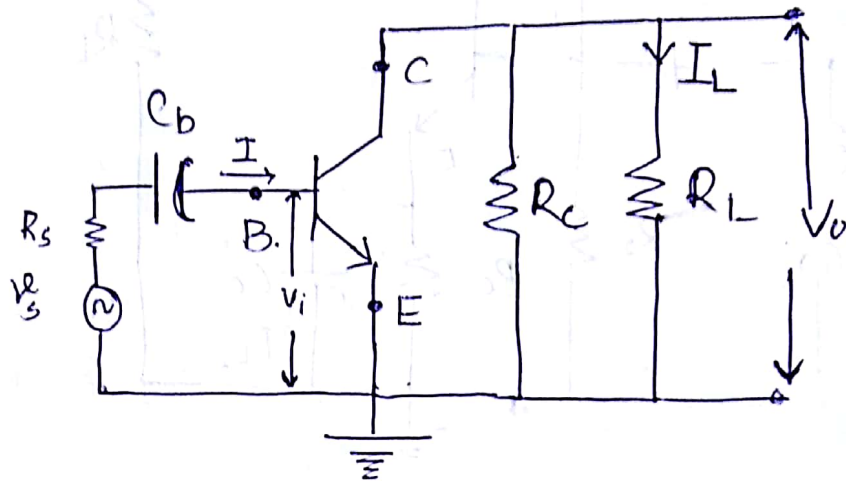

h-parameter model :

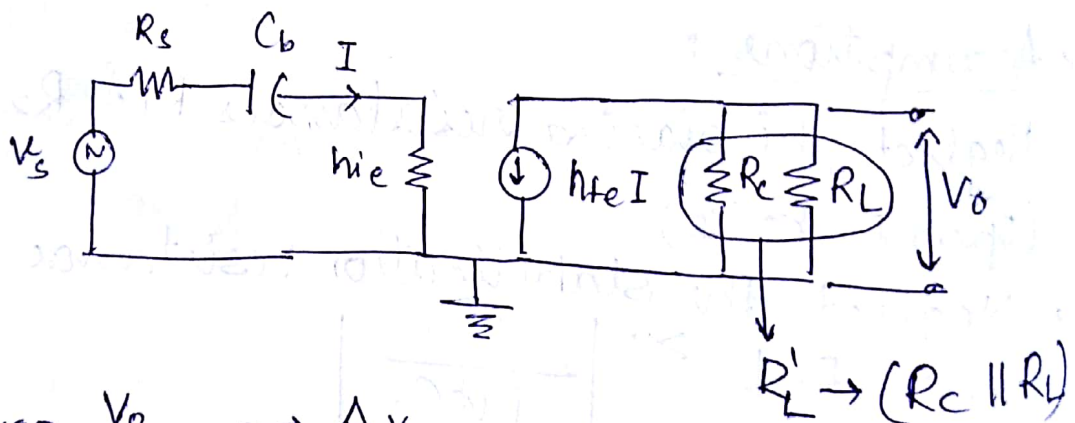

$$1) A_{VS} = \frac{V_o}{V_s} \rightarrow A_v$$

$$= \cancel{I R_L} - h_{fe} I \cdot R'_L$$

$$I = \frac{V_s}{Z}$$

$$\text{where } Z = R_s + h_{ie} + \frac{1}{j\omega C_b}$$

$$V_o = \frac{-h_{fe} V_s R_L'}{Z}$$

$$\Rightarrow A_v = \frac{-h_{fe} V_s R_L'}{Z \cdot V_s}$$

$$A_v = \frac{-h_{fe} R_L'}{Z}$$

$$Z = (h_{ie} + R_s) + \frac{1}{j\omega C_b}$$

$$= (R_s + h_{ie}) \left[1 + \frac{1}{j2\pi f C_b (R_s + h_{ie})} \right]$$

$$= (R_s + h_{ie}) \left[1 - \frac{j f_{L_1}}{f} \right]$$

$$\text{where, } f_{L_1} = \frac{1}{2\pi (R_s + h_{ie}) C_b}$$

$$\Rightarrow A_v = \frac{-h_{fe} R_L'}{(R_s + h_{ie}) \left(1 - \frac{j f_{L_1}}{f} \right)}$$


$$\therefore A_v = \frac{A_{max}}{\left(1 - \frac{j f_{L_1}}{f} \right)}$$

$$\text{where } A_{max} = \frac{-h_{fe} R_L'}{R_s + h_{ie}}$$

$$\frac{A_v}{f}$$

$$\frac{A_{mid}}{\sqrt{1 + \left(\frac{f_{L1}}{f}\right)^2}}$$
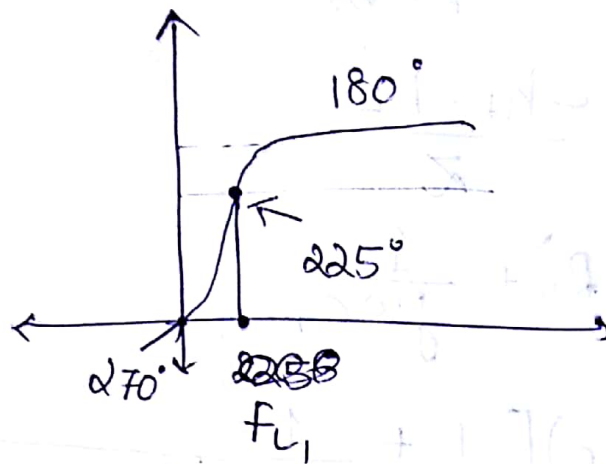
$$\left[180 + \tan^{-1} \frac{f_L}{f} \right]$$



phase shift between input & output is decreasing with increase in frequency and became constant at mid-frequency.

different frequencies show different phase shifts (phase distortion).

H.W

1. Perform low frequency analysis by considering C_e alone and derive the expression for its lower 3dB frequency (f_L)
2. Perform the analysis by using C_c alone