

UNIT - IIIFEEDBACK AMPLIFIERS and OSCILLATORSPart : A Feedback AmplifiersPart : B Oscillators.PART : ATopics to be covered:

- 1 Transistor parameters affecting gain of an amplifier & Need to stabilize gain.
- 2 Concept of Feedback.
- 3 Types of Feedback or Methods of FB
- 4 Derivation for gain with Feedback.
- 5 General characteristics of Negative Feedback and Explanation.
- 6 Classification of amplifiers based on input and output impedances.
- 7 Block diagram of -ve FB amplifier, Sampling and Mixing networks.
- 8 Negative FB amplifier Topologies and Assumptions made for Analysis.
- 9 Effect of Negative Feedback on input and output impedances.
- 10 Step-by-step procedure for the Analysis of -ve FB amplifiers.
- 11 Analysis of Voltage-Series FB amp.
- 12 Analysis of Voltage-Shunt FB amp.
- 13 Analysis of Current-Series FB amp.
- 14 Analysis of Current-Shunt FB amp.
- 15 Problems
- 16 Effect of -ve FB on Lower and upper cutoff frequencies.

### ① Effect of Transistor Parameters on gain:

We know the Transistor amplifier parameters are given by

$$A_I = \frac{-h_{fe}}{1+h_{oe}R_i}$$

$$R_i = h_{ie} + h_{re} A_I R_L$$

$$A_V = A_I \frac{R_L}{R_i}$$

$$\gamma_0 = h_{oe} - \frac{h_{fe} h_{re}}{R_L + h_{ie}}$$

The values of h-parameters ~~are~~ are not constant, if h-parameter values changes then all the amplifier parameters will be affected. If we design an amplifier for a given value of gain, the gain should ~~not~~ be constant irrespective of variations in h-parameters, but in practice, the gain changes due to the following reasons.

① change in temperature

② aging effect of the active device (BJT)

③ Active device replaced with new device.

So if the gain of the amplifier is made independent of transistor parameters then gain is said to be stabilized.

The use of negative feedback stabilizes the gain using

Note: ① Normally it is convenient to represent voltage sources Thvenin's model and current sources with Norton's model. So, in this unit the same notations are to be followed.

(P.T.O.)

## ⑥ Classification of Amplifiers (based on $R_i$ & $R_o$ )

Based on the magnitudes of  $R_i$  and  $R_o$  relative to  $R_S$  and  $R_L$ , amplifiers are classified as

① Voltage Amplifier (Voltage gain  $A_v = \frac{V_o}{V_s}$ )


② Current Amplifier (Current gain  $A_I = \frac{I_o}{I_s}$ )

③ Transconductance Amplifier (Transconductance gain  $G_m = \frac{I_o}{V_s}$ )

④ Transresistance Amplifier (Transresistance gain  $R_m = \frac{V_o}{I_s}$ )

① Voltage Amplifier: ( $A_v = \frac{V_o}{V_s}$ )

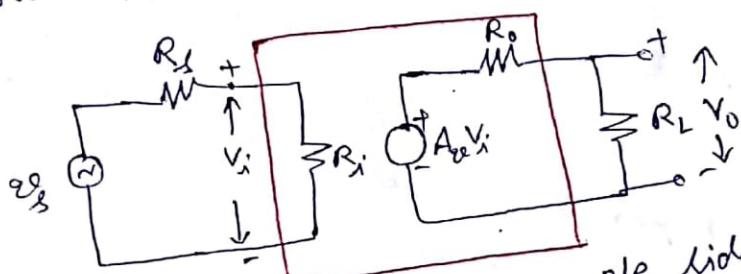A voltage amplifier with Thevenin equivalent circuit can be shown as below.



on s/p side

$$V_i = \frac{R_s R_i}{R_s + R_i}$$

if  $R_i \gg R_s$  then

$$V_i \approx V_s$$

on o/p side

$$V_o = A_{v2} V_i + \frac{R_L}{R_o + R_L}$$

if  $R_L \gg R_o$  &  $R_o \ll R_L$  then

$$V_o \approx A_{v2} V_i \approx A_{v2} V_s$$

therefore

if  $R_i \gg R_s$  and  $R_o \ll R_L$  then

$$V_o \approx A_{v2} R_s$$

$$\Rightarrow V_o \approx V_s$$

then the voltage gain is

independent of  $R_s$  and  $R_L$  magnitudes. Then the amplifier approaches ideal voltage amplifier characteristics.

C.P.T.O. (3)

(3)

For an ideal voltage amplifier  $R_i = \infty$  and  $R_o = 0$ .  
In general the voltage is given by

$$A_v = \frac{V_o}{V_i} = \frac{A_{oe} V_i}{R_o + R_L} \frac{R_L}{R_o + R_L}$$

$$A_v = A_{oe} \frac{R_L}{R_o + R_L}$$

$$\underset{R_L \rightarrow \infty}{\text{Let}} A_v = \underset{R_L \rightarrow \infty}{\text{Let}} A_{oe} \frac{R_L}{R_o + R_L} = \underset{R_L \rightarrow \infty}{\text{Let}} A_{oe} \frac{1}{1 + \frac{R_o}{R_L}}$$

$$= A_{oe}$$


$A_{oe}$  → called as open-circuit voltage gain  
(i.e.,  $R_L = \infty$ )

$A_v$  → called as voltage gain with  $R_L$ .

when  $R_L = \infty$  then the circuit is said to be open-circuited.
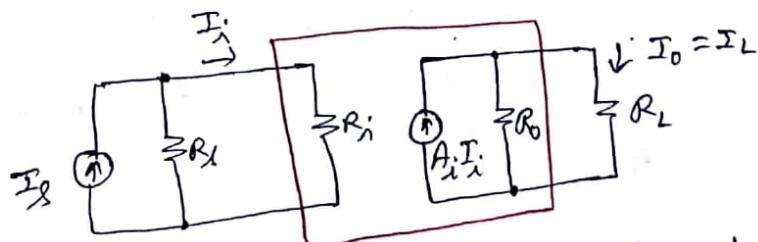
## ② Current Amplifiers : ( $A_i = \frac{I_o}{I_s}$ )

A current amplifier with Norton's equivalent is shown below.



on o/p side

$$I_o = A_i I_i \frac{R_o}{R_o + R_L}$$

if  $R_o \gg R_L$  then

$$I_o \approx A_i I_i \approx A_i I_s$$

$$I_i \approx I_s$$

on input side

$$I_i = I_s \frac{R_s}{R_s + R_i}$$

if  $R_i \ll R_s$  then

(P.T.O.)

If  $R_i \ll R_s$  and  $R_o \gg R_L$  then

$$I_o \approx A_{2s} I_s$$

$$\Rightarrow I_o \approx I_s$$

then the current gain is

independent of  $R_s$  and  $R_L$ . Then the amplifier approaches ideal current amplifier characteristics.

For an ideal current amplifier  $R_i = 0$  &  $R_o = \infty$ .

In general the current gain is given by

$$A_I = \frac{I_o}{I_s}$$
$$= \frac{A_i I_s}{R_s} \frac{R_o}{R_o + R_L}$$

$$A_I = A_i \frac{R_o}{R_o + R_L}$$

$$A_I = \frac{A_i R_o}{R_o + R_L} = A_i \quad \text{when } R_L \rightarrow 0$$

$R_L \rightarrow 0$  short circuit

$R_L = 0 \Rightarrow$  short circuit current gain ( $I_o R_L = 0$ )

$A_i \rightarrow$  short circuit current gain with load resistance  $R_L$ .


$A_I \rightarrow$  current gain with load resistance  $R_L$ .

when  $R_L = 0$  then the circuit is said to be short-circuited

(P.T.O.)  
.. 4

③ Transconductance Amplifier:  $(G_m = \frac{I_o}{V_s})$

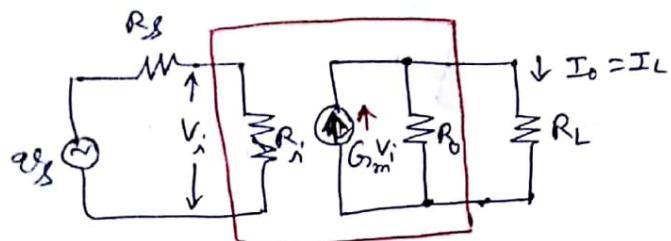A transconductance amplifier is as shown below.



on o/p side

$$V_i = \frac{V_s}{R_i + R_s}$$

if  $R_i \gg R_s$  then

$$V_i \approx V_s$$

on o/p side

$$I_o = G_m V_i \times \frac{R_o}{R_o + R_L}$$

if  $R_o \gg R_L$  then

$$I_o \approx G_m V_i \approx G_m V_s$$

Therefore

if  $R_i \gg R_s$  and  $R_o \gg R_L$  then

$$I_o \approx G_m V_s$$

$$\therefore I_o \propto V_s$$

then the transconductance

gain is independent of  $R_s$  and  $R_L$  magnitudes. Then the amplifier approaches ideal transconductance amplifier characteristics.

For an ideal Transconductance amplifier  $R_i = \infty$  &  $R_o = \infty$ .

In general the Transconductance gain is given by

$$G_M = \frac{I_o}{V_s} = \frac{G_m V_i}{V_i} \frac{R_o}{R_o + R_L}$$

$$G_M = G_m \frac{R_o}{R_o + R_L}$$

$$\begin{aligned} \text{If } G_M &= \frac{G_m}{R_o \rightarrow \infty} \frac{R_o}{R_o + R_L} \\ &= \frac{G_m}{R_o \rightarrow \infty} \frac{1}{1 + \frac{R_L}{R_o}} \end{aligned}$$

$$\therefore \underset{R_o \rightarrow \infty}{\text{LT}} G_M = G_m$$

$R_L = \infty \Rightarrow$  open-circuited


$G_m \rightarrow$  open-circuited Transconductance gain

$G_M \rightarrow$  Transconductance gain with  $R_L$ .

(P.T.O.)

④ Transresistance amplifier: ( $R_M = \frac{V_o}{I_i}$ )

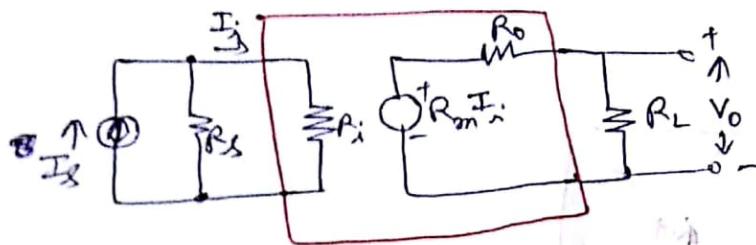The Transresistance amplifier is as shown



On o/p side

$$I_o = I_s + \frac{R_s}{R_s + R_i} I_i$$

$\Rightarrow R_s \gg R_i$  then  $R_s \ll R_s$

$$I_o \approx I_s$$

Therefore

if  $R_s \gg R_i$  and  $R_o \ll R_L$  then

$$V_o \approx R_m I_s$$

$$\Rightarrow V_o \propto I_s$$

on o/p side

$$V_o = \frac{R_m I_s}{R_s + R_i} \times \frac{R_L}{R_o + R_L}$$

if  $R_o \ll R_L$  then

$$V_o \approx R_m I_s \approx R_m I_s$$

then the Transresistance amplifier approaches

is independent of  $R_s$  and  $R_L$ , then the amplifier characteristics.

ideal ~~Transresistance~~ amplifier  $R_i = 0$  &  $R_o = 0$

For an ideal Transresistance amplifier the gain is

$$R_M = \frac{V_o}{I_i} = \frac{R_m I_s}{I_i} + \frac{R_L}{R_o + R_L}$$

$$R_M = R_m \frac{R_L}{R_o + R_L}$$

$$R_M = R_m \frac{\frac{R_L}{R_o + R_L}}{\frac{R_L}{R_o + R_L}} = \frac{R_m}{1 + \frac{R_o}{R_L}} = R_m$$

$R_M$   $\underset{R_L \rightarrow \infty}{\approx}$  Open-circuit Transresistance gain

$R_M$   $\rightarrow$  Open-circuit Transresistance gain with  $R_L$ .

$R_M$   $\rightarrow$  Transresistance gain with  $R_L$ .

(P.T.O.) ⑥

## (2) & (3) Concept of Feedback:

on an electronic circuit, when some portion of output signal is sampled and applied back at the input then feedback is said to be present in the circuit.

Definition: The process of applying a fraction of output signal at the input is called as feedback.

### Two methods of FB

① LOCAL FB: If ~~the~~<sup>a fraction of</sup> o/p of a circuit is applied back at the input of the same circuit then it is said to be local FB.

② GLOBAL FB: If ~~the~~<sup>a fraction of</sup> o/p of another circuit is applied back at the input of another circuit then it is said to be global FB.

### TWO TYPES OF FB

① Positive FB & ② Negative FB.

#### ① Positive FB

When the feedback signal is in phase with external input signal then the effective input signal to the basic amplifier increases and hence output also increases, hence gain increases. This type of feedback is called as +ve FB.

with +ve FB: ① Feedback signal and External signal are in phase.

② Gain of the op amplifier circuit increases

③ The circuit becomes unstable and falls into oscillations.

Note: In oscillatory circuits +ve FB is used.

(P.T.O.)

## ② Negative FB:


If the FB signal is out of phase with External input signal then the effective input signal decreases and output signal also decreases, hence gain decreases. This type of Feedback is called as negative feedback.

With -ve Feedback: ① FB signal and external input signal are out of phase by  $180^\circ$ .

② Gain decreases.

③ The circuit becomes more stable and hence -ve FB is used in all amplifiers.

Block diagram of FB amplifier.

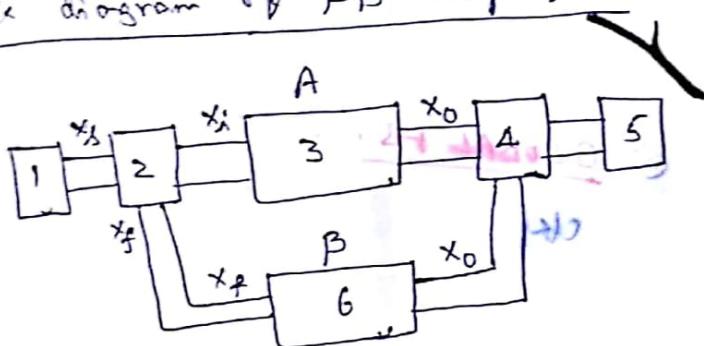

1 → Source (or) External source signal  $x_s$  ( $v_s$  or  $I_s$ )

2 → Comparator or Mixing network

its o/p  $x_i = x_s \pm x_f$

3 → Basic amplifier with gain  $A = \frac{x_o}{x_i}$

4 → Sampling Network, Samples o/p signal  $v_o$  or  $I_o$

5 → Load  $R_L$  to the amplifier


6 → Feedback network with  $\beta = \frac{x_f}{x_o}$  where

$\beta$  is called as feedback factor or feedback network factor.

(P.T.O.)

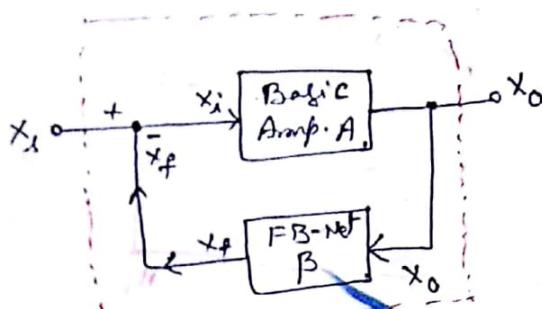**④ Derivation for gain with -ve feedback:**

The simple block diagram with -ve feedback is shown below



The gain with -ve Feedback ( $A_f$ ) is defined as

$$A_f = \frac{x_o}{x_i}$$

From the figure we know

$$x_i = x_b - x_f$$

$$\therefore x_i = x_i + x_f$$

$$\text{but } x_f = \beta x_o$$

$$\text{and } x_o = Ax_i$$

$$\left[ \begin{array}{l} \therefore \beta = \frac{x_f}{x_o} \\ \therefore A = \frac{x_o}{x_i} \end{array} \right]$$

$$\therefore x_b = x_i + \beta x_o$$

$$= x_i + A\beta x_i$$

$$x_b = x_i (1 + AB)$$

$$= \frac{A}{1 + AB}$$

$$\therefore A_f = \frac{x_o}{x_b} = \frac{x_o}{x_i (1 + AB)}$$

$$\boxed{\therefore A_f = \frac{A}{1 + AB}}$$

$A_f \rightarrow$  gain with feed back

$A_f \rightarrow$  transfer gain of the amplifier including the loading effect of  $\beta$ -net,  $R_L$  and  $R_S$ .

$A \rightarrow$  Transfer network factor.

(P.T.O.)

If  $|A_f| < |A|$  then the feedback is called as negative or degenerative where the gain decreases by a factor of  $D = 1 + AB$ , called as degeneracy factor. Sensitivity is equal to the reciprocal of  $D$ .  $A_f$

$$\therefore \boxed{\text{sensitivity} = \frac{1}{D} = \frac{1}{1+AB}} = \frac{A_f}{A} F$$

Hence sensitivity can be defined as "the ratio of % change in gain with FB to the % change in gain without FB."

Loop gain :  $-AB(A + \beta X^{-1})$  is called as loop gain or return ratio

Loop gains :  $-AP$  (1)   
return ratio

Sensitivity :  $(1 - \text{return ratio})$  is called as sensitivity  
 or return difference. P.  $\frac{1}{A+B}$

$$\therefore D = 1 + A\beta$$

$$\therefore A_f = \frac{A}{1 + A\beta}$$

We know  $A_f = \frac{A}{1+A\beta}$   
 The amount of feedback introduced into the amplifier  
 $\therefore$   $A_f = \frac{A}{1+A\beta}$  in dB

is given by  $\frac{dy}{dx}$ , if expressed in  $y$

$$\frac{A_f}{A} = \frac{1}{1+AB}$$

$$N = 20 \log \left( \frac{AF}{A} \right) = 20 \log \left( \frac{1}{1+AB} \right)$$

$$N = 20 \log \left( \frac{A_f}{A} \right) = 20 \log \left( \frac{1}{1+AB} \right)$$

for negative feedback       $N$  is a negative number &  
 for positive feedback       $N$  is a positive number.

## ⑤ General Characteristics of Negative Feedback Amplifiers:

or

### Merits and Demerits of -ve FB.

or

### Advantages and disadvantages of -ve FB

The only disadvantage of negative feedback is reduction of Transfer gain. But -ve FB has significant advantages in contrary to the reduction in gain. The general characteristics of -ve FB ~~are~~ are as follows:

- (a) Desensitization of Transfer gain (or) stabilization of gains
- (b) Reduction of Non-linear distortion
- (c) Reduction of Noise
- (d) Reduction of frequency distortion
- (e) Improved frequency response (or) Bandwidth increases
- (f) Modified input and output impedances.

### a) Stabilization of Transfer gain:

The gain of the amplifier with negative FB is given by

$$A_f = \frac{A}{1+AB}$$

Differentiate both sides with A

$$\begin{aligned} \therefore \frac{dA_f}{dA} &= \frac{1}{(1+AB)^2} \\ &= \frac{A_f}{A(1+AB)} \end{aligned}$$

$$\therefore \frac{dA_f}{A_f} = \left( \frac{1}{1+AB} \right) \times \frac{dA}{A}$$

where  $\frac{dA_f}{A_f}$  → Fractional change in gain with FB

$\frac{dA}{A}$  → Fractional change in gain without FB.

(P.T.O.)

$$\text{always } \left| \frac{dA_f}{A_f} \right| < \left| \frac{dA}{A} \right|.$$

Hence the fractional change ~~with~~ in gain ~~is~~ with  $-FB$  is reduced by a factor of Degravitability  $D = (1 + A\beta)$ , to that of without Feedback.

### (b) Reduction of Non-linear Distortion:

Due to non-linearity of the active device, harmonic distortion will be introduced at the output terminals of the amplifier. This is also called as non-linear distortion or amplitude distortion. When negative FB is introduced this distortion will be reduced by a factor of  $D$ .

$$D_f = \frac{D}{1 + A\beta}$$

where  $D$  is the total non-linear distortion. If only second harmonic distortion is considered then

$$B_{2f} = \frac{B_2}{1 + A\beta}$$

where  $B_2$  is the second harmonic distortion without feedback and  $B_{2f}$  is the second harmonic distortion with feedback.

### (c) Reduction of Noise:

There are many sources of noise in an amplifier, specifically in the active device, this noise will also be amplified along with external signal. When negative feedback is employed then the total noise  $N$  will be reduced by factor of Degravitability.

$$\therefore N_f = \frac{N}{1 + A\beta}$$

(d) Reduction of Frequency Distortion:

The gain with -ve FB is given by

$$A_f = \frac{A}{1+AB}$$

if  $|AB| \gg 1$  then  $1+AB \approx AB$

$$\therefore A_f \approx \frac{A}{AB}$$

$$A_f \approx \frac{1}{B}$$

The gain with -ve FB is almost equal to reciprocal of feedback network factor  $B$ . In negative feedback feedback network consists of only resistive components which are independent of frequency. So, the gain with -ve FB is almost constant for the entire frequency range.

in Bandwidth:

(e) enforcement  
When negative FB is employed in an amplifier the lower and upper cut off frequencies will be modified such that the overall bandwidth more than that of without feedback. The Bandwidth with -ve FB is given by

$$BW_f = BW \times (1+AB)$$

where  $A$  is the mid band gain without feedback.

(P.T.O.)

Note: Student should be careful in understanding the reduction of frequency distortion, this means, for the given Bandwidth  $BW$  the frequency response is almost constant, but the upper cut off and lower cut off frequencies are controlled by internal and external capacitances only.

(P.T.O.)

(f) Modified input and output impedances:

When negative FB is employed, the feedback signal is mixed with the external input signal. This mixing either in series or in shunt. If the mixing is in series the net input impedance increases by a factor D.

$$\therefore R_{if} = R_f (1 + AB)$$

where  $R_f \rightarrow$  Input Impedance without FD.

If the mixing is in shunt the net input impedance decreases by a factor of D.

$$\therefore R_{if} = \frac{R_i}{1 + AB}$$

The output impedance of a negative feedback amplifier depends the signal sampled. If output voltage (node sampling) is sampled then the output impedance decreases by a factor of D.

$$\therefore R_{of} = \frac{R_o}{1 + AB}$$

If the output current is sampled (loop sampling) then the output impedance increases by a factor of  $(1 + AB)$ .

$$\therefore R_{of} = R_o (1 + AB)$$

(P.T.O.)

Note: The proof of these 4 expressions will be discussed in the later sections.

10/10

P.T.O.  
9


(7) & (8) Negative Feedback amplifier Topologies  
and  
Block diagrams

The four negative feedback amplifier topologies are

- ① Voltage-series FB
- ② Voltage-shunt FB
- ③ Current-series FB
- ④ Current-shunt FB.



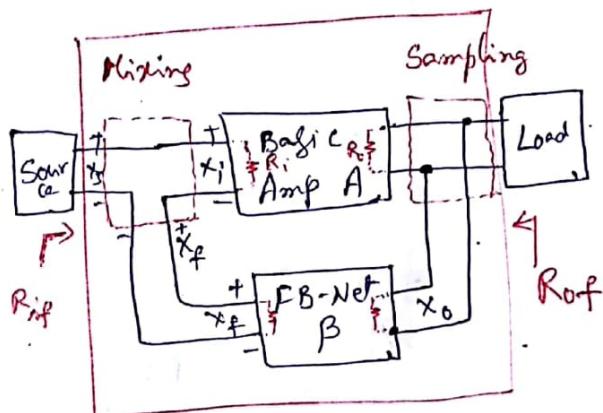① Voltage-Series FB amplifiers  $[x_0 = V_o, x_s = V_s, A = Av = \frac{V_o}{V_i}]$



① Sampling  $\rightarrow$  Node Sampling or voltage sampling  
indicate the o/p variable is voltage  $V_o$

② Mixing  $\rightarrow$  series mixing  
indicate the input variable is voltage  $V_i$

$$③ Av = \frac{x_o}{x_i} = \frac{V_o}{V_i}$$


$$④ \beta = \frac{x_f}{x_o} = \frac{V_f}{V_o}$$

$$⑤ Av_f = \frac{x_o}{x_s} = \frac{V_o}{V_s} = \frac{Av}{1+Av\beta}$$

$$⑥ R_{if} = R_f(1+Av\beta) \text{ & } R_{of} = \frac{R_o}{(1+Av\beta)}$$

② Voltage-shunt FB amplifier [ $x_0 = v_o$ ,  $x_i = I_s$ ,  $A = \frac{x_0}{x_i} = \frac{v_o}{I_s}$ ]

Feedback comp.

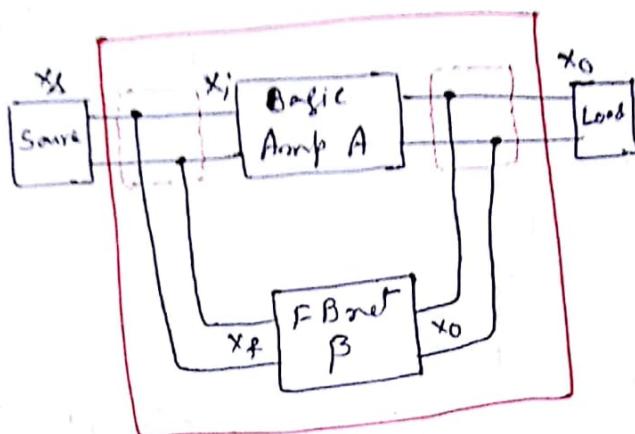

Sampling  $\rightarrow$  Node Sampling or voltage Sampling  
indicate o/p variable is voltage  $v_o$ .

Mixing  $\rightarrow$  shunt mixing  
indicate o/p variable is current  $I_s$

$$A \rightarrow R_M = \frac{x_0}{x_i} = \frac{v_o}{I_s}$$


$$\beta \rightarrow \beta = \frac{x_f}{x_0} = \frac{I_f}{V_o}$$

$$A_f \rightarrow R_{Mf} = \frac{x_0}{x_s} = \frac{V_o}{I_s} = \frac{R_M}{1 + R_M \beta}$$

$$R_{if} = \frac{R_i}{1 + R_M \beta} \quad \text{and} \quad R_{of} = \frac{R_o}{1 + R_M \beta}$$

③ Current-Series FB amplifier  $[x_o = I_o, x_i = V_i, A = G_M = \frac{I_o}{V_i}]$

Feedback amp.

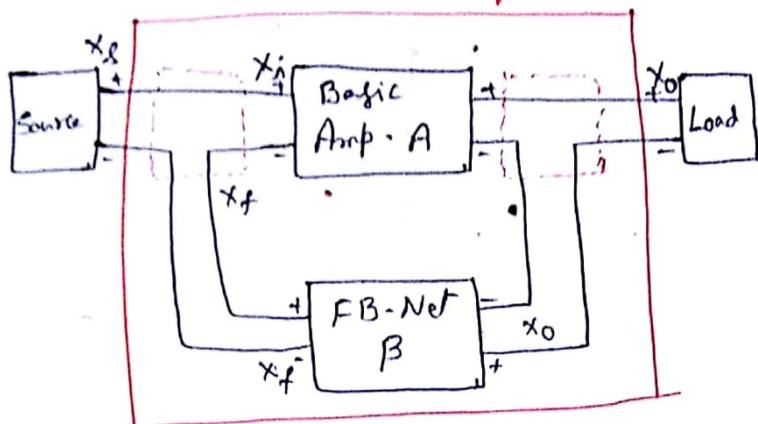

① Sampling  $\rightarrow$  Loop Sampling or Current Sampling  
indicates the o/p variable is current  $I_o$

② Mixing  $\rightarrow$  Series mixing  
indicates the input variable is voltage  $V_i$



$$③ A \rightarrow G_M = \frac{x_o}{x_i} = \frac{I_o}{V_i}$$

$$④ \beta \rightarrow \beta = \frac{x_f}{x_o} = \frac{V_f}{I_o}$$

$$⑤ A_f \rightarrow G_{Mf} = \frac{x_o}{x_f} = \frac{I_o}{V_f} = \frac{G_M}{(1 + G_M \beta)}$$

$$⑥ R_{if} = R_i(1 + G_M \beta) \quad \& \quad R_{of} = R_o(1 + G_M \beta)$$

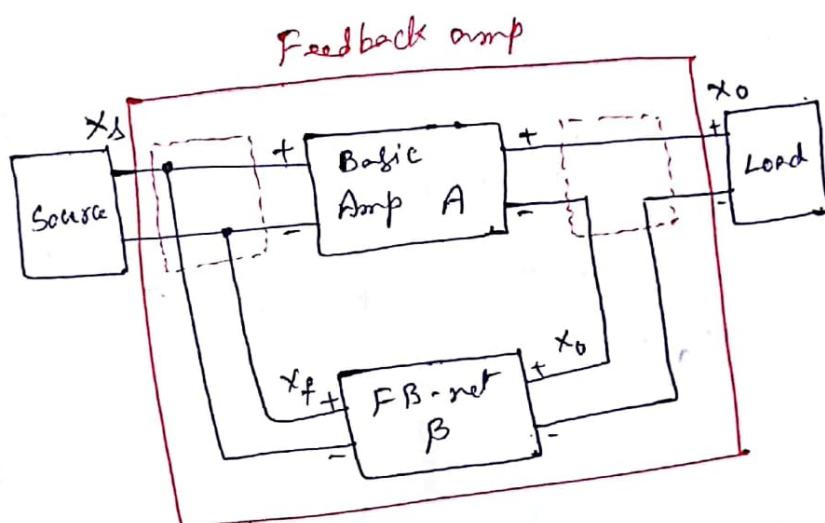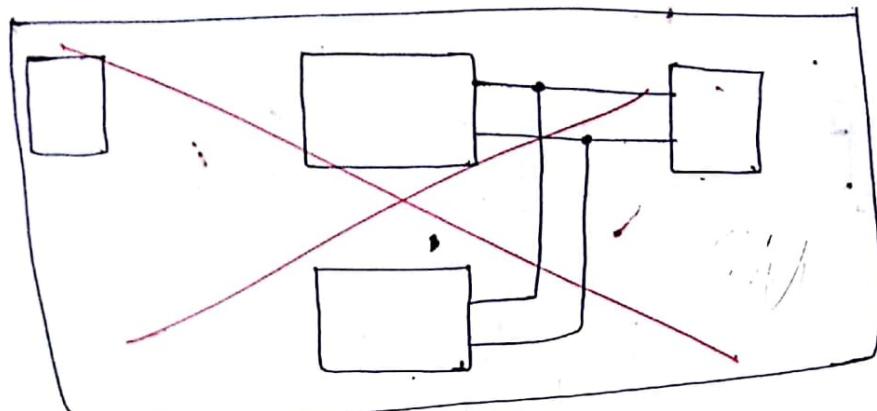④ Current-shunt Feedback amplifier  $[X_o = I_o, X_i = I_i, A = A_I = \frac{I_o}{I_i}]$



① Sampling  $\rightarrow$  Loop sampling or current sampling  
indicate output variable is current  $I_o$

② Mixing  $\rightarrow$  Shunt mixing  
indicate input variable is ~~voltage~~<sup>current</sup>  $I_i$

$$③ A \rightarrow A_I = \frac{X_o}{X_i} = \frac{I_o}{I_i}$$

$$④ \beta \rightarrow \beta = \frac{X_f}{X_o} = \frac{I_f}{I_o}$$

$$⑤ A_f \rightarrow A_{If} = \frac{X_o}{X_f} = \frac{I_o}{I_f} = \frac{A_I}{(1 + A_I \beta)}$$

$$⑥ R_{if} = \frac{R_i}{(1 + A_I \beta)} \quad \& \quad R_{of} = R_o (1 + A_I \beta)$$


(P.T.O.)

(9) Effect of Negative Feedback on input and output impedances:

Derivation of  $R_{if}$  and  $R_{of}$  for 4 topologies:

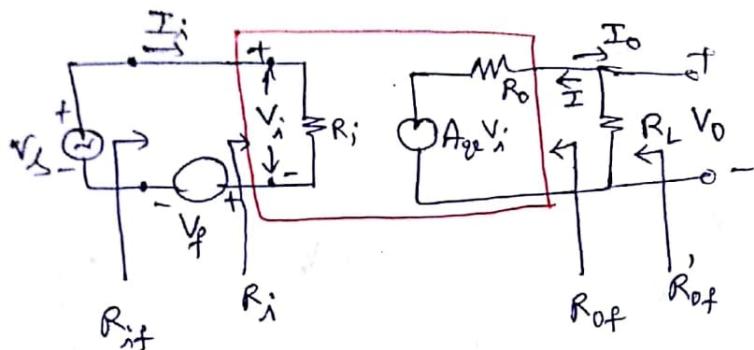(a) voltage series feedback topology:

The linear circuit with voltage series feedback is as shown below.



① input impedance ( $R_{if}$ ) : we know  $R_i = \frac{V_i}{I_i}$

$\rightarrow R_{if}$  is defined as

$$R_{if} = \frac{V_i}{I_i}$$

from S/P ckt we have

$$\begin{aligned} V_f &= V_i + V_f \\ &= V_i + \beta V_o \\ &= V_i + A\beta V_i \end{aligned}$$

$$V_f = V_i (1 + A\beta)$$

$$V_i = \frac{V_i (1 + A\beta)}{\beta}$$

$$\therefore R_{if} = \frac{V_i}{I_i}$$

$$\boxed{\therefore R_{if} = R_i (1 + A\beta)}$$

$$\left( \because \beta = \frac{X_o}{X_f} = \frac{V_o}{V_f} \right)$$

$$\left( \because A_v = \frac{A_v R_L}{R_L + R_o} \right)$$

$$\left( \therefore R_i = \frac{V_i}{I_i} \right)$$

② Output impedance ( $R_{of}$ ) : we know  $R_o = \frac{V_o}{I_o} = \frac{V_o}{I}$

The o/p impedance is defined as the ratio of voltage ( $V$ ) impressed between o/p terminals to the current ( $I$ ) flowing through o/p terminals when  $R_L = \infty$  and  $V_o = 0$  (or  $I_o = 0$ ).

(P.T.O.)

Let a voltage  $V$  is applied between o/p terminals ( $V = V_o$ ) and the current through o/p terminals is  $I$  and  $R_L$  is disconnected (i.e.  $R_L = \infty$ ). &  $R_{of} = \frac{V}{I}$   
then the Current  $I$  is given by

$$I = \frac{V - A_{v2} V_i}{R_o}$$

from o/p KVL we have

$$V_o - V_i - V_f = 0$$

$$\text{set } V_o = 0$$

$$\therefore V_i = -V_f = -\beta V_o$$

$$V_i = -\beta V$$

$$\therefore \beta = \frac{x_f}{x_o} = \frac{V_f}{V_o} = \frac{V_f}{V}$$

$$\beta = \frac{x_f}{x_o} = \frac{V_f}{V_o} = \frac{V_f}{V}$$

$$\therefore I = \frac{V + A_{v2}\beta V}{R_o}$$

$$I = \frac{V(1 + A_{v2}\beta)}{R_o}$$

$$\therefore R_{of} = \frac{V}{I} = \frac{R_o}{1 + A_{v2}\beta}$$

$$\therefore R_{of} = \frac{R_o}{1 + A_{v2}\beta}$$


With load resistance  $R_L$  the o/p impedance is  $R'_{of}$

$$R'_{of} = R_{of} \parallel R_L$$

$$R'_{of} = \frac{R_o}{1 + A_{v2}\beta}$$

Note:  $R_{if} \gg R_i$  and  $R_{of} \ll R_o$  hence this amplifier  
~~functions as a very good voltage amplifier~~

(b) current-series FB topology:

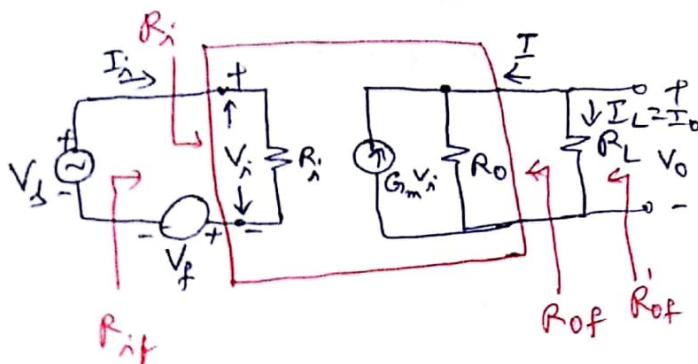

① input impedance ( $R_{if}$ ) we know

$$R_i = \frac{V_i}{I_i}$$

$R_{if}$  is defined as

$$R_{if} = \frac{V_s}{I_i}$$

from opamp ckt we have

$$V_s - V_i - V_f = 0$$

$$\therefore V_s = V_i + V_f \\ = V_i + \beta I_o$$

$$\beta = \frac{x_o}{x_o} = \frac{V_f}{I_o}$$

$$G_m = \frac{I_o}{V_i}$$

$$V_s = V_i + G_m \beta V_i$$

$$\therefore V_s = V_i (1 + G_m \beta)$$

$$\therefore R_{if} = \frac{V_s}{I_i} = \frac{V_i (1 + G_m \beta)}{I_i}$$

$$\therefore R_{if} = R_i (1 + G_m \beta)$$

② output impedance ( $R_{of}$ )

The o/p impedance is defined as the ratio of voltage ( $V$ ), impressed between o/p terminals, to the current ( $I$ ) flowing into o/p terminals when  $R_L = \infty$  and  $V_s = 0$  (or  $I_s = 0$ ).

$$\begin{aligned} & [2+1] \\ & [2+1] \\ & (2+2+1) \end{aligned}$$

Let a voltage  $V$  is impressed between o/p terminals ( $V = V_o$ ) and the current through o/p terminals is  $I$  and  $R_L$  is disconnected. Now  $R_{of}$  is defined as

$$R_{of} = \frac{V_o}{I} = \frac{V}{I}$$

According to the o/p mode given

$$I = \frac{V}{R_o} - G_m V_i$$

from o/p loop we have

$$V_S - V_i - V_f = 0$$

$$\text{set } V_S = 0$$

$$\begin{aligned} \therefore V_i &= -V_f \\ &= -\beta I_0 \\ &= +\beta I \end{aligned}$$

$$\left[ \begin{aligned} \therefore \beta &= \frac{x_f}{x_0} = \frac{V_f}{I_0} \\ \therefore I &= -I_0 \end{aligned} \right]$$

$$\therefore I = \frac{V}{R_o} - G_m \beta I$$

$$\therefore \frac{V}{R_o} = I (1 + G_m \beta)$$

$$\therefore R_{of} = \frac{V}{I} = R_o (1 + G_m \beta)$$

$$\boxed{\therefore R_{of} = R_o (1 + G_m \beta)}$$

Note:  $R_{if} \gg R_i$  and  $R_{of} \gg R_o$  hence this amplifier functions as a very good transconductance amplifier.

$$R'_{of} = R_{of} \| R_L = \frac{R_{of} R_L}{R_{of} + R_L} = \frac{R_o R_L (1 + G_m \beta)}{R_o + R_o G_m \beta + R_L}$$

$$= \frac{R_o R_L (1 + G_m \beta)}{(R_o + R_L) \left[ 1 + \frac{G_m \beta R_o}{R_o + R_L} \right]}$$


$$\boxed{\therefore R'_{of} = \frac{R_o (1 + G_m \beta)}{(1 + G_m \beta)}}$$

(P.T.O.)

13
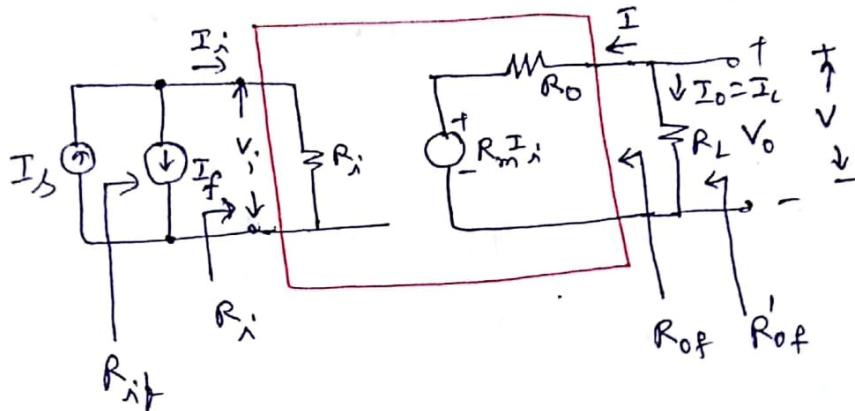
### C) Voltage-shunt FB amplifier:

The linear circuit of a voltage-shunt FB amplifier is shown below.



#### ① Input impedance ( $R_{if}$ ):

We know  $R_i = \frac{V_i}{I_i}$  and  $R_{if}$  is defined as

$$R_{if} = \frac{V_i}{I_s}$$

~~KCL to S/P mode gives~~

$$\begin{aligned} I_s - I_f - I_i &= 0 \\ \therefore I_s &= I_i + I_f \\ &= I_i + \beta V_o \\ &= I_i + \beta R_M I_i \\ I_s &= I_i (1 + R_M \beta) \\ \therefore R_{if} &= \frac{V_i}{I_i (1 + R_M \beta)} \end{aligned}$$

$$R_{if} = \frac{R_i}{(1 + R_M \beta)}$$

$$\boxed{\beta = \frac{x_f}{x_o} = \frac{I_f}{V_o}}$$

$$\begin{aligned} \therefore V_o &= R_m I_i \times \frac{R_L}{R_L + R_o} \\ &= R_m I_i \end{aligned}$$

where  $R_m = R_m \frac{R_L}{R_L + R_o}$

② current sheet

Output impedance;  $R_{of}$  =

The o/p Impedance is defined as the ratio of voltage ( $V$ ), impressed between o/p terminals, to the current ( $I$ ) flowing into o/p terminals when  $R_L = \infty$  and  $V_S = 0$  ( $I_A = 0$ )

Let a voltage  $V$  is impressed between o/p terminals ( $V = V_0$ ) and the current through o/p terminals is  $I$  and  $R_L$  is disconnected (i.e.  $R_L = \infty$ ). Now  $R_{of}$  is defined as

$$R_{of} = \frac{V_0}{I} = \frac{V}{I}$$

from o/p Ckt

$$I = \frac{V - R_m I_A}{R_o}$$

from input mode we have

$$I_S - I_A - I_f = 0$$

$$\therefore I_A = 0$$

$$\therefore I_A = -I_f \\ = -\beta V_0$$

$$I_A = -\beta V$$

$$\therefore I = \frac{V + R_m \beta V}{R_o}$$

$$I = \frac{V(1 + R_m \beta)}{R_o}$$

$$\therefore R_{of} = \frac{V}{I} = \frac{R_o}{1 + R_m \beta}$$

$$\boxed{\therefore R_{of} = \frac{R_o}{1 + R_m \beta}}$$

$$\left[ \begin{aligned} \beta &= \frac{x_f}{x_o} = \frac{I_f}{V_0} \\ \therefore V &= V_0 \end{aligned} \right]$$

$$\therefore R'_{of} = R_{of} || R_L = \frac{R_{of} R_L}{R_{of} + R_L} = \frac{R_o R_L}{R_o + R_L(1 + R_m \beta)}$$


$$= \frac{R_o R_L}{R_o + R_L + R_m \beta R_L} = \frac{R_o R_L}{(R_o + R_L) \left[ 1 + \frac{R_m R_L \beta}{R_o + R_L} \right]} = \frac{R_o}{1 + R_m \beta}$$

$$\boxed{\therefore R'_{of} = \frac{R_o}{1 + R_m \beta}}$$

(P.T.O.) ... 12

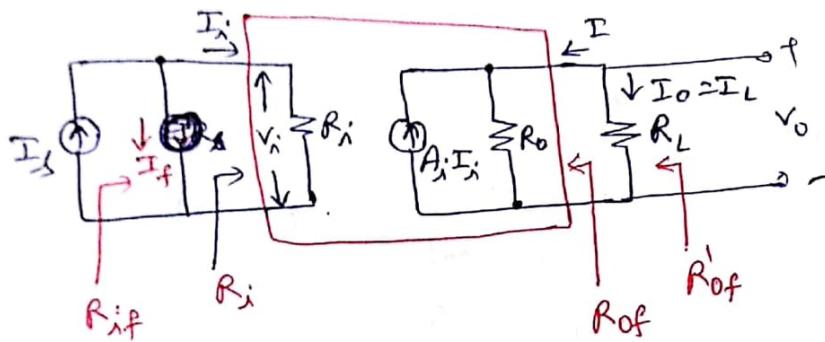(d) Current-shunt FB topology:  $A_I = \frac{I_o}{I_i}$

The linear circuit for current-shunt FB amplifier is shown below.



① input impedance ( $R_{if}$ )

$$\text{We know } R_i = \frac{V_i}{I_i} \quad \text{and}$$

$$R_{if} = \frac{V_i}{I_f}$$

KCL at 1st node given

$$I_s - I_f - I_i = 0$$

$$\therefore I_s = I_i + I_f$$

$$\beta = \frac{x_f}{x_o} = \frac{I_f}{I_o}$$

$$I_s = I_i + \beta I_o$$

$$\text{but } I_o = A_i I_i \times \frac{R_o}{R_o + R_L}$$

$$\therefore I_o = A_I I_i$$

$$\therefore I_s = I_i + A_I \beta I_i = I_i (1 + A_I \beta)$$

$$\therefore R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + A_I \beta)} = \frac{R_i}{(1 + A_I \beta)}$$

$$\boxed{R_{if} < R_i}$$

(P.T.O.)

## ② Output Impedance ( $R_{of}$ ):

The o/p impedance is defined as the ratio of voltage ( $V$ ), impressed between o/p terminals, to the current flowing into o/p terminals when  $R_L = \infty$  and  $V_S = 0$  ( $I_S = 0$ ).

$$V_S = 0 \quad (I_S = 0)$$

Let a voltage  $V$  is impressed between o/p terminals ( $V_o = V$ ) and the current through o/p terminal is  $I$  and  $R_L$  is disconnected. Now  $R_{of}$  is defined as

$$R_{of} = \frac{V_o}{I} = \frac{V}{I}$$

from the o/p circuit

$$I = \frac{V}{R_o} - A_{oi} I_i$$

from o/p mode we have

$$I_S - I_f - I_i = 0$$

$$\text{but } I_S = 0$$

$$\therefore I_i = -I_f \\ = -\beta I_o$$

$$\therefore I_i = +\beta I$$

$$\therefore I = \frac{V}{R_o} - A_{oi} \beta I$$

$$\therefore \frac{V}{R_o} = I (1 + A_{oi} \beta)$$

$$\therefore R_{of} = \frac{V}{I} = R_o (1 + A_{oi} \beta)$$

$$\therefore R_{of} = R_o (1 + A_{oi} \beta)$$

$$\beta = \frac{X_f}{X_o} = \frac{I_f}{I_o}$$

$$\text{but } I_o = -I$$

$$R_{of} \gg R_o$$

$$\therefore R'_o = R_{of} // R_L = \frac{R_{of} R_L}{R_{of} + R_L} = \frac{R_o (1 + A_{oi} \beta) R_L}{R_o + R_L + A_{oi} \beta R_o}$$

$$= \frac{R_o R_L (1 + A_{oi} \beta)}{(R_o + R_L) \left[ 1 + \frac{A_{oi} \beta R_o}{R_o + R_L} \right]} = R_o \frac{(1 + A_{oi} \beta)}{(1 + A_I \beta)}$$

$$\therefore R'_o = R_o \frac{1 + A_{oi} \beta}{1 + A_I \beta}$$

(P.T.O.)  
15

### (16) Effect of -ve FB on Frequency response:

We know the gain with feedback is given by

$$A_f = \frac{A}{1+AB}$$

The frequency response of an amplifier with feedback is to be studied in Mid, Low and High frequency regions, and the Band width of the amplifier depends on the cut off frequencies.

#### Case 1: Mid Frequency Region:

We know the gain in Mid frequency region is independent of frequency and represented with  $A_{mid}$ .

Therefore the gain in Mid band region with feedback is given by

$$A_f = \frac{A_{mid}}{1+A_{mid}B}$$

#### Case 2: Low Frequency Region:

We know the gain in Low frequency region is given by

$$A_{LF} = A_{Lfreq} = \frac{A_{mid}}{1-j\frac{f_L}{f}}$$

So in the expression of  $A_f$ ,  $A$  is to be replaced with  $A_{LF}$ .

Major frequency

$$\begin{aligned}
 A_{LFF} &= \frac{A_{LF}}{1 + A_{LF}\beta} \\
 &= \frac{A_{mid}}{\left[1 - j \frac{f_L}{f}\right] \left[1 + \frac{A_{mid}\beta}{\left(1 - j \frac{f_L}{f}\right)}\right]} \\
 &= \frac{A_{mid}}{1 + A_{mid}\beta - j\left(\frac{f_L}{f}\right)} \\
 &= \frac{A_{mid}}{1 + A_{mid}\beta} \cdot \frac{1}{\left[1 - j \frac{f_L}{f(1 + A_{mid}\beta)}\right]}
 \end{aligned}$$

$$\therefore A_{LFF} = \frac{A_f}{1 - j\left(\frac{f_{Lf}}{f}\right)}$$

where  $A_f = \frac{A_{mid}}{1 + A_{mid}\beta}$

$$f_{Lf} = \frac{f_L}{1 + A_{mid}\beta}$$

$$f_{Lf} < f_L$$

### Case 3: High Frequency Region

We know the gain in High frequency Region is given by

$$A_{HF} = \frac{A_{mid}}{1 + j\left(\frac{f}{f_H}\right)}$$

So, in the expression of  $A_f$ ,  $A$  is to be replaced with  $A_{HF}$ ; to obtain the gain with feedback with in High frequency region.

(P.T.O.)

$$\therefore A_{HFf} = \frac{A_{HF}}{1 + A_{HF}\beta}$$

$$= \frac{A_{mid}}{\left[1 + j \frac{f}{f_H}\right] \left[1 + \frac{A_{mid}\beta}{1 + j\left(\frac{f}{f_H}\right)}\right]}$$

$$= \frac{A_{mid}}{1 + A_{mid}\beta + j \cdot \frac{f}{f_H}}$$

$$= \frac{A_{mid}}{(1 + A_{mid}\beta)} \times \frac{1}{\left[1 + j \frac{f}{6f_H(1 + A_{mid}\beta)}\right]}$$

$$\therefore A_{HFf} = \frac{A_f}{1 + j\left(\frac{f}{f_{HF}}\right)}$$

where

$$A_f = \frac{A_{mid}}{1 + A_{mid}\beta}$$

$$f_{HF} = f_H(1 + A_{mid}\beta)$$

$$f_{HF} > f_H$$

Effect on Band width.

Ques: 4

Bandwidth of an amplifier is defined as

$$B.W. = f_H - f_L \approx f_H$$

with Feedback

$$(B.W.)_f = f_{HF} - f_{Lf} \approx f_{HF}$$

$$\begin{aligned} \therefore (B.W.)_f &\approx f_{HF} = f_H(1 + A_{mid}\beta) \\ &= (B.W.) \times (1 + A_{mid}\beta) \end{aligned}$$

$$\therefore B.W.f = B.W. \times (1 + A_{mid}\beta)$$

(P.T.O.)

Case : 5

Gain Band width product with feedback

The gain BW product of an amplifier with FB is given by

$$(GBP)_f = (\text{Gain})_f \times (\text{B.W.})_f$$

$$= A_f \times f_{HF}$$

$$= \frac{\text{Amid}}{(1 + \text{Amid}\beta)} \times f_H (1 + \text{Amid}\beta)$$


$$= \text{Amid} + f_H$$

$\therefore (GBP)_f = \text{G.B.P. without feedback}$

$$\therefore GBP_f = GBP_{wof}$$

Note: Negative feedback does not (change) effect the gain Band width Product. The decreament in gain with feedback is compensated with increment in Band width.

Frequency Response:

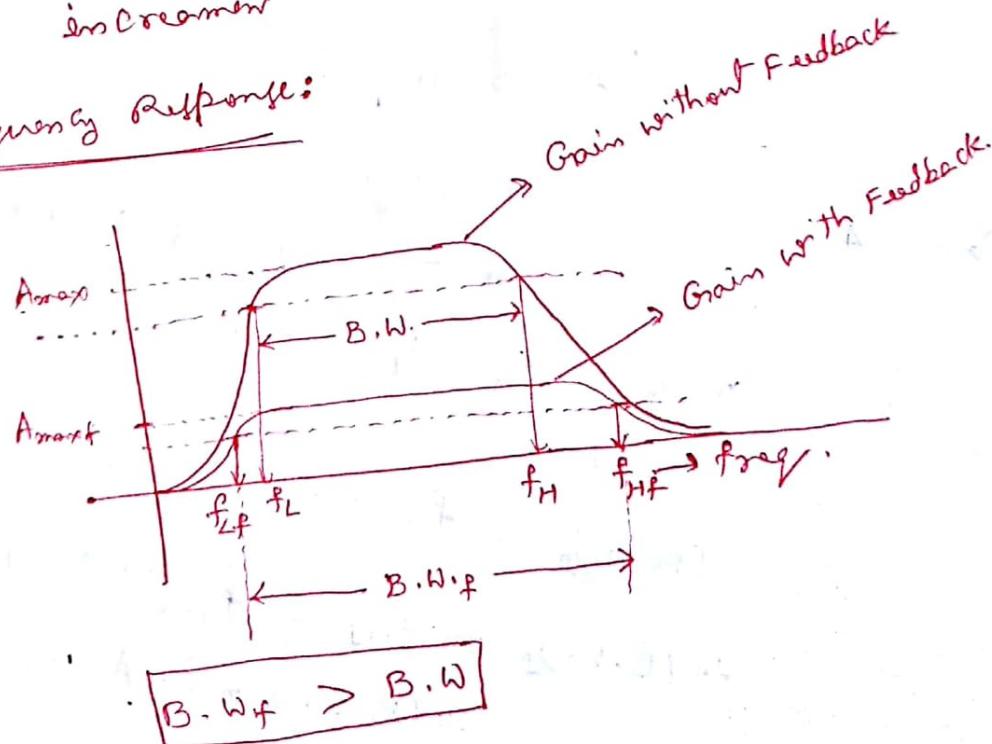

(P.T.O.)

17

## (10) Step-by-step procedure for the Analysis of -ve FB Amplifiers:

- Note: There are 3 fundamental assumptions ~~are~~ made for simplifying the Analysis procedure. These are.
- ① The input signal is transmitted to the output through the <sup>basic</sup> Amplifier A and not through the  $\beta$ -network.
  - ② The feedback signal is transmitted from output to input through the  $\beta$ -network and not through the amplifier.
  - ③ The reverse transmission factor  $\beta$  is independent of load, ( $R_L$ ) and source resistance ( $R_s$ ).

By Considering the above assumptions ① & ② the model for BJT to be used is given below.

### PROCEDURE

- ① Identify the topology.
  - a) Is the feedback signal  $x_f$  a voltage or current  
[in other words, is  $x_f$  applied in series or shunt with  $x_i$ ]
  - b) Is the sampled signal  $x_o$  a voltage or current?  
[in other words, is the sampled signal taken from output node or output loop?]
- ② Draw the basic amplifier circuit without feedback but taking the loading effect of  $\beta$ -network into account, as explained below.

② To find the input circuit:

- ① Set  $V_o = 0$  for voltage sampling i.e. short circuit o/p node
- ② Set  $I_o = 0$  for current sampling i.e. open o/p loop

③ To find the output circuit:

- ① Set  $V_i = 0$  for shunt compensation i.e. short circuit S/P node
- ② Set  $I_i = 0$  for series compensation i.e. open the S/P loop

④ Use a Thevenin source if  $x_f$  is a voltage and a Norton's source if  $x_f$  is a current.

⑤ Replace each active device by the proper model,

[h-parameter model ~~for~~ at low frequencies (or) hybrid- $\pi$  model  
at high frequencies.]

⑥ Indicate  $x_f$  and  $x_0$  on the ac equivalent obtained above.

⑦ Evaluate  $\beta = \frac{x_f}{x_0}$  and  $A$  by applying KVL or KCL to the above circuit.

⑧ From  $A$  and  $\beta$ , find  $D$ ,  $A_f$ ,  $R_{if}$ ,  $R_{of}$  and  $R'_f$ .

Table for Feedback amplifiers Analysis.


Characteristics	Topology			
	Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
① Source(Signal)	Thevenin	Thevenin	Norton	Norton
② $\beta = x_f/x_0$	$V_f/V_o$	$V_f/I_o$	$I_f/V_o$	$I_f/I_o$
③ $A = x_0/x_i$	$A_v = V_o/V_i$	$G_m = I_o/V_i$	$R_m = V_o/I_i$	$A_I = I_o/I_i$
④ $D = 1 + AB$	$1 + A_v\beta$	$1 + G_m\beta$	$1 + R_m\beta$	$1 + A_I\beta$
⑤ $A_f = \frac{A}{D}$	$A_v/D$	$G_m/D$	$R_m/D$	$A_I/D$
⑥ $R_{if}$	$R_i D$	$R_i D$	$R_i/D$	$R_i/D$
⑦ $R_{of}$	$\frac{R_o}{1 + A_v\beta}$	$R_o(1 + G_m\beta)$	$\frac{R_o}{1 + R_m\beta}$	$R_o(1 + A_I\beta)$
⑧ $R'_f$	$\frac{R'_o}{D}$	$\frac{R'_o}{D}(1 + G_m\beta)$	$\frac{R'_o}{D}$	$\frac{R'_o}{D}(1 + A_I\beta)$

## (11) Analysis of Voltage-Series FB Amplifier

- ① FET Source Follower } These two circuits are the examples  
 ② The Emitter Follower } for voltage-series F-B ampl.

### ① Source-Follower:

The circuit is as shown below

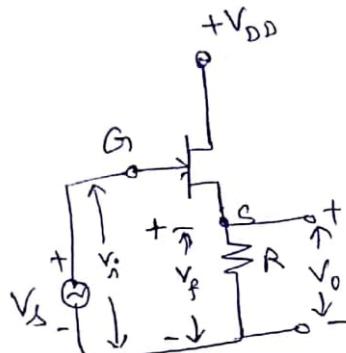

Hint: KVL to SLP loop


$V_g - V_{gs} - V_0 = 0$   
 Since  $V_g - V_{gs}$  is appearing on SLP side, hence  
 op voltage is appearing in the loop and the  
 here it is voltage sampling. and the  
 op voltage is appearing in the loop  
 hence it is series mixing.

Step 1: Identifying the topology:  
 the output voltage  $V_0$  is appearing in the input loop  
 and the voltage across  $R$  ( $V_f$ ) is fed back. Hence  
 here is the topology of the circuit is voltage series.


$$\text{Hence } x_0 = V_0 \quad ; \quad x_i = V_i \quad \& \quad x_f = V_f$$

Step 2: To obtain input ckt set  $V_0 = 0$  and  
 To obtain output ckt set  $I_i = 0$  (open gate terminal)  
 Then obtain the ac equivalent circuit without feedback and  
 including the loading effect of  $\beta$  network ( $R$ ).


Step

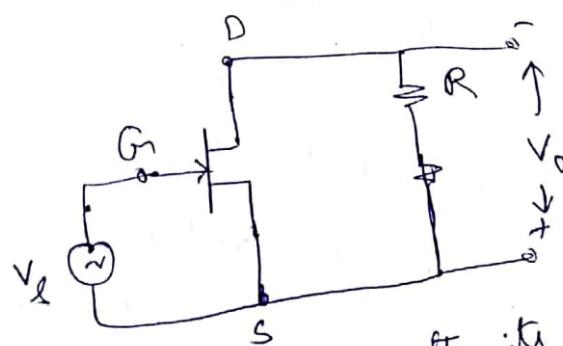

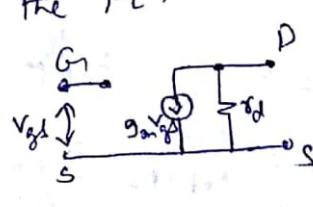Step 3: Replace the FET with its low frequency model



(P.T.O.)

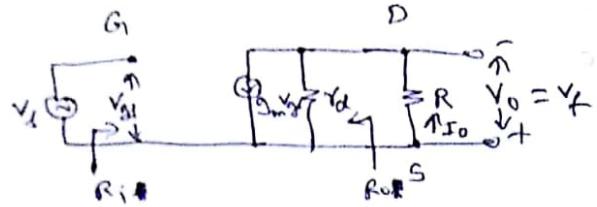

Step 4: (a)  $\therefore \beta = \frac{V_f}{V_o} = \frac{V_f}{V_o} = 1$

$$\boxed{\therefore \beta = 1}$$

(b)  $A_v = \frac{V_o}{V_i} = \frac{V_o}{V_i} = \frac{V_o}{V_{GS}} = \frac{V_o}{V_s}$

$$= \frac{g_m V_{GS} r_d R}{(r_d + R) V_{GS}}$$

$$\boxed{\therefore A_v = \frac{MR}{r_d + R}}$$

(c)  $\therefore D = 1 + A_v \beta = 1 + \frac{MR}{r_d + R}$

$$\therefore D = \frac{r_d + R + MR}{r_d + R} = \frac{r_d + R(1+M)}{r_d + R}$$

(d)  $\therefore A_{vf} = \frac{A_v}{D}$   
 $= \frac{MR}{\frac{r_d + R}{r_d + R(1+M)}}$

$$\boxed{\therefore A_{vf} = \frac{MR}{r_d + R(1+M)}}$$

(e) For this circuit  $R_i = \infty$   
 $\therefore R_{if} = R_i; D = \infty$

(f) We know  $R_{of}$  for voltage series FB amp given by  
 $R_{of} = \frac{R_o}{1 + \beta A_v}$  where  $R_o = r_d$  and  $\beta = g_m r_d$


$$A_{ve} = \frac{A_v}{R_L \rightarrow \infty} = \frac{1}{1 + M}$$

$$\therefore R_{of} = \frac{R_o}{1 + M} = \frac{r_d}{1 + M}$$

(g)  $R'_{if} = R_{of} \| R_L = \frac{R_{of} R_L}{R_{of} + R_L} = \frac{R_o R_L}{(R_o + R_L)[1 + M R_L / R_o + R_L]} = \frac{R'}{1 + A_v}$

where  $R_L = R$ ,  $R' = R_o \| R_L = R_o / (1 + M R)$   
 P.T.O. - 19


(b) The Emitter Follower:

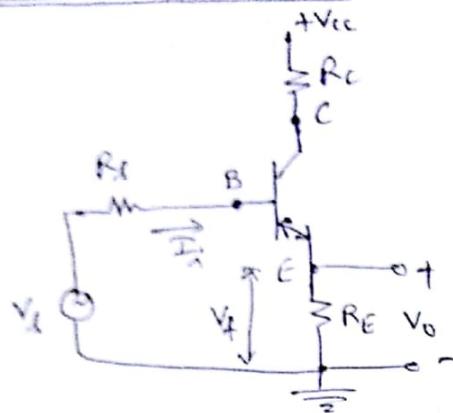



Step 1: Identify the topology:

The output voltage  $V_o$  is appearing in the input loop and the voltage across  $R$  ( $V_f$ ) is fed back. Therefore the circuit is Common Emitter with voltage series feedback.  
Hence:  $x_0 = V_o$ ;  $x_i = V_i$ ,  $x_f = V_f$  &  $x_d = V_d$

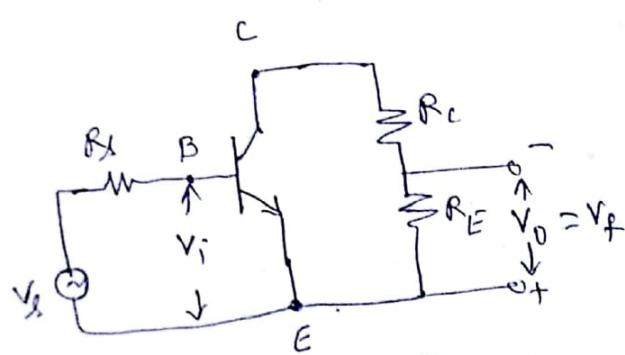Step 2: To obtain ac circuit set  $V_o = 0$  and to obtain output ac circuit set  $I_i = 0$  (open gate terminal). Then obtain the ac equivalent circuit without feedback and including the loading effect of  $\beta$ -network.



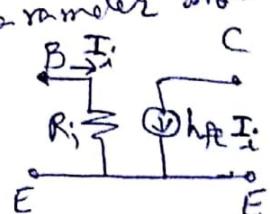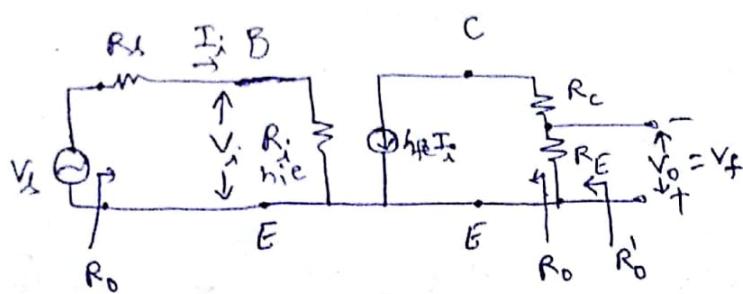Step 3: Replace BJT with its approximate h-parameter model.



Step 4:

$$\textcircled{a} \quad \beta = \frac{x_f}{x_i} = \frac{V_f}{V_i} = 1 \quad \boxed{\therefore \beta = 1}$$

$$\textcircled{b} \quad A_v = \frac{x_o}{x_i} = \frac{V_o}{V_i} = \frac{V_o}{V_f} \quad \boxed{\therefore A_v = A_{v_f} \text{ in FB amplifiers}}$$

$$\therefore A_v = h_{fe} I_i R_E$$

$$\text{but } I_i = \frac{V_i}{R_s + h_{ie}}$$

$$\boxed{\therefore A_v = \frac{h_{fe} R_E}{R_s + h_{ie}}}$$

$$\textcircled{c} \quad \therefore D = 1 + A_v \beta = 1 + \frac{h_{fe} R_E}{R_s + h_{ie}} \therefore = \frac{R_s + h_{ie} + h_{fe} R_E}{R_s + h_{ie}}$$

$$\textcircled{d} \quad \therefore A_{v_f} = \frac{A_v}{D} = \frac{h_{fe} R_E}{R_s + h_{ie} + h_{fe} R_E}$$

$$\textcircled{e} \quad R_i = \frac{V_i}{I_i} = R_s + h_{ie}$$

$$\therefore R_{if} = R_i D = (R_s + h_{ie}) \times \frac{R_s + h_{ie} + h_{fe} R_E}{(R_s + h_{ie})}$$

$$\boxed{\therefore R_{if} = R_s + h_{ie} + h_{fe} R_E}$$

\textcircled{f}  $R_o = \infty$ ;  $\therefore R_{of} = \frac{R_o}{D} = \infty$  but the amplifier has a finite output impedance. So to obtain  $R_{of}$  first calculate  $R'_{of}$  and then take  $L^T R'_{of}$  to get  $R_{of}$ .  $R_L \rightarrow \infty$

$$\therefore R'_{of} = \frac{R_o}{D} = \frac{R_E}{D} \quad \boxed{\therefore R'_o = R_E}$$

$$\boxed{R'_{of} = \frac{R_E (R_s + h_{ie})}{(R_s + h_{ie} + h_{fe} R_E)}}$$

$$\therefore R_{of} = L^T R'_{of}$$

$$R_E \rightarrow \infty$$

$$= L^T \frac{R_E (R_s + h_{ie})}{R_s + h_{ie} + h_{fe} R_E}$$

$$R_E \rightarrow \infty$$


$$\boxed{\therefore R_{of} = \frac{R_s + h_{ie}}{h_{fe}}}$$

Note: Can also obtain  $R_o$

$$R_{of} = \frac{R_o}{D} \Rightarrow R_o = R_{of} D = \frac{(R_s + h_{ie}) \times (R_s + h_{ie} + h_{fe} R_E)}{h_{fe}} \quad \boxed{2}$$

$$R_o = \frac{R_s + h_{ie} + h_{fe} R_E}{h_{fe}}$$
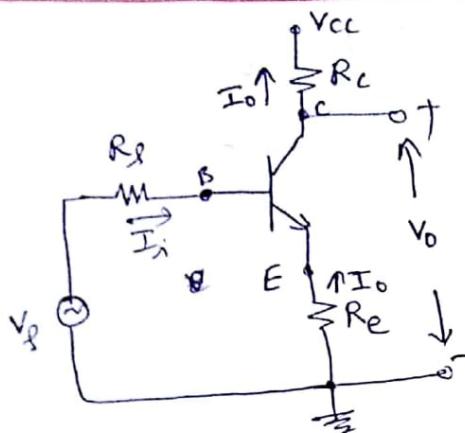
### (13) Analysis of current-series FB amp:




Hint: KVL to 1st loop  
 $V_f - I_o R_L - V_{be} - (I_o R_E) = 0$   
 o/p current is appearing on o/p side  
 hence o/p current is sampled and  
 $I_o$  is appearing in the loop  
 hence it is series mixing.

Step 1: Identifying the topology:  
 The output current is appearing in input loop hence

The circuit is conforming Current-series FB topology.  
 Hence  $x_o = I_o$ ,  $x_i = V_f$ ;  $x_L = V_o$  &  $x_f = V_f$

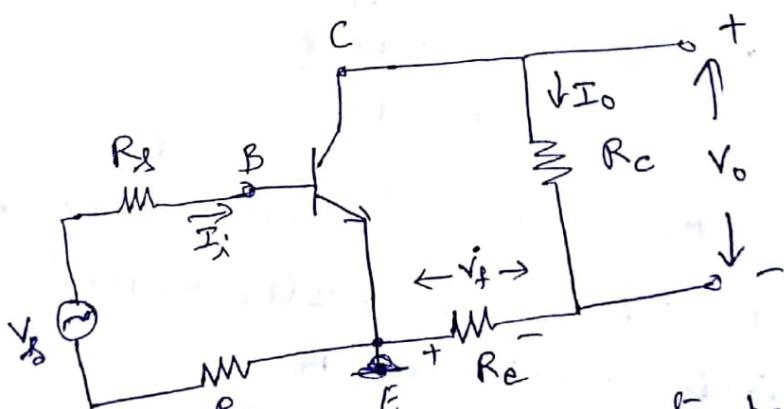Step 2: To obtain input ckt set  $I_o = 0$ , so open at  
 collector terminal and to obtain output equivalent  
 circuit set  $I_o \neq 0$  (series mixing), so, open Base terminal.  
 Draw the ac equivalent ckt



Step 3: Replace BJT with its approximate h-parameter model.

$$\frac{g_m + 1}{g_m + 1 + \beta} = 10^9$$


$$\text{and } g_m = 10^9 \text{ and } \beta = 10^9$$

$$\alpha_{BJT} = \frac{g_m}{g_m + 1} = 10^9 \text{ (approx)}$$

$$\beta_{BJT} = \beta = 10^9$$

$$\beta_{BJT} = \beta = 10^9$$

(P.T.O.)

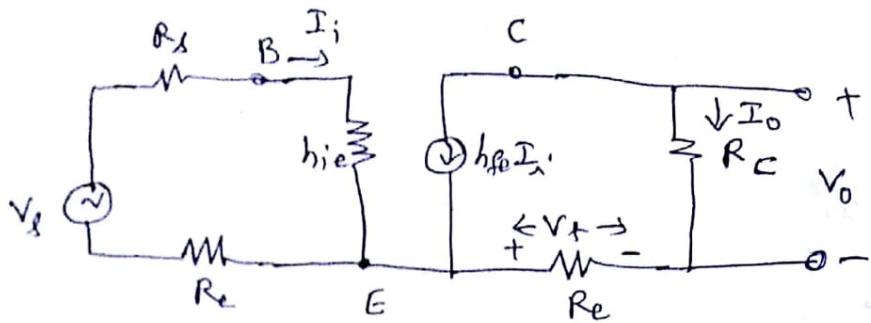

Step 4: (a)  $\beta = \frac{x_f}{x_i} = \frac{V_f}{I_0} = \frac{-R_E I_0}{I_0} = -R_E \therefore \beta = -R_E$

(b)  $A = \frac{x_o}{x_i} = \frac{x_o}{x_L} = \frac{I_0}{V_s} = G_M$

$$\begin{aligned} \therefore G_M &= \frac{I_0}{V_s} \\ &= \frac{-h_{fe} I_B}{V_s} \\ &= \frac{-h_{fe} \cancel{I_B}}{\cancel{R_x + h_{ie} + R_E}} \end{aligned}$$

$\therefore G_M = \frac{-h_{fe}}{(R_x + h_{ie} + R_E)}$

(c)  $D = 1 + G_M \beta$

$$= 1 + \frac{h_{fe} R_E}{R_x + h_{ie} + R_E}$$

$\therefore D = \frac{R_x + h_{ie} + (1+h_{fe}) R_E}{R_x + h_{ie} + R_E}$

(d)  $\therefore G_{Mf} = \frac{G_M}{D} = \frac{-h_{fe}}{R_x + h_{ie} + (1+h_{fe}) R_E}$

(e)  $R_{if} = R_x D \quad ; \quad R_i = (R_x + h_{ie} + R_E)$

$\therefore R_{if} = R_x + h_{ie} + (1+h_{fe}) R_E$

(f)  $R_o = \infty$  then  $R_{of} = R_o D = \infty$  if

$R'_{of} = R_{of} \parallel R_C = R_C$   
alternate formula for  $R'_{of}$  is given by


$$R'_{of} = R'_o \frac{1 + G_M \beta}{1 + G_M \beta}$$

we know  $\frac{G_m}{R_{of}} = L \frac{R_C}{R_L} G_M = G_M \quad \left[ \because G_M \neq f(R_L) \right]$

$\therefore R'_{of} = R'_o = R_L$

P.T.O... (2)
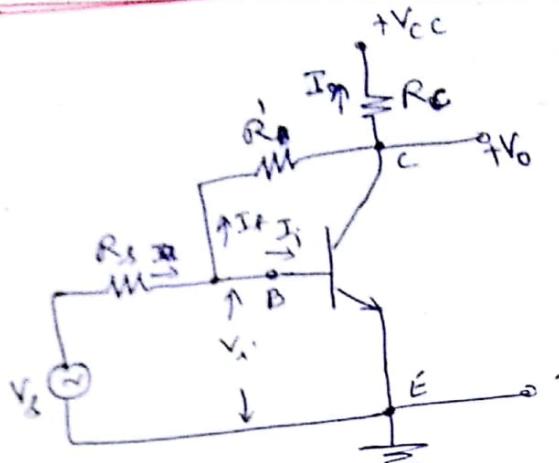
## (12) Analysis of Voltage shunt FB Amp:



Hint: KCL to SLP node

$$I_S - I_i - I_f = 0$$


$I_S - I_i - \left( \frac{V_0 + V_i}{R_f} \right) = 0$

o/p voltage is appearing in SLP  
KCL, hence off voltage sampling  
and shunt mixing.

Step 1: identifying the topology:


Feedback is taken from output node hence it is ~~output~~ sampling  
the mixing at Base is in shunt hence shunt mixing.  
Therefore the circuit conforms voltage-shunt Feedback topology.

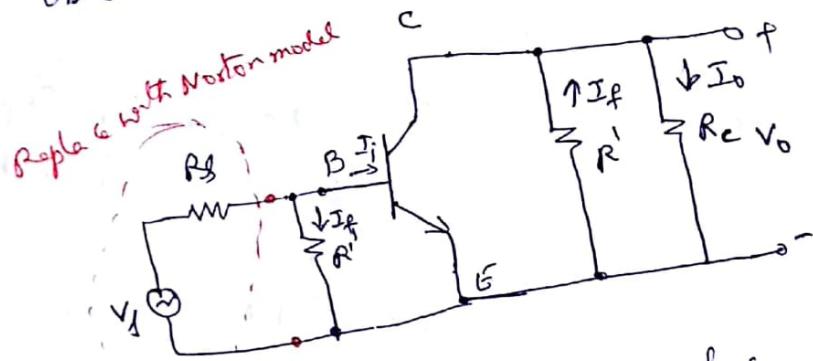Step 2: To obtain SLP equivalent circuit set  $V_0 = 0$ , so short o/p node.  
To obtain o/p equivalent circuit set  $V_i = 0$ , so short SLP node.



Step 3: Since the mixing is shunt, replace the source with its equivalent Norton model and replace BJT with its approximate h-parameter model.

(P.T.O.)

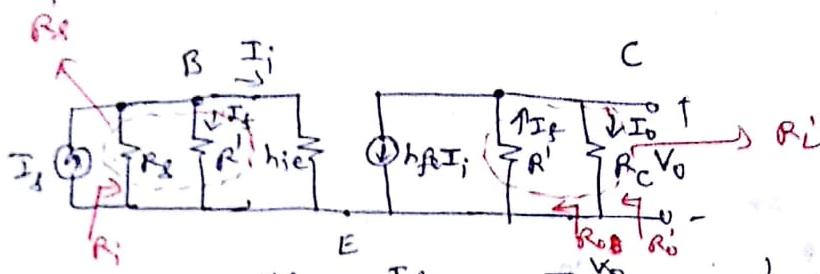

Step 4: (a)  $\beta = \frac{x_f}{x_0} = \frac{I_f}{V_0} = \frac{-V_0}{R' V_0} = -\frac{1}{R'}$

$$\therefore \beta = -\frac{1}{R'}$$

(b)  $A = \frac{x_0}{x_i} = \frac{x_0}{x_s} = \frac{V_0}{I_s} = \frac{-h_{fe} I_s R'_L}{I_s}$  where  $R'_L = R' || R_C$

but  $I_i = I_s \times \frac{R'_s}{R'_s + h_{ie}}$

$$\therefore A = -\frac{h_{fe} R'_s R'_L}{(R'_s + h_{ie})} = R_M$$

$$\therefore R_M = -\frac{h_{fe} R'_s R'_L}{R'_s + h_{ie}}$$

(c)  $D = 1 + R_M \beta = 1 + \frac{h_{fe} R'_s R'_L}{R' (R'_s + h_{ie})}$

$$\therefore D = \frac{h_{fe} R'_s R'_L + R' (R'_s + h_{ie})}{R' (R'_s + h_{ie})} \quad \frac{h_{fe} R'_s R'_L}{(R'_s + h_{ie})}$$

(d)  $\therefore R_{Mf} = \frac{R_M}{D} = -\frac{h_{fe} R'_s R'_L + R' (R'_s + h_{ie})}{h_{fe} R'_s R'_L + R' (R'_s + h_{ie})}$

$$\therefore R_{Mf} = -\frac{h_{fe} R'_s R'_L R'}{(h_{fe} R'_s R'_L + R'_s R' + h_{ie} R')}$$

(e)  $R_{if} = \frac{R_i}{D} = \frac{R_s || R' || h_{ie}}{D}$

(f)  $R_o = R'$  and  $R_{of} = \frac{R_o}{1 + R_m \beta}$

Now  $R_m$  is to be calculated as  $R_m = L_T R_M$   $R_C \rightarrow \infty$

$$\therefore R_m = -\frac{h_{fe} R'_s}{R'_s + h_{ie}} \times L_T R'_L \quad R_C \rightarrow \infty$$

$$\text{but } R'_L = R_C || R' \\ \text{as } R_C \rightarrow \infty \quad R'_L \rightarrow R'$$

$$\therefore R_m = -\frac{h_{fe} R'_s R'}{R'_s + h_{ie}}$$

$$\therefore 1 + R_m \beta = 1 + \frac{h_{fe} R'_s R'}{(R'_s + h_{ie}) R'} = \frac{R'_s (1 + h_{fe}) + h_{ie}}{(R'_s + h_{ie})}$$


(P.T.O.) (22)

$$\therefore R_{of} = \frac{R_o}{1 + R_m \beta} = \frac{R'(R'_L + h_{ie})}{R'_L(1 + h_{fe}) + h_{ie}}$$

$$\therefore R_{of} = \frac{R'(R'_L + h_{ie})}{R'_L(1 + h_{fe}) + h_{ie}}$$

$$\therefore R'_{of} = R_{of} \parallel R_C$$

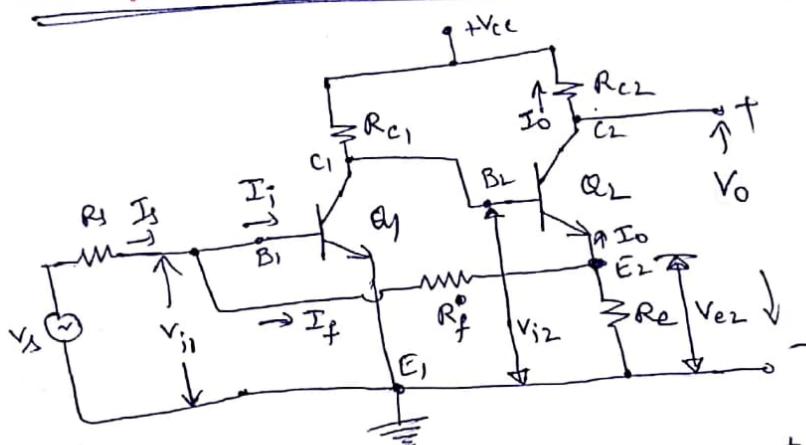
### (A) Analysis of Current-shunt FB Amp:



Hint: KCL to o/p node  
 $I_S - I_i - I_f = 0$   
 $bV_T - I_f = (-I_O) \frac{R_E}{R_E + R'_f} \quad \because V_{i1} = 0$   
 $\therefore I_S - I_i - I_O \frac{R_E}{R_E + R'_f} = 0$   
So,  $I_O$  is sampled and  
mixing is in shunt.


Step 1: Feedback signal is taken from output loop, hence it is current sampling and feedback signal is mixing in shunt with source, hence shunt mixing. Therefore the 3rd Conformal Current-shunt topology.

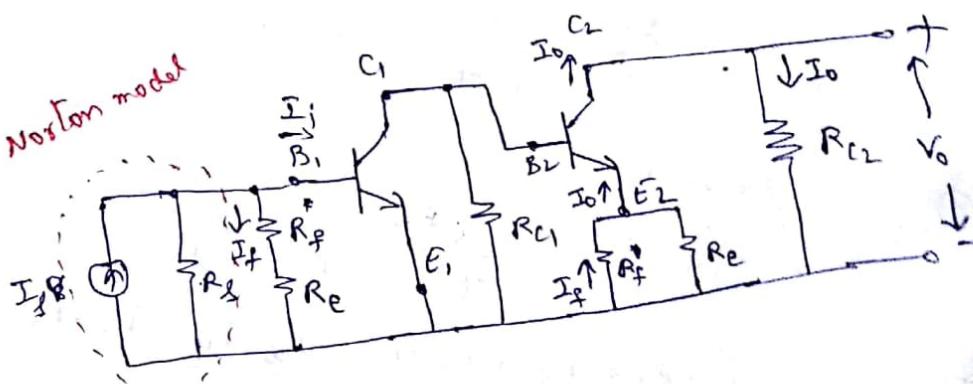Step 2: To obtain the o/p circuit set  $I_O = 0$ , so open at  $C_2$  terminal and to obtain the o/p circuit set  $V_i = 0$



(P.T.O.)

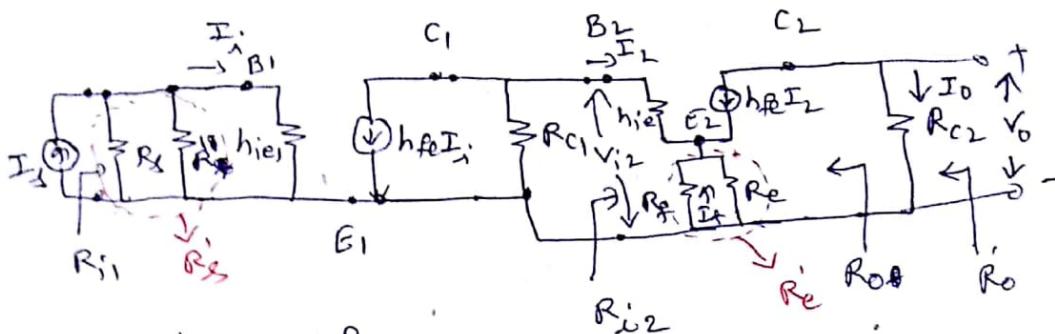Step ③: Replace BJT with approximate h-parameter models.



$$\text{where } R' = R_f + R_e$$

$$R'_s = R_s \parallel R'$$

$$R'_e = R_f \parallel R_e$$

$$\text{Step 4: (a) } \beta = \frac{I_f}{I_s} = \frac{I_f}{I_o} = \frac{R_e}{R_e + R_o} \quad I_f = I_o \times \frac{R_e}{R_e + R_f}$$

$$(b) A_I = \frac{I_o}{I_s} = \frac{I_o}{I_2} \times \frac{I_2}{I_1} \times \frac{I_1}{I_s}$$

$$I_o = -h_{fe} I_2 \Rightarrow \frac{I_o}{I_2} = -h_{fe}$$

$$I_2 = -h_{fe} I_1 \times \frac{R_{c1}}{R_{c1} + R_{i2}} \quad \text{where } R_{i2} = \frac{V_{i2}}{I_2}$$

$$\therefore \frac{I_2}{I_1} = -\frac{h_{fe} R_{c1}}{R_{c1} + R_{i2}}$$

$$V_{i2} = h_{ie} I_2 + (1+h_{fe}) I_2 R'_e$$

$$\therefore \frac{V_{i2}}{I_2} = h_{ie} + (1+h_{fe}) R'_e$$

$$I_1 = I_s \times \frac{R'_s}{R'_s + h_{ie}}$$

$$\therefore \frac{I_1}{I_s} = \frac{R'_s}{R'_s + h_{ie}}$$

$$\therefore A_I = [-h_{fe}] \times \left[ \frac{-h_{fe} R_{c1}}{R_{c1} + R_{i2}} \right] \times \left[ \frac{\frac{R'_s}{R'_s + h_{ie}}}{R'_s + h_{ie}} \right]$$

$$A_I = h_{fe} \times \frac{R_{c1}}{R_{c1} + R_{i2}} \times \frac{R'_s}{R'_s + h_{ie}}$$

$$(c) D = 1 + A_I \beta$$

$$= 1 + \frac{h_{fe} R_{c1} R'_s R_e}{(R_{c1} + R_{i2})(R'_s + h_{ie})(R_e + R_f)}$$

$$\therefore D = \frac{h_{fe} R_{c1} R'_s R_e + (R_{c1} + R_{i2})(R'_s + h_{ie})(R_e + R_f)}{(R_{c1} + R_{i2})(R'_s + h_{ie})(R_e + R_f)}$$

(P.T.O.) ... 23

(23)

$$\textcircled{d} \quad A_{If} = \frac{A_I}{D}$$

$$A_{If} = \frac{h_{fe} R_{c1} R'_s (R_e + R_f)}{h_{fe} R_{c1} R'_s R_e + (R_{c1} + R_{j2}) (R'_s + h_{ie}) (R_e + R_f)}$$

$$\textcircled{e} \quad R_i' = R_s \parallel R' \parallel h_{ie}$$

$$\therefore R_{if} = \frac{R_i'}{D}$$

$$\textcircled{d} \quad R_{of} = R_o D \quad \text{but } R_o = \infty; \therefore R_{of} = \infty$$

$$R'_o = R_o \parallel R_L = R_{c2}$$

$$R'_o = R_o \parallel R_L = R_{c2}$$

$$\therefore R'_o = R'_o = R_{c2}.$$