

Introduction :

Almost all-electronic equipment (communication, instrumentation, control, and data processor) and its subsystems require stabilized dc power supplies of different voltage levels. To cite few examples, all PCs require $\pm 5V$, $+12V$ dc supplies. Similarly, analog circuits using operational amplifiers, instrumentation amplifier, analog to digital converter, digital to analog converters etc. require $\pm 12V$ or $\pm 15V$. The industrial control loops work on $24V$ dc. The RADAR units require $10KV-15KV$ dc power supplies. The power ratings of these dc supplies may vary from a few watts to a few kilowatts. Hence we must know the requirements of dc power supplies. A dc power supply must meet the following requirement :

- ◆ Better Line Regulation,
- ◆ Better Load Regulation,
- ◆ Higher Conversion Efficiency,
- ◆ Higher power density for reduction in size and weight,
- ◆ Less Harmonics in Input and Output Waveform for reduction in Filter size,
- ◆ Higher reliability.

The regulated (stabilized) dc power supply family can be categorized as ;

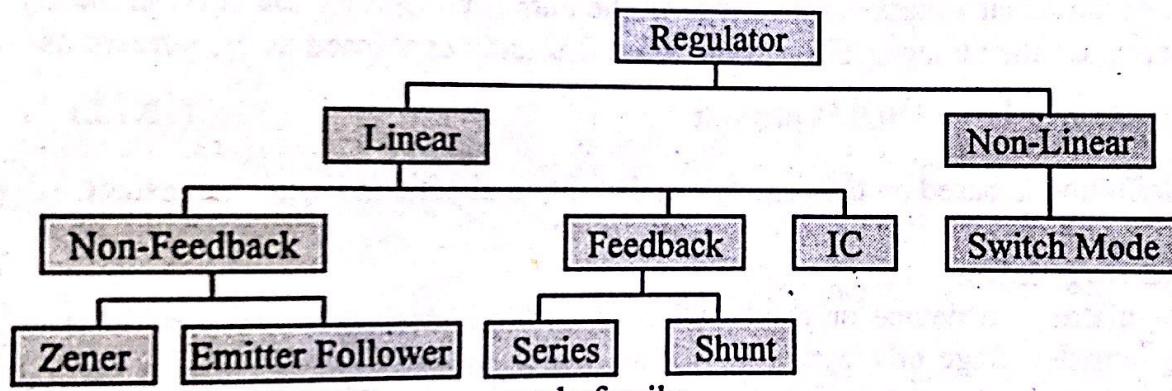


Fig.18.1 DC power supply family

The common terminology used for these dc power supplies is :

Regulated Output :

The output dc voltage of the supply must remain constant within a specified limit, usually 1% or better.

Isolation :

The output terminals of dc supplies must electrically be isolated from the input power source which is generally ac supply i.e. mains. This isolation permits different ground voltage levels in different sections of any electronic equipment or system/subsystems.

Multiple Outputs :

These different sections of any electronic equipment may require different output voltage levels of positive as well as negative polarities. The positive and negative voltage levels must also be isolated from each other, as well as from the ac mains.

Supervisory Circuits :

Different levels of dc voltages may be required in different sections of electronic equipment/systems at different time in a desired sequence which must be controlled with the help of logical supervisory circuit.

Load Regulation :

An ideal dc power supply must be able to supply a constant voltage between its output terminals, no matter what current is drawn from it. However, the output voltage of practical power supply does not remain constant, rather it changes with variation in the load current (I_L). Generally, the output voltage drops with increasing load current. The power-supply specifications include a full load current (I_{FL}) rating, which is the maximum current that can be drawn from it within the tolerance limit of its output voltage. The terminal voltage at full-load current(I_{FL}) is called the full-load voltage (V_{FL}). Similarly, the no-load voltage (V_{NL}) is the terminal voltage when zero current is drawn from the supply. In other words, it is called the open-circuit voltage. One of the measures of power-supply performance is in terms of how well it is able to maintain a constant voltage between its no-load to full-load conditions. It is referred as load regulation and is expressed as ;

$$\% \text{ Load Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} * 100 \quad (18.1.1)$$

Line Regulation :

The line regulation is another measure of the ability of a power supply to maintain a constant output voltage with the corresponding change in the mains voltage. In this case, it is a measure of the sensitiveness in the change of the output voltage for the corresponding changes in input, or line voltage. This specification is usually expressed as the percent as:

$$\% \text{ Line Regulation} = \frac{\Delta V_o / V_o}{\Delta V_i} 100 \% \text{ per volt} \quad (18.1.2)$$

The above definition is based on the assumption that the load current remains constant.

18.2 Voltage Regulator :

A voltage regulator is a device or combination of devices, designed and combined to maintain the output voltage of a power supply as nearly constant as possible. It can be considered as a closed-loop system because it monitors output voltage and generates appropriate feedback that automatically increases or decreases the output supply voltage as per the necessity to compensate for any tendency in change of the output voltage. Thus the purpose of a regulator is to eliminate any variation in output voltage that might otherwise occur because of changes in load, line(input) voltage or changes in temperature. Thus the output voltage of a dc power supply might depend on the following :

- ◆ load current variation,
- ◆ input voltage variation, and
- ◆ temperature changes.

In other words the output voltage is expressed as the function of three variables i.e. V_i , I_L , and T . Mathematically it is expressed as :

$$V_o = f(V_i, I_L, T) \quad (18.2.1)$$

The output dc voltage is partially dependent on the change in the load current I_L , partially dependent on the change in the input voltage V_i , and partially dependent on the temperature change. The total change ΔV_o in the output voltage V_o can be expressed

mathematically as the sum of the partial contributions of all parameters. Thus, ΔV_o can be written as :

$$\Delta V_o = \frac{\partial V_o}{\partial V_i} \Delta V_i + \frac{\partial V_o}{\partial I_o} \Delta I_o + \frac{\partial V_o}{\partial T} \Delta T \quad (18.2.2)$$

or, $\Delta V_o = S_v \Delta V_i + S_{R_o} \Delta I_o + S_T \Delta T$

or, $\Delta V_o = S_v \Delta V_i + R_o \Delta I_o + S_T \Delta T \quad (18.2.3)$

Each of the derivatives in Eqn.(18.2.3) is a measure of regulation or stabilization of the voltage regulator with reference to a particular variable. Thus, the input regulation or stabilization factor (S_v) is expressed as ;

$$S_v = \left. \frac{\partial V_o}{\partial V_i} \right|_{I_o \text{ & } T \text{ constant}} = \text{Constant} \quad (18.2.4)$$

As the load regulation is the ratio of change in the output voltage to the change in the load current, its dimension is of resistance and hence it is termed as output resistance (R_o) or internal resistance of the voltage regulator. It is given by :

$$R_o = - \left. \frac{\partial V_o}{\partial I_o} \right|_{V_i \text{ & } T \text{ constant}} \quad (18.2.5)$$

The negative sign is associated as because with increasing load current output voltage decreases as indicated in Fig 18.2(a).

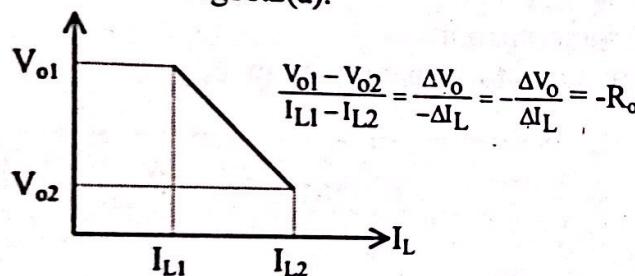


Fig.18.2(a) Output dc Voltage versus Load current Variation

The negative sign in the above expression indicates that R_o must be taken positive when V_o decreases for increasing $I_o = I_L$ or vice versa.

The temperature coefficient (S_T) of the voltage regulator is given by ;

$$S_T = \left. \frac{\partial V_o}{\partial T} \right|_{V_i \text{ & } I_L \text{ constant}} \quad (18.2.6)$$

A dc power supply is normally rated in terms of output dc voltage and the output dc current or the output voltage & current product. In some power supply units, the output voltage can be varied within a certain voltage range with the condition that the units can be loaded up to a certain maximum permissible current limit.

18.3 Classification of Voltage Regulator :

Electronic power supplies (or power supplies used in electronic systems) are more or less charged with the task of controlling or regulating electrical power. The word control is quite inclusive here in this context because whether we rectify, invert, regulate, or change the voltage or current levels, some control technique is involved. Such control of power delivered to a load can be achieved only by absorbing surplus power in any control

- ♦ Its disadvantages are :
- ♦ Poor efficiency due to loss in series resistance and diode itself.
- ♦ Stabilized voltage is equal to breakdown voltage and can not be varied.
- ♦ Breakdown voltage is dependent on temperature.

The Zener diode regulator circuits have been discussed in article-3.11.3. The advantages of Zener Regulators are :

- ♦ Simple,
- ♦ Light in weight,
- ♦ Reliable, and
- ♦ Regulates over a range of current.

In series type regulator, the control element is in series between input and output circuit, so it can work with much lower voltage than the output voltage but the total load current passes through it. Hence, it is suitable for low current and high voltage regulation so high current and low voltage applications.

Only a fraction of the total load current but works at full load voltage. Hence, it is suitable needs. In shunt type regulator, the control element is paralleled to the load, so it passes only a fraction of the total load current but works at full load voltage. Hence, it is suitable for high current and low voltage applications.

- ♦ Feedback types:
- ♦ Series Regulator, and
- ♦ Shunt Regulator.

These are normally employed only for coarse regulation with low cost, low output currents, and where efficiency is not an important consideration.

Zener diode and emitter-follower regulators are the simplest regulator, one can conceive.

- ♦ Emitter-follower regulator.
- ♦ Zener diode regulator, and
- ♦ Non-feedback types:

In linear voltage regulator circuit, the control elements are generally an active device power transistor, which is always operated in the active conduction mode. The active device senses the output of the circuit continuously, and adjusts its conduction to maintain output voltage at a desired value. Here the power dissipation is function of input voltage and load fluctuations. The linear voltage regulator can be of feedback or non-feedback type. The following voltage regulators are important in this category.

18.4 Linear (Dissipative) Voltage Regulator :

Power and accordingly classified as :

- ♦ Linear (Dissipative) Voltage Regulator, and
- ♦ Switch-Mode (Non-dissipative) Voltage Regulator.

device. In order to be energy conscious, the very concept of surplus or throwaway power deserves close scrutiny. The voltage regulator employs different approaches to control the

transistor to conduct more heavily and to produce more load current.

As V_R is constant, any change in V_o must cause a corresponding change in V_{BE} , in order to maintain the equality valid. When V_o decreases, V_{BE} increases, which causes the NPN


(۱۸۵۷)

(C.S.81)

The Zener diode is reverse biased and that reverse current is limited through resistor R . Although V_i is unregulated, it must remain sufficiently large and R must be sufficiently small to keep the Zener in its break down region. Through the unregulated input voltage (V_i) varies V_R remains essentially constant.

Here, the control element is the NPN transistor, often called the PNP transistor because it conducts or passes total load current of the regulator. It is usually a power transistor and mounted on a heat sink in a heavy-duty power supply, that delivers substantial current. The Zener diode provides the reference voltage, and the base to emitter voltage of the transistor is the control voltage.

Fig. 18.5(a) Emitter Follower Voltage Regulator

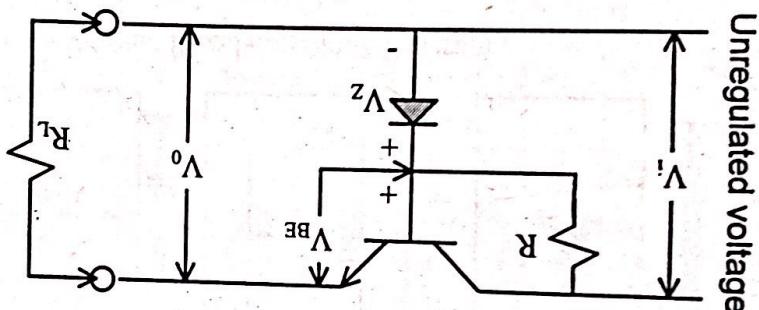


The Zener diode regulator has inherent limitation of current. In other words the current rating of the diode must be higher than the load current. This condition can not be met by one Zener diode. Hence, other type of regulator is required. The Emitter follower circuit shown in the Fig. 18.5(a) is a simplest non-feedback type of transistor voltage regulator. The transistor, which is connected in series with the unregulated input and regulated output voltages and hence called the series type of voltage regulator.

18.6 **Emitter-FET** - Z_out of Diodes connected as Stabilizer Regulator

4

(c) Sensitive type Regulator

Fig. 18.4(a) Stabilizer type B coil

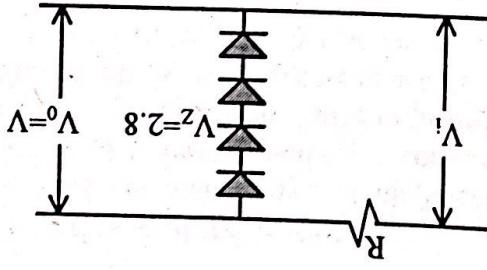


If is well known that the diode current beyond cut-in voltage rises very sharply for fractional change of voltage across its base-emitter voltage. The typical change of 0.2V brings a change in few tens of mA. The single diode regulator in forward bias case is shown in Fig. 18.4(a). A number of diodes as shown in Fig. 18.4(a) may be connected in series to increase the regulated voltage.

S-81

Regulated Power Supply: Discrete


The voltage regulation is taken up here for load current (I_L) variation. The regulation against the load current variation is performed by comparing a sample of the output voltage w.r.t. a fixed reference voltage. The difference of the two is amplified and is used to control the series control element T_1 .

Fig. 18.6(b) Block Diagram of Series Regulator

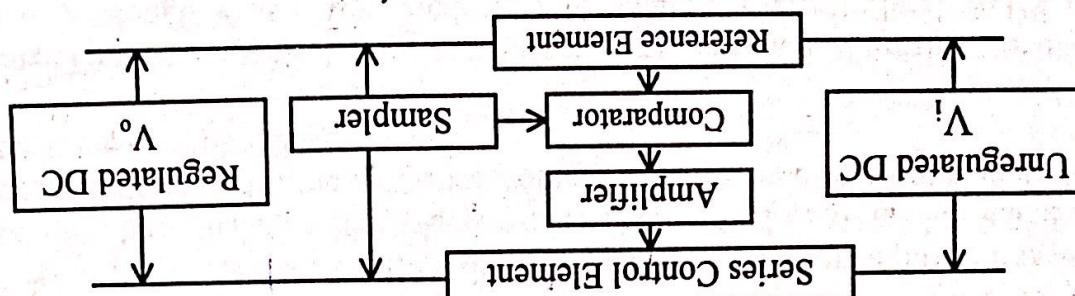

As we have already discussed rectifiers and filters in Chapter-5, we start our discussions on regulators. A series regulator is divided into five blocks as arranged in Fig. 18.6(b).

Fig. 18.6(a) Voltage Regulator Block Diagram

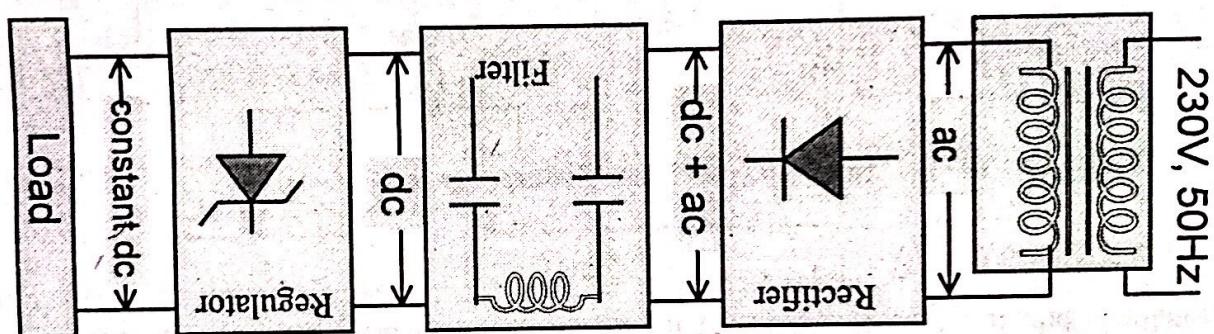

The above blocks are connected in series as shown in Fig. 18.6(a).

- ◆ Transformer,
 - ◆ Rectifier,
 - ◆ Filter,
 - ◆ Regulator, and
 - ◆ Load.
- A stabilized voltage supply essentially consists of following blocks :
- A type regulator is taken up here in details.
- The most common used of all linear regulators is the series regulator. The shunt regulator is generally used for a constant load whereas the series regulator is normally used for a variable load. Since most of the applications require variable load, the series regulator is taken up here in details.
- The above blocks are connected in series as shown in Fig. 18.6(a).

18.6 Series Voltage Regulator :

$$V_o = V_{CE} + V_o \quad (18.5.3)$$

Notice that the transistor is used essentially as an emitter follower. The load is connected to the emitter and the base follows the emitter. The load is connected to a constant voltage V_R . Hence, it is known as emitter follower regulator. For successful regulator operation, the pass transistor must remain in its active region, V_i must not drop to a level so small that the Zener is no longer in its breakdown region and the Zener voltage V_R should be highly independent of both current and temperature.

The complete equivalent circuit of the Zener diode in the Zener region includes a small dynamic resistance r_z in series with a battery voltage equal to the Zener breakdown potential V_z , as indicated in Fig. 18.8(b). However, for all practical applications it is assumed that the external resistances are much larger than the dynamic resistance of the Zener diode.

18.8 Reference Element:

Generally Zener diodes are used as constant voltage reference element as because its characteristics that are taken into considerations for the selection of the Zener diodes effect of temperature, reverse current, and diode resistance on the breakdown voltage are breakdown voltage remains relatively constant over a wide range of reverse current. The generally Zener diodes are used as constant voltage reference element as because its

18.7 Sample:

The resistances R_1 , R_2 , and $R_{p1} + R_{p2} = R_p$ should be made of the same material and are kept at the same temperature.

$$V_s = \frac{R_1 + R_2 + R_{p1} + R_{p2}}{R_2 + R_{p2}} V_o = \frac{R_1 + R_2 + R_p}{R_2 + R_p} V_o \quad (18.7.1)$$

The sample voltage (V_s) derived from the sampler is :

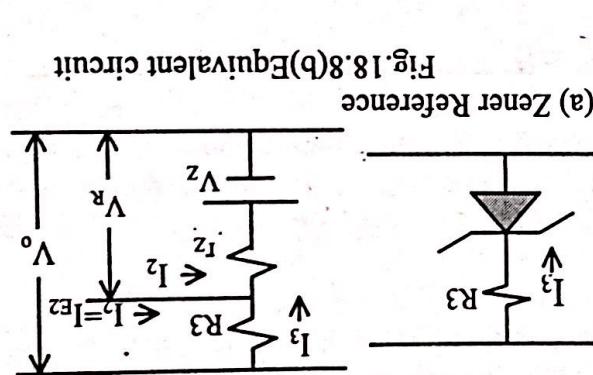


Fig. 18.7(a) Sampler Circuit


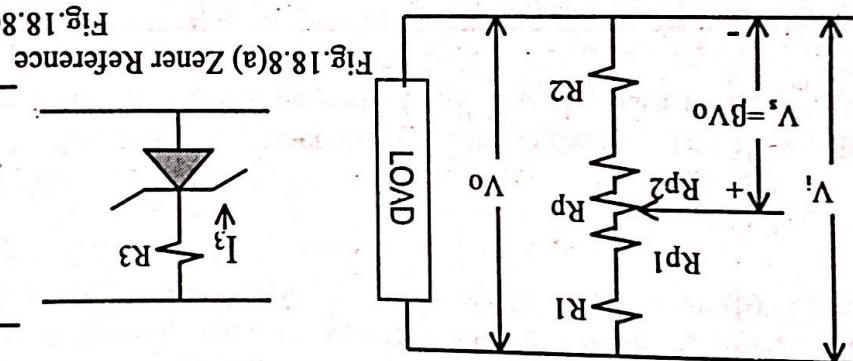


Fig. 18.7(b) Equivalent circuit

Usually it is a simple resistive voltage divider across the regulated output V_o . as indicated in Fig. 18.7(a).

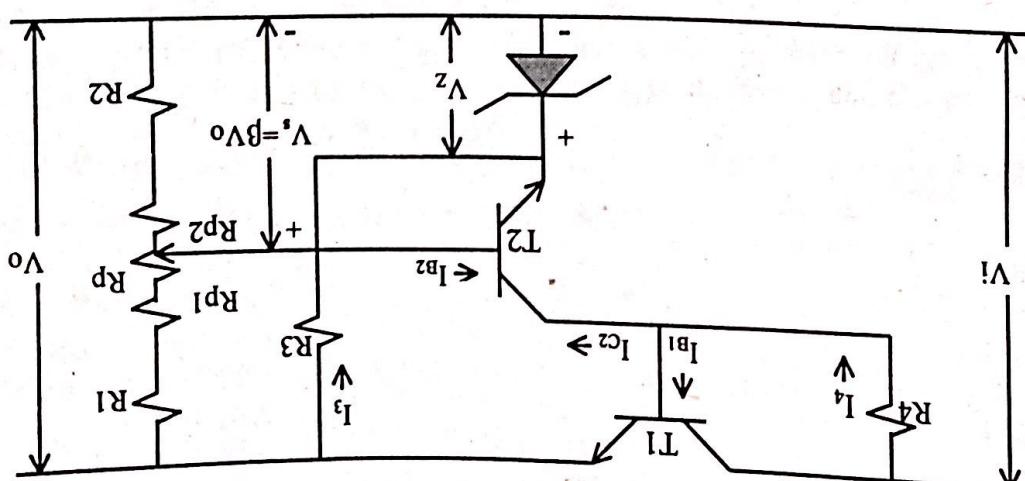18.7 Sampler : Fig. 18.6(c) Series Regulator



A simple circuit of a series regulator is shown in Fig. 18.6(c)

Regulated Power Supply: Discrete

Fig. 18.9(a) performs the comparison element. In most of the cases the single transistor T2 is sufficient to drive the amplifier raises the level of the difference signal to such a value that is sufficient to

18.10 Amplifier :

Since I_C is proportional to I_B , the decrease in I_B will force I_C also to decrease proportionately.

Fig. 18.9 Comparator

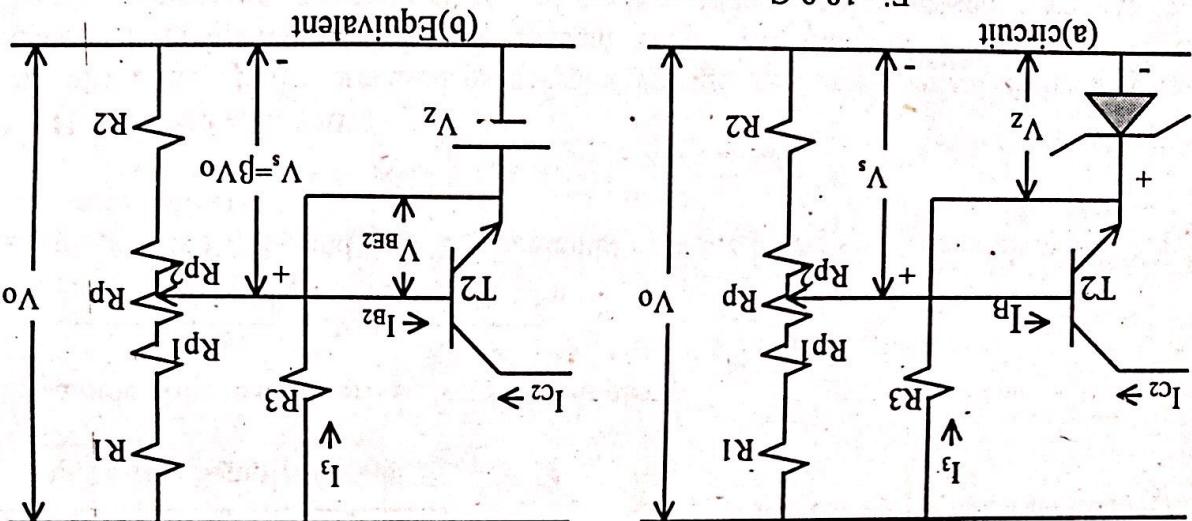


Fig. 18.9(c).

Suppose output voltage V_0 decreases with increase in the load current I_C . The V_{BE2} will also decrease accordingly and hence the base current will also decrease as shown in

$$\text{Since } I_B = f(V_{BE2}) = f(V_s - V_z)$$

$$V_{BE2} + V_z = V_s \quad (18.9.1)$$

Fig. 18.9(b)

The common-emitter or emitter-coupled differential amplifier is normally used as a comparator. The voltage V_s and produces output proportional to the difference voltage of the two signals. A CE amplifier compares the sample of the output voltage w.r.t. the constant reference voltage V_z , and produces output proportional to the difference voltage can be made very small w.r.t. to the change in the reference voltage by selecting the Zener diode having very low dynamic resistance.

It is clear from Eqn. (18.8.6) that the change in the reference voltage can be made very small w.r.t. to the change in the output regulated voltage by selecting the Zener diode

$$(R_3 + r_z) \frac{\Delta V_R}{\Delta V_o} = \Delta V_o, \text{ or, } \frac{\Delta V_R}{\Delta V_o} = \frac{R_3 + r_z}{r_z} \quad (18.8.6)$$

Hence, combining Eqs. (18.8.3) and (18.8.4) yields:

$$A_S \Delta V_z = 0, r_z A_I^3 = \Delta V_R$$

$$(R_3 + r_z) A_I^3 = \Delta V_o$$

$$I_3 R_3 + r_z I_3 + V_z = V_o$$

As $I_3 \gg I_2$ Eqn. (18.8.1) reduces to :


$$I_3 R_3 + r_z (I_3 + I_2) + V_z = V_o$$

only. From Fig. 18.8(b),

Zener diode and hence $r_z = 0$. Thus the Zener diode is equated by a constant voltage V_z .

Following characteristics are essential for the selection of the series control element:
 As V_i is constant, $V_i = V_{CEI} + V_o$. With decreasing value of V_o , V_{CEI} has to increase.
 $V_{CE(min)} \geq V_i(max) - V_o(max)$
 $I_{C(max)} \geq I_{o(max)}$
 $P_{C(max)} \geq V_o(max) I_{C(max)}$

Fig. 18.11(a) Series element working

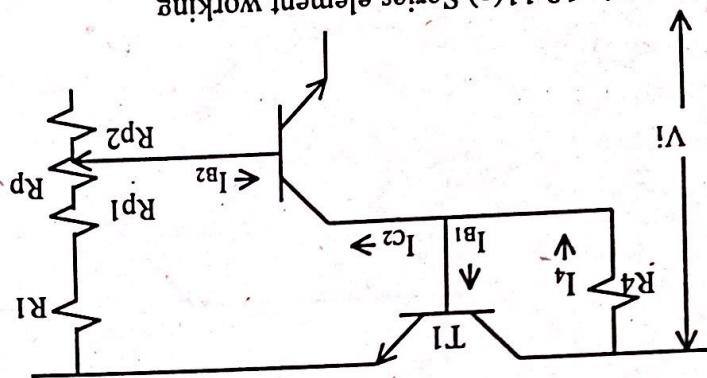

by a flow chart in Fig. 18.11(c).

compensated by the equal amount of voltage released by V_{CEI} . This process is explained gaimed by the output voltage V_o . Hence, any attempt to decrease in the output voltage is V_{CEI} to V^*_{CEI} . Thus, the part of the voltage released by V_{CEI} ($\Delta V_{CE} = V_{CEI} - V_{CE}$) is from Fig. 18.11(b) that the quiescent point shifts from Q_1 to Q_2 resulting in decrease of thus, increases proportionately from I_{C1} to I_{C2} as shown in Fig. 18.11(b). It is evident assumed to be constant, decreasing I_{C2} forces I_{B1} to increase. The collector current of T_1 , $= I_{B1} = I_c - I_{B2} = I_4 - B_1 I_{B2}$. As I_4 remains constant because input voltage for the time being indicated in Fig. 18.9(c) and I_{C2} will also proportionally decrease. The base current of T_1 base current of $T_2 = I_{B2} = f(V_{BE2}) = f(V_s - V_z)$, it decreases consequently from I_{B2} to I_{B2}' as the forward bias between base-emitter of $T_2 = V_{BE2} = V_s - V_z$, also decreases. Since the I_{C1} . If the output (load) voltage V_o decreases due to increase in the load current I_L , then T_2 are I_{B2} and I_{C2} . Similarly, let us assume that the base and collector currents of transistor T_1 are I_{B1} and the process of adjustment; let us assume that the base and collector currents of transistor T_2 are I_{B2} and I_{C2} . In order to understand control element is shown in Fig. 18.6(c) is redrawn as Fig. 18.11(a). In order to understand series control element to maintain the output voltage constant. The circuit of a series appropriate adjustment to interpret the amplified difference signal and makes

18.11 Series Control Element:

Fig. 18.9(c) Variation of I_{B2} with Forward bias V_{BE2} . Fig. 18.11(b) I_{C2} with V_{CE2}


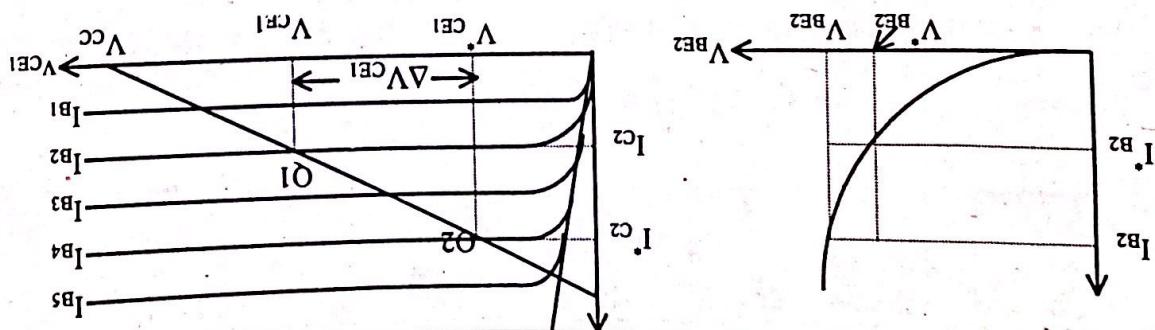


Fig. 18.12(b) Series Voltage Regulator with Pre-regulator

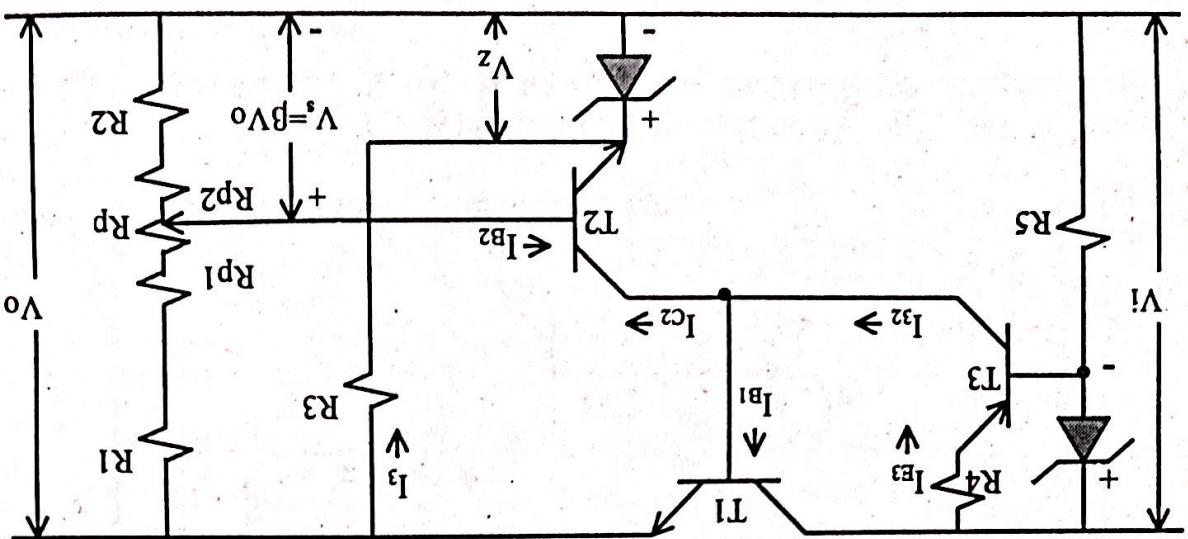

(18.12.3)

(18.12.2)

(18.12.1)

As V_z is connected across R_3 and V_{BE3} , the collector current of T_3 is independent of the change in V_{BE3} caused by even the input voltage variation. In other words, transistor T_3 is working as a constant current source.

$$or, R_4 = \frac{V_z - V_{BE3}}{I_{E3}}$$

$$V_z = V_{BE3} + R_4 I_E3$$


$$I_{C3} = I_{E3} - I_{B3} = I_{B1} + I_{C2}$$

WBE based on a constant cutting

Causes of VBF₃ by every

connected across R₃


Fig. 18.12(a) Preregulator

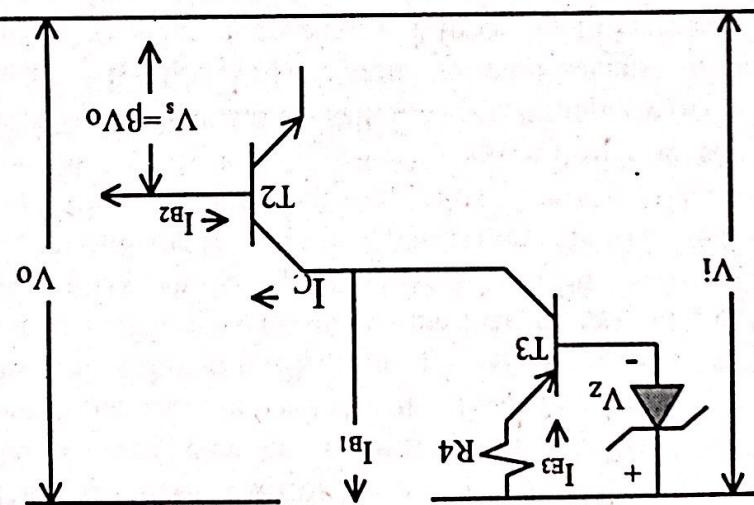

The preregulator is included as one of the blocks in the voltage regulator to take care of the input voltage variations. The preregulator is to provide the constants current to the junction of the base of TI and the collector of the T3. A simple preregulator circuit is

shown in Fig. 18.12(a)

Fig. 18.11(b) Regulation Process of Output Voltage

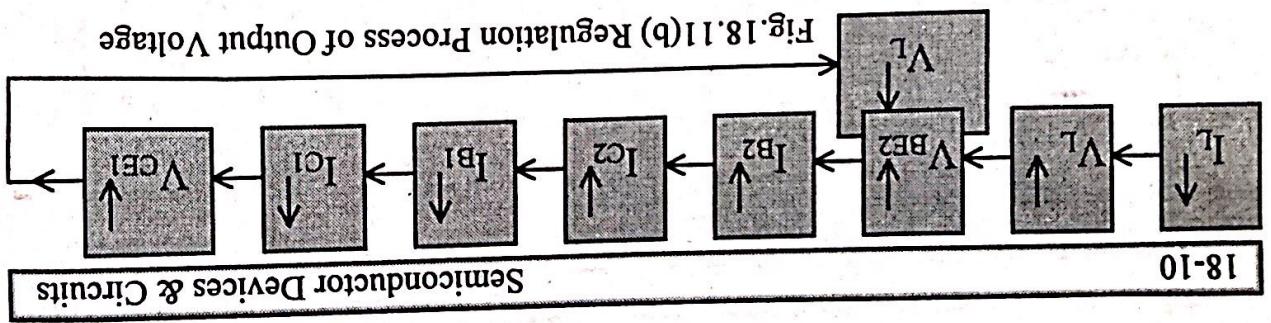


It is convenient to think that the control element in shunt regulator works as a variable resistor. When the load voltage decreases, the resistance of the control element increases. Conversely, when the load voltage increases, the resistance of the control element decreases, and more current is shunted away from load. From another view point, the source resistance on the unregulated side forms a voltage divider with the parallel combination of the control element and R_L . Thus, when the resistance of the control element increases, and hence I_L increases. As I_C decreases, the drop across $V_{BE} = V_L - V_B$, as $I_B \propto V_{BE}$, $I_C \propto I_B$ decreases and hence V_L increases. Other way $V_L = V_Z + V_{BE}$, as V_Z constant, $V_{BE} \propto V_L$, as $I_B \propto V_{BE}$, $I_C = I_B$, $I_C \propto I_B$ decreases to the original value and hence remains constant.

Applying KVL results in $V_{BE} = V_L - V_Z$, As V_Z constant divider action the load voltage increases.

element increases, the resistance of the parallel combination increases and by voltage divider action the load voltage increases. Thus, when the resistance of the control element increases, the source resistance on the unregulated side forms a voltage divider with the parallel combination of the control element and R_L . Conversely, when the load voltage increases, the resistance of the control element decreases, and more current is shunted away from load. From another view point, the source resistance on the unregulated side forms a voltage divider with the parallel combination of the control element and R_L . Thus, when the resistance of the control element increases, the resistance of the control element decreases, and hence I_L increases. As I_C decreases, the drop across $V_{BE} = V_L - V_B$, as $I_B \propto V_{BE}$, $I_C \propto I_B$ decreases and hence V_L increases. Other way $V_L = V_Z + V_{BE}$, as V_Z constant, $V_{BE} \propto V_L$, as $I_B \propto V_{BE}$, $I_C = I_B$, $I_C \propto I_B$ decreases to the original value and hence remains constant.

regulator circuit is shown in Fig. 18.13(b). This type of regulator is usually recommended for relatively constant load. Each of the blocks in the shunt regulator performs the same function as its counterpart in the series regulator. The control element that is in parallel to the load maintains a constant load voltage by shunting more or less current from the load. The simplest shunt voltage regulator circuit is shown in Fig. 18.13(a). In sharp contrast to the series regulator, the control device in this case is in the shunt path. Although the shunt regulator is not as efficient as the series regulator, it has greater economy and simplicity.

Fig. 18.13(a) Block Diagram of Shunt Regulator

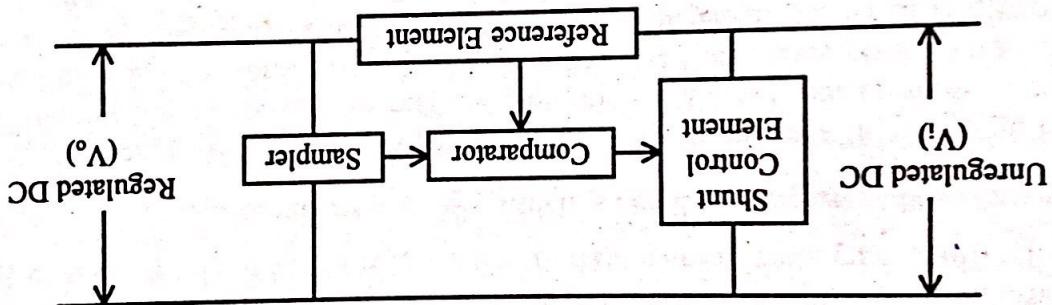

- ◆ advantages of :
- ◆ greater economy and
- ◆ simplicity.

Fig. 18.13(a). In sharp contrast to the series regulator, the control device in this case is in the shunt path. Although the shunt regulator is not as efficient as the series regulator, it has the sharp contrast to the series regulator as described by blocks in Fig. 18.13(a).

18.13 Shunt Regulator :

- ◆ Heat sink for series transistor to dissipate heat due large power loss.
- ◆ Large size due to large transformer,
- ◆ Less efficient,
- ◆ The prominent disadvantages of linear type dc voltage regulators are :

A simple circuit of series voltage regulator is shown in Fig. 18.12(b).

$$(18.12.4)$$

$$R_s = \frac{V_i(\text{min}) - V_z - I_{zT}^2}{I_z + I_{B3}}$$

Regulated Power Supply: Discrete

18-11

A series fuse is sometimes used in an attempt to protect the series-pass transistor from excessive power dissipation. Hence, it is essential that the protective means introduced to it become effective almost instantaneously.

times the transistor ratings. In such a case, the power dissipated in T_1 can become several times the input voltage (V_i) appears across transistor T_1 and the resulting current out of it $= V_i/R_0$ passes through it. In such a case, the power dissipated in T_1 can become several shorted, full input voltage (V_i) protected. For example, when the output terminals are transistor (T_1), if it is not properly protected, even a permanent damage to the series-pass regulator circuit, overloading can result in even a wide range. In the series regulator circuits wherein the load current can vary over a wide range. In the series circuit, this is particularly important in the emitter follower regulator and the series regulator, it is necessary to introduce protective measures for the over load current in the circuit. Therefore, it is well known that the voltage regulator circuits offer very low output resistance.


Almost all-general purpose dc power supplies have short-circuited or overload protection circuitry. One form of protection circuitry is called current limiting which by specially designed circuitry limits the current that can be drawn from the supply to a certain specific maximum, even if the output terminals are short-circuited. In other words, the protection circuit provides a shunting path to it.

18.14. Current Limiting Techniques:

Resistor R_4 under short-circuited condition of output. Since the load current must flow through R_4 , the power dissipation in the resistor may be quite high, especially under short circuit conditions. This condition forces us to include some circuit arrangements that can take care of it automatically. These types of circuit arrangements are called current limiting circuits.

Advantage of short circuit protection circuit is that it has inherent current limiting capability. It is clear that the load current cannot exceed $\frac{V_o}{R_4}$ which is equal to the current flow through R_4 , under short-circuited condition of output. Since the load current must flow through R_4 , the power dissipation in the resistor may be quite high, especially under short circuit conditions. This condition forces us to include some circuit arrangements that can take care of it automatically. These types of circuit arrangements are called current limiting circuits.

Fig. 18.13(c) Shunt Voltage Regulator Circuit Diagram

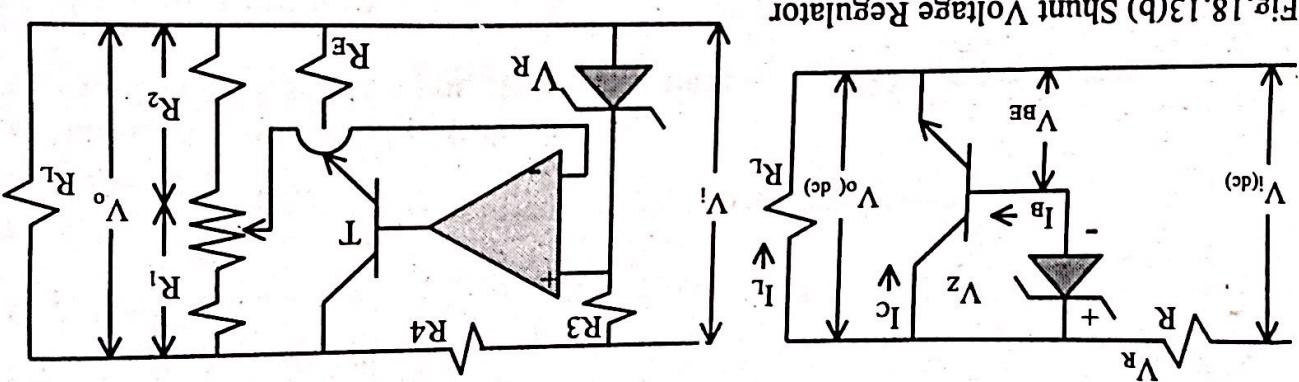

The 723 is a general-purpose integrated circuit voltage regulator. It is an example of a popular and very versatile adjustable (variable) regulator. It can be connected to produce positive or negative outputs from 2V to 37V, with an external pass transistor it can handle load currents up to 10A, and can be used as switching regulator.

Table-18.18(a) shows electrical characteristics of the 723. Note the terminal labeled V_{REF} at the output of the voltage reference amplifier. This is an internal terminal generated voltage of approximately 7V that is available with an external pin.

Table-18.18(a) Electrical characteristic of the 723

Parameter	Min	Typical	Max	Unit
Input Voltage	9.5V	2.0V	3.0V	Input Output Voltage Difference
Output Voltage	40V	37V	38V	Short Circuit Current Limit ($R_s = 10\Omega$, $V_{out} = 0$)
Long Term Stability	4.0mA	2.3mA	6.5mA	Standby Current Drain ($I_L = 0$, $V_m = 30V$)
Ripple Rejection (50Hz to 10kHz, $C_{ref} = 0pF$)	74db	86db	—	Average Temp. (-55°C ST $\Delta S + 125^\circ C$)
Output Noise Voltage (BW=100Hz to 10kHz, $C_{ref} = 0pF$)	20μV _{rms}	2.5μV _{rms}	—	Coeff. of Output voltage (0°C ST $\Delta S + 70^\circ C$)
Current from V_Z	2.5mA	15mA	800mW	Current from V_{REF}
Internal Power Dissipation	7.5V	7.15V	6.8V	Reference Voltage
Line Regulation ($V_i = 12V$ to 15V, 0°C ST $\Delta S + 70^\circ C$)	0.1%V _o	0.01%V _o	0.01%V _o	($V_i = 12$ to 40V, 0°C ST $\Delta S + 70^\circ C$)
Load Regulation ($I_L = 1mA$ to 50mA)	0.15%V _o	0.03%V _o	—	(-55°C ST $\Delta S + 125^\circ C$)
Voltage proportional to V_o . Depending on whether the reference is connected to a error amplifier is a comparator that compares the externally connected reference to an extremely divided-down portion of it, to one of the line input of the error amplifier. The order to set a desired regulated output voltage, the user connects this 7V output, or an	0.2%V _o	0.1%V _o	0.1%V _o	0.1%V _o