

PART - BOSCILLATORSTopics to be covered:

- ① oscillator definition.
- ② classification of oscillators.
- ③ Conditions for obtaining oscillations (or) Barkhausen Criterion.
- ④ Conditions for obtaining oscillations (or) Barkhausen Criterion.
- ⑤ List of oscillators to be discussed and Analysis.
- ⑥ RC oscillator circuits using FET and BJT and Analysis.
- ⑦ Derivation for frequency of oscillations.
- ⑧ Condition on minimum gain required for active devices (h_{fe}, μ)
- ⑨ Design Considerations and Variable frequency of oscillations.
- ⑩ Generalized LC oscillators
- ⑪ Colpitts oscillator
- ⑫ Hartley oscillator.
- ⑬ Wien-Bridge oscillator
- ⑭ Crystal oscillator
- ⑮ Stability of oscillations
 - ⑯ Frequency stability
 - ⑰ Amplitude stability
- ⑲ Problems.

① OSCILLATOR:

An oscillator is an electronic circuit which (produces) generates a periodic ac signal at its output ~~with~~ without any external input signal.

~~Note:~~ ① oscillator converts DC power into AC power.

② oscillator is a switch which ~~selects~~ generates a periodic signal with a single frequency desired.

② CLASSIFICATION OF OSCILLATORS:

The oscillators are classified based on various parameters as given below:

② Based on the shape of the waveform:

- ① Sinusoidal oscillators → O/P is sine (or) cosine wave [uses RC (or) LC or crystal circuit]
- ② Non-sinusoidal osc. → O/P is square, triangle, sawtooth etc. [uses VJT (or) multivibrators]

③ Based on Fundamental Mechanism involved:

① Negative Resistance osc's

These circuits uses 2/3-terminal devices like Tunnel diodes or VJT, which exhibit negative resistance region.

② Feedback oscillators (To be discussed here)


These circuits uses positive feedback for generating sinusoidal oscillations.

③ Based on Frequency generated:

- ① Audio Frequency Oscillators (AFO) : up to 20 kHz
- ② Radio Frequency Oscillators (RFO) : 20 kHz to 30 MHz
- ③ Very High Frequency osc. (VHF) : 30 MHz to 300 MHz
- ④ Ultra High Frequency osc. (UHF) : 300 MHz to 3 GHz
- ⑤ Micro Wave Frequency osc. (MWFO) : above 3 GHz

③ List of oscillators to be discussed and Analyzed:

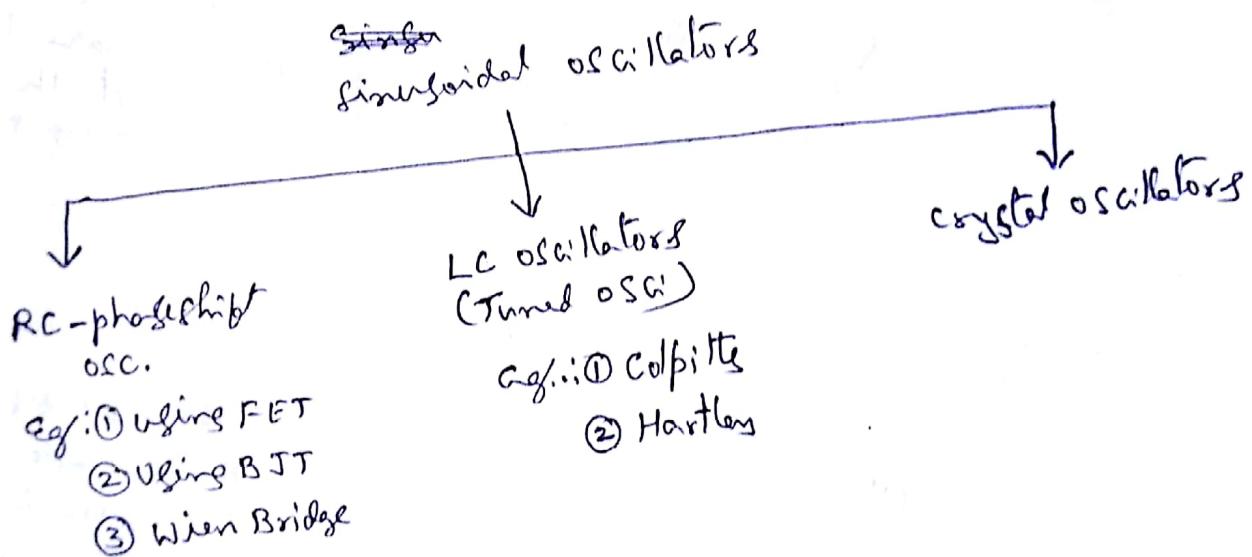
Sinusoidal oscillators are further classified based on the components used in β -network, which provides positive feedback to the basic amplifier.



④ BARKHUSEN CRITERION/CONDITIONS

(or) Conditions for obtaining oscillations:

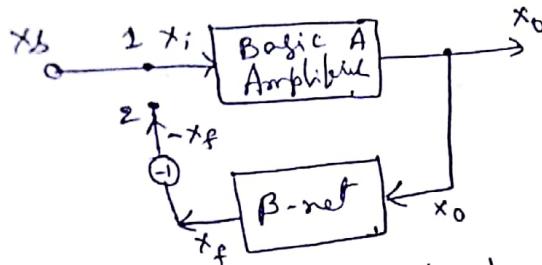The block diagram of a feedback amplifier can be drawn as shown below. To complete the feedback loop



points 1 and 2 are to be joined together, then

$$x_i = x_s - x_f \quad \text{Basic amplifier amplifies } x_i \text{ and produces } x_o.$$

Suppose if $x_i = -x_f$ then a Basic amplifier produces x_o , because it cannot distinguish how x_i is generated whether due to x_s (or) due to FB signal. So, if we set $-x_f = x_i$ then it is possible to obtain x_o without x_s , the external source.

$$\therefore -x_f = x_i$$

$$-\beta x_o = x_i$$

$$-ABx_i = x_i$$

$$\boxed{\therefore -AB = 1}$$

Therefore if the loop gain ($-AB$) is equal to unity then output x_o can be obtained without any external source signal. This is the condition to be satisfied by any feedback circuit for obtaining oscillations.

Barkhausen Conditions:

To obtain oscillations the condition is

$$-AB = 1$$

the gain of the amplifier A is a complex quantity (except in Mid Band region), so the LHS expression is a complex quantity. Hence the above expression can be expressed as (a) Magnitude part and (b) phase part.

Condition : 1

$$|-AB| = 1$$

i.e. Magnitude of loop gain should be unity.

Condition : 2

$$\angle -AB = 0 \text{ or } 2n\pi \text{ for } n=1, 2, 3, \dots$$

i.e. the loop phase shift should be 0° or 360° or integer multiple of 360° .

The above 2 conditions are called as

Barkhausen conditions.

Note: ① If any circuit satisfies above two conditions it produces sinusoidal oscillations without any external signal.

② For any circuit to produce oscillations it should satisfy the \angle Barkhausen conditions.

③ We know the β -net in -ve FB amplifier does not produce any additional phase-shift.

④ To obtain oscillations the loop phase-shift should be 360° , The basic amplifier produces 180° phase shift. Therefore β -network should provide another 180° phase shift.

(5) To produce additional phase-shift of 180° , B-network should consist of reactive elements like capacitors and inductors along with resistors.

(6) If B-network consists of RC circuits then the oscillator is called as RC oscillator.

(7) If B-network consists of LC circuits then it is called as LC oscillator or Tuned oscillator.

(8) In Wien-Bridge oscillator → B-network consists of Wien-Bridge ckt with RC elements. Oscillations will be obtained when the bridge is balanced. Wien-Bridge oscillator is the one in which both negative and positive feedback are used.

(9) In crystal oscillators, B-network consists of a crystal which exhibits piezo-electric effect.

(10) Frequency stability of RC oscillators is poor and for LC oscillators it is good. Frequency stability of crystal oscillators is very high (1 part in 10^9)

RC oscillators are used for audio range.

LC oscillators are used for above audio range.

Crystal oscillators can be used for the frequency range of 0.5 to 30 MHz.

Applications (11) B-net consists of passive element

in oscillator ckt B-net consists of passive element (R, L, C) hence power dissipation occurs, so the output amplitude gradually decays and the oscillations become damped oscillations. To overcome this problem the magnitude of the loop gain is set 5% larger than unity in all practical circuits.

$$\therefore | -AB | = 1.05 \text{ for practical ckt.}$$

The maximum amplitude of the output is limited by the non-linearity of the active device.


(P.T.O.)

Range
10 Hz to
1 MHz

Practical
consideration


⑤ ② RC phase-shift oscillator using FET:

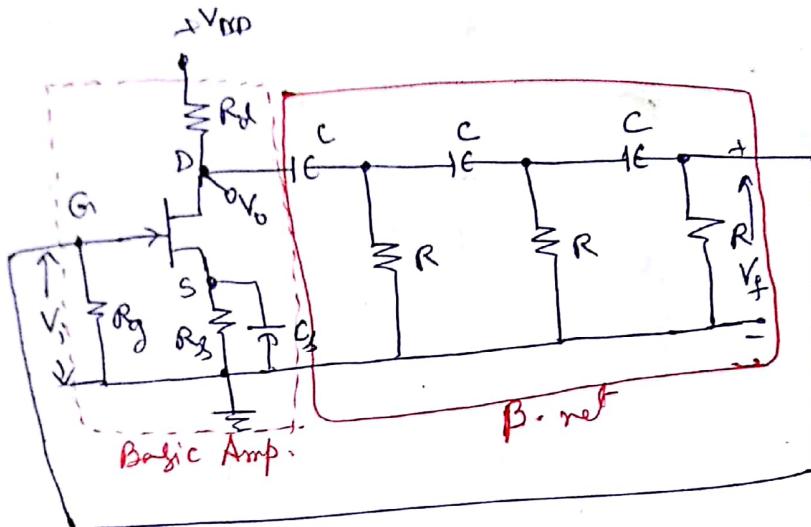② The RC phase-shift oscillator ckt is as shown below.
using FET



Explanation.

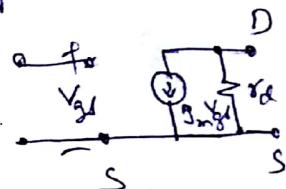① Common source amplifier is used as basic amplifier. During analysis ground V_{DD} , short ckt C_S , so R_S is bypassed and ignore R_S in the biasing ckt. Replace the FET with its low frequency model.



② β -network consists of 3 identical RC stages. Each RC circuit is designed to produce 60° phase shift such that the total phase-shift is 180° .

③ CS Configuration provides 180° phase-shift and if β -network provides another 180° then total loop phase-shift would be equal to 360° .

④ Basic Amplifier input impedance is very high so, it does not load the β -network. Hence the Basic amplifier and β -network can be analyzed separately.

⑤ Gain of the β -network is given by

$$\beta = \frac{V_f}{V_o}$$

(P.T.O.)

⑥ the gain of the Basic amplifier A_V is given by

$$A_V = \frac{V_o}{V_i} = -g_m R_d' \quad (\text{known})$$


$$= - \frac{g_m r_d R_d}{r_d + R_d}$$

$$A_V = - \frac{\mu R_d}{r_d + R_d}$$

⑦ Derivation for frequency of oscillations:

The β -network should provide 180° phase shift, the gain of the β -network is given by

$$\beta = \frac{V_f}{V_o}$$

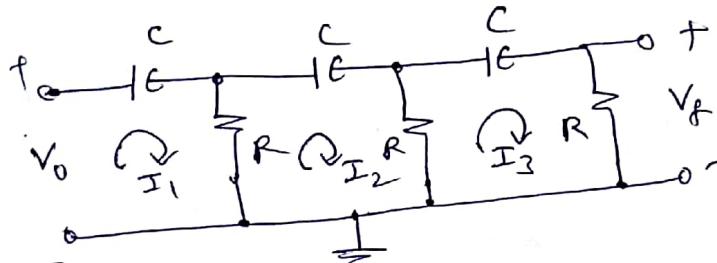

write the 3 loop equations

$$V_o - (-jx_c)I_1 - R(I_1 - I_2) = 0$$

$$\therefore -I_1(R - jx_c) + I_2R = -V_o$$

$$\therefore I_1(R - jx_c) - I_2R = V_o \quad \text{--- I}$$

$$I_1(1-j\omega) - I_2 = \frac{V_o}{R} \quad \text{--- II}$$

$$-R(I_2 - I_1) - (-jx_c)I_2 - R(I_2 - I_3) = 0$$

$$-R(I_2 - I_1) - (-jx_c)I_2 - R(I_2 - I_3) = 0 \quad \text{--- III}$$

divide with R

divide with R

$$I_1R - I_2(2R - jx_c) + I_3R = 0$$

$$I_1 - I_2(2 - j\omega) + I_3 = 0$$

$$-R(I_3 - I_2) - (-jx_c)I_3 - RI_3 = 0$$

$$\therefore I_2R - I_3(2R - jx_c) = 0$$

$$\therefore I_2 = I_3(2 - j\omega) \quad \text{--- III}$$

$$\text{where } \omega = \frac{x_c}{R} = \frac{1}{LCR}$$

(P.T.O.)

Substitute III in II

$$\begin{aligned}\therefore I_1 &= I_3 (2 - j\omega)^2 - I_3 \\ &= I_3 [4 - \omega^2 - j4\omega - 1] \\ I_1 &= I_3 [3 - \omega^2 - j4\omega] \quad \text{--- } \underline{\text{IV}}\end{aligned}$$

Substitute III & IV in I

$$\begin{aligned}I_3(1 - j\omega)(3 - \omega^2 - j4\omega) - I_3(2 - j\omega) &= \frac{V_0}{R} \\ \therefore I_3 R [3 - \omega^2 - j4\omega - j3\omega + j\omega^3 - 4\omega^2 - 2 + j\omega] &= V_0 \\ \therefore V_f [1 - 5\omega^2 + j(\omega^3 - 6\omega)] &= V_0 \\ \therefore \beta = \frac{V_f}{V_0} &= \frac{1}{1 - 5\omega^2 + j(\omega^3 - 6\omega)}\end{aligned}$$

The condition to obtain oscillations is $\angle \beta = 180^\circ$

$$\therefore \angle \beta = -\tan^{-1} \left(\frac{\omega^3 - 6\omega}{1 - 5\omega^2} \right) = 180^\circ$$

$$\therefore \omega^3 - 6\omega = 0 \Rightarrow \boxed{\omega^2 = 6}$$

$$\therefore \boxed{\omega = \sqrt{6}}$$

$$\text{but } \omega = \frac{1}{\sqrt{LC}} = \frac{1}{2\pi f RC}$$

$$\therefore \frac{1}{2\pi f RC} = \sqrt{6}$$

$$\therefore f = \frac{1}{2\pi RC\sqrt{6}}$$

At this frequency only the β -network will provide 180° phase shift. To obtain sustained oscillations the magnitude condition should also be satisfied at this frequency.

(P.T.O.) ... (6)

(29) (6)

(c) Condition on Minimum gain Required:
 Therefore at this frequency the magnitude of β -network is given by

$$|\beta| = \left| \frac{1}{1 - 5\omega^2} \right| = \frac{1}{29}$$

So, to obtain sustained oscillations

$$|AB| = 1$$

$$\Rightarrow |A| = \frac{1}{|\beta|}$$

$$\therefore |A| = 29$$

so a FET as amplifier with amplification factor (M) less than 29 cannot produce sustained oscillations.

$$\therefore |A| \approx M > 29$$


$$|A| = g_m R_d \approx \mu \text{ if } R_d \rightarrow \infty$$

- (d) Design Considerations:**
- ① Select a FET with $M = g_m R_d > 29$ and operate in CS mode
 - ② During design the frequency of oscillations f will be given then to complete the design proceed as follows:
 - ③ Select $C \leq 1 \mu F$ (depending on availability in the market)
 - ④ Calculate R using the formula
- $$f = \frac{1}{2\pi RC\sqrt{6}}$$
- Exact value of the resistance above may not be available in the market, then select a ~~pot~~ potentiometer with appropriate value and adjust the as per the requirement.

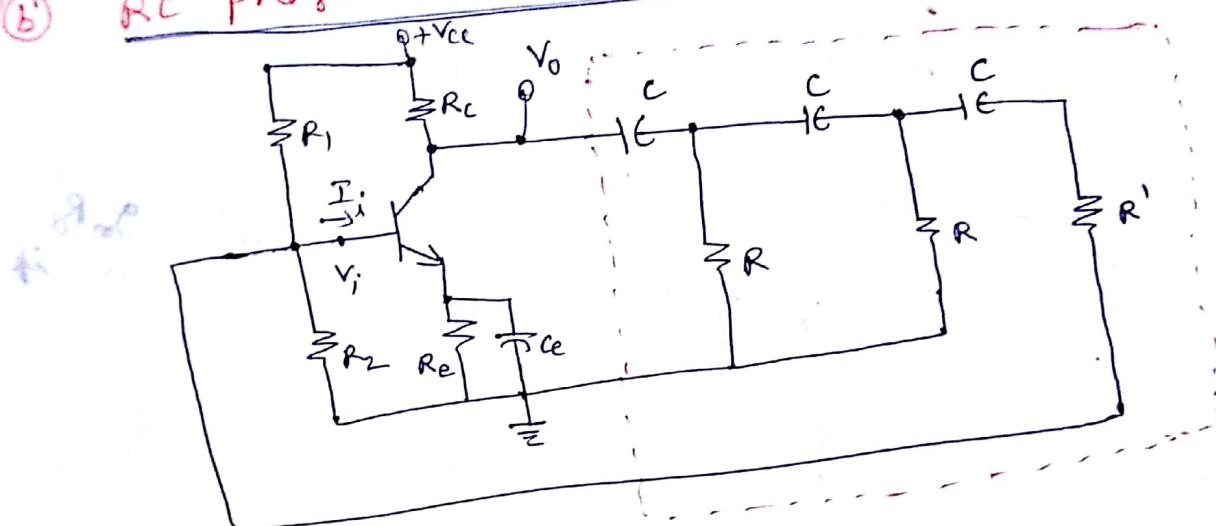e) Frequency Variability:

Once the design is completed for a given frequency f_1 , to design an oscillator with f_2 frequency, use 3-ganged capacitors, [in which the 3 capacitors are connected to a single shaft] and varying all the capacitor values simultaneously, till the desired frequency is obtained.


5@b) RC phase-shift oscillator using BJT:



Explanation:

The RC phase-shift oscillator using BJT is as shown above.

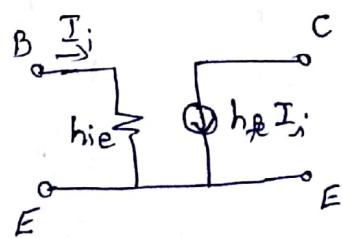- ① The RC phase-shift oscillator using BJT is used as basic amplifier.
- ② Common Emitter amplifier is used as basic amplifier. During analysis V_{cc} is grounded, C_e is to be short circuited then R_e is bypassed. The effect of biasing resistances R_1 & R_2 is neglected. BJT is to be replaced with its approximate h-parameter model.




- ③ The β -out work consists of 3 identical RC stages. Each RC circuit is designed to produce 60° phase-shift such that total phase-shift is 180° .

- ④ CIE Configuration provides 180° phase-shift and β -network provides another 180° phase shift and the total loop phase-shift would be equal to 180° .
- ⑤ In this circuit the basic amplifier input impedance is low, so the loading effect of the β -network should be considered and BJT is a current controlled device. Hence it is convenient to calculate the loop gain (I_f/I_i) by considering basic amplifier and β -network combinedly as a single circuit.
- ⑥ The loop gain ($-A_B$) is obtained as (I_f/I_i)


$$\therefore -A_B = \frac{I_f}{I_i}$$

⑦ Derivation for frequency of oscillations:

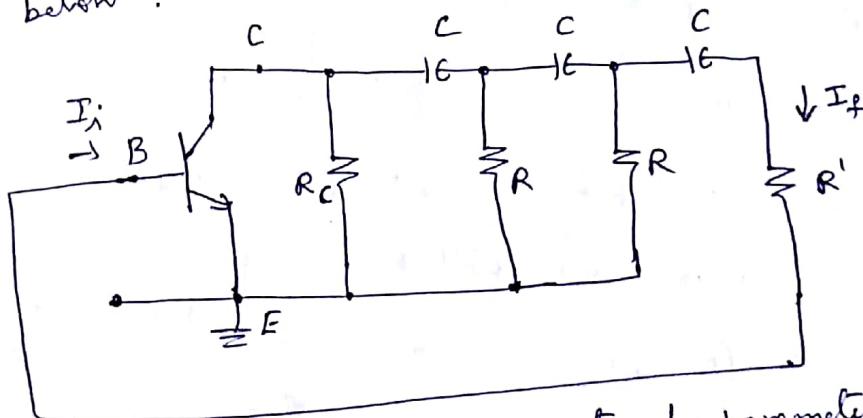The basic amplifier with β -network, after V_{cc} is grounded and C_E shorted to ground and by neglecting R_1 & R_2 , the circuit is as shown below.




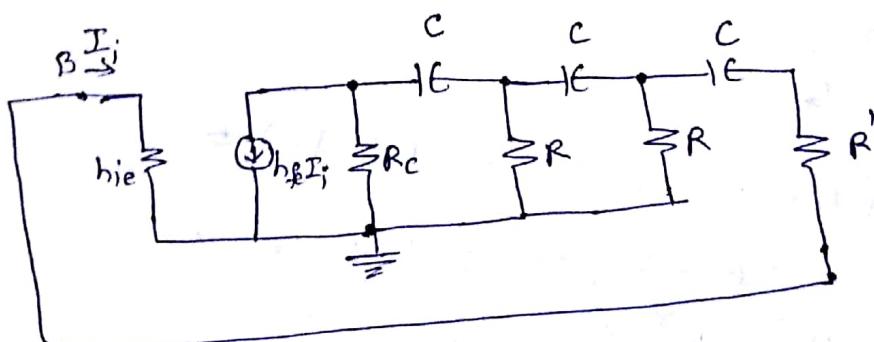Replace the BJT with approximate h-parameter model.




(P.T.O.)

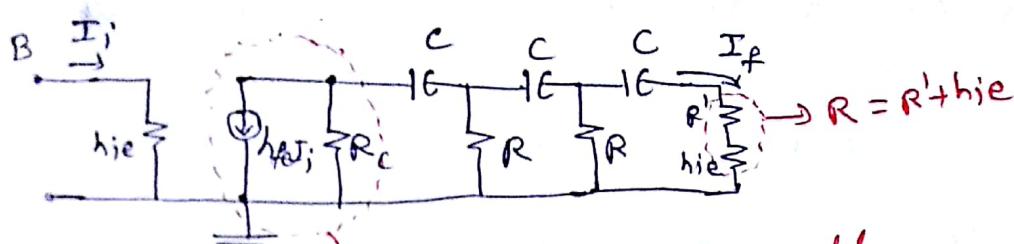After the input and output circuits are separated



Replace with its Thevenin model

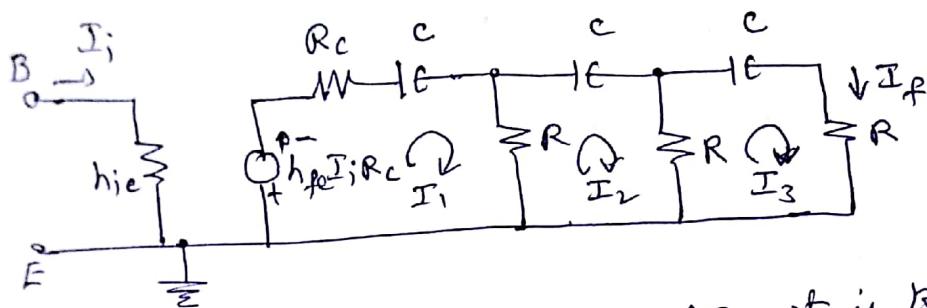After replacing the current source with Thevenin model



To determine the loop gain $-AB$, it is to be calculated
the ratio of I_f to I_i and equated to unity

$$\therefore -AB = \frac{I_f}{I_i} = \frac{I_3}{I_1} = 1$$

Write KVL & to the three loops and solve for I_3

First loop
 $-h_{fe}I_1R_C - R_C I_1 - (-jx_c)I_1 - R(I_1 - I_2) = 0$

$$\therefore -I_1(R_C + R - jx_c) + I_2 R = h_{fe} I_1 R_C$$

Divide both sides with R

$$\therefore I_1 \left(\frac{R_C}{R} + 1 - j\omega \right) - I_2 = -h_{fe} I_1 \frac{R_C}{R}$$

$$\text{Let } K = \frac{R_C}{R} \text{ and } \omega = \frac{jx_c}{R} = \frac{1}{LCR}$$

$$\therefore I_1 (1 + K - j\omega) - I_2 = -h_{fe} K I_1 \quad \text{--- I}$$

Second loop

$$-(I_2 R) - I_2 (-jx_c) - R(I_2 - I_3) = 0$$

$$\therefore I_1 R - I_2 (2R - jx_c) + I_3 R = 0$$

Divide with R

$$\therefore I_1 - I_2 (2 - j\omega) + I_3 = 0 \quad \text{--- II}$$

Third loop

$$-R(I_3 - I_2) - I_3(-jx_c) - I_3 R = 0$$

$$\therefore I_2 R + I_3(2R - jx_c) = 0$$

$$\therefore I_2 = I_3(2 - j\omega) \quad \text{--- III}$$

Substitute III in II

$$\therefore I_1 = I_3(2 - j\omega)(2 - j\omega) - I_3$$

$$= I_3[4 - \omega^2 - j4\omega - 1]$$

$$\therefore I_1 = I_3[3 - \omega^2 - j4\omega] \quad \text{--- IV}$$

Substitute III & IV in eq: I.

$$I_3(3 - \omega^2 - j4\omega)(1 + K - j\omega) - I_3(2 - j\omega) = -h_{fe} K I_i$$

$$\therefore I_3[3 + 3K - j3\omega - \omega^2 - K\omega^2 + j\omega^3 - j4\omega - j4K\omega - 4\omega^2 - 2 + j\omega] = -h_{fe} K I_i$$

$$\therefore I_3[1 + 3K - 5\omega^2 - K\omega^2 + j\omega^3 - j(6 + 4K)\omega] = -h_{fe} K I_i$$

$$\therefore \frac{I_3}{I_i} = \frac{I_f}{I_i} = \frac{-h_{fe} K}{[1 + 3K - \omega^2(5 + K) + j[\omega^3 - \omega(6 + 4K)]]} = -AB$$

For obtaining ~~sustained~~ oscillations according to Barkhausen criteria the loop phase shift should be equal to 0° or $2\pi n^\circ$.

$$\therefore (-AB) = \left[\frac{I_f}{I_i} \right] = -\tan^{-1} \left[\frac{\omega^3 - \omega(6 + 4K)}{1 + 3K - \omega^2(5 + K)} \right] = 0$$

$$\Rightarrow \omega^3 - \omega(6 + 4K) = 0$$

$$\therefore \omega^2 = 6 + 4K$$

$$\therefore \omega = \sqrt{6 + 4K}$$

$$\therefore f = \frac{1}{2\pi RC\sqrt{6 + 4K}}$$

So, at this frequency the loop phase shift is equal to 90° (or) 360° .

Condition on loop gain or Minimum gain required for active device:

The magnitude of the loop gain at this frequency is given by

$$|-AB| = \left| \frac{I_f}{I_i} \right| = \left| \frac{-h_{fe}k}{1+3k-2^2(5+k)} \right|$$

but $k^2 = (6+4k)$

$$\begin{aligned} \therefore |-AB| &= \left| \frac{-h_{fe}k}{1+3k-30-6k} \right| = \left| \frac{-h_{fe}k}{1+3k-(6+4k)(5+k)} \right| \\ &= \left| \frac{-h_{fe}k}{-29-3k} \right| \\ &= \left| \frac{-h_{fe}k}{1+3k-(30+26k+4k^2)} \right| \\ &= \left| \frac{-h_{fe}k}{-29+23k+4k^2} \right| \end{aligned}$$

$$\therefore |-AB| = \frac{h_{fe}k}{29+23k+4k^2}$$

where h_{fe} is +ve
or $k = \frac{R_C}{R}$ is +ve.

To obtain sustained oscillations the loop gain should be little more than unity.

$$\therefore \frac{h_{fe}k}{29+23k+4k^2} \geq 1$$

$$\therefore h_{fe} \geq 23 + 4k + \frac{29}{k}$$

This is the condition on gains i.e. h_{fe} .

(P.T.O.) (9)

Note: $f(k) = h_{fe} = 23 + 4k + \frac{29}{k}$; To know for what value of k , $f(k)$ is minimum, $f'(k) = 0$

$$\therefore f'(k) = 4 - \frac{29}{k^2} = 0$$

$$\Rightarrow k^2 = \frac{29}{4}$$

$$\therefore k = 2.693$$

$$\therefore k = 2.7$$

Hence for $k = 2.7$ h_{fe} value will be minimum.

(P.T.O.)

$\therefore \text{Let } K = 2.7$

$$h_{fe} = 23 + 10.8 + 10.77$$

$$h_{fe} = 44.57$$

$$\therefore h_{fe\min} = 44.5$$

Therefore for obtaining sustained oscillations using BJT, the h_{fe} value of the transistor should be greater than 44.5. A BJT with $h_{fe} \leq 44.5$ no oscillations can be obtained.


Design Considerations:

- ① During design the frequency(f) of oscillations will be given so, select $C \leq 1 \mu F$ and calculate R using the formula $f = \frac{1}{2\pi RC \sqrt{6+4K}}$
- ② If exact value of resistance is not available then select a potentiometer with proper value and set it equal to R .
- ③ Select a BJT, with $h_{fe} > 44.5$, and operate in CE configuration with $R_C = K R = 2.7 R$ for obtaining sustained oscillations.
- ④ Draw the full circuit with design values.

Note: Advantages & disadvantages of RC phase-shift oscillator is on Page: 9.a

⑥ Generalized LC oscillators: (Tuned oscillators)

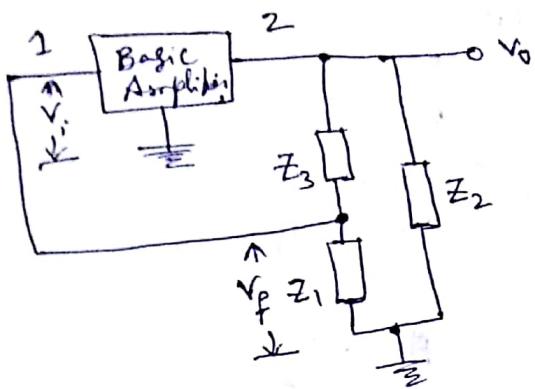A generalized LC oscillator can be shown as below



Explanation

Note: ① The Basic Amplifier may be a CE or CS amplifier. Z_1, Z_2, Z_3 are reactance of either inductive or capacitive type.

$$\textcircled{2} \quad Z_1 = jX_1$$

$$Z_2 = jX_2$$

$$Z_3 = jX_3$$

if any of Z_1, Z_2, Z_3 are inductive reactance then $X_p = WL$ & if capacitive then

$$X = -\frac{1}{WC}$$

- ③ Z_1, Z_2 & Z_3 forms the β -network and the voltage across Z_1 is fed back to the basic amplifier.

- ② When the Basic Amplifier is a FET then ~~Basic Amp~~ ^{Basic Amp} does not load the β -network, because its input impedance is very high.

- ⑤ If Basic amplifier is a BJT then Basic Amp loads the β -network due to its low input impedance.

Derivation for loop gain:

- ⑥ It is convenient to calculate the loop gain $-AB$ and equate it to unity for getting the expression for frequency of oscillations.

- ⑦ Hence calculate the voltage gains of the Basic Amplifier and β separately and substitute in $-AB = 1$.

- ⑧ Assume a FET is used in CS Configuration as the basic amplifier. The equivalent ~~of~~ circuit will be as shown below.

(P.T.O.) 10

AC phase shifter

Advantages:

- ① The circuit is simple to design.
- ② Produces pure sinusoidal output waveform.
- ③ Provides the output over audio frequency range.
- ④ It needs high ' β ' ~~the~~ hfe Transistor to over come losses in the network.

Disadvantage: The frequency of oscillations, all the capacitors are to be varied simultaneously.

- ① To change the frequency of oscillations, all the capacitors are to be varied simultaneously.
- ② The frequency stability is poor due to change in parameter values with temperature, aging etc.

Wien Bridge:


Advantages:

- ① It provides a stable low distortion output over a wide range of frequency.
- ② It provides better stability as it uses both positive and negative feedback.
- ③ Overall gain is high because two stage amplifier is used.
- ④ Frequency can be easily adjusted by varying either a resistor or capacitors.

Disadvantages:

- ① It is costlier because more components are used.
- ② It can not be used to generate very high frequencies.

Derivation for β and gain A_v .

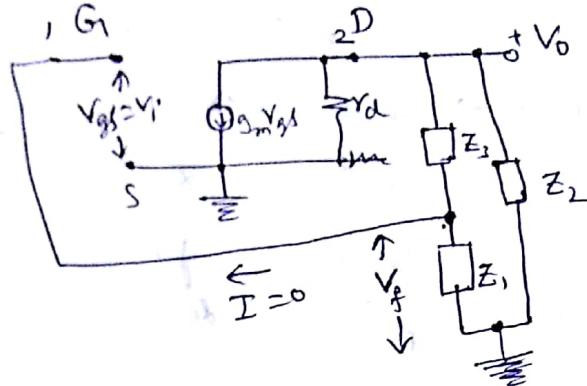

$$\textcircled{1} \quad \beta = \frac{V_f}{V_o} = \frac{V_f}{V_o}$$

$V_f = -\frac{V_o}{Z_1 + Z_3} \times Z_1$

$$\therefore \beta = -\frac{Z_1}{Z_1 + Z_3}$$

$$\textcircled{2} \quad \text{Basic Amplifier voltage gain}$$

$$Z_L = Z_2 || (Z_1 + Z_3) = \frac{Z_2(Z_1 + Z_3)}{Z_1 + Z_2 + Z_3}$$

$$\therefore V_o = -G_m V_{gs} \times \frac{r_d Z_L}{r_d + Z_L}$$

$$\therefore A_v = \frac{V_o}{V_{gs}} = -\frac{G_m r_d Z_L}{r_d + Z_L}$$

$$= -\frac{M \cancel{Z_2(Z_1 + Z_3)}}{\cancel{Z_2(Z_1 + Z_3)} / (Z_1 + Z_2 + Z_3)}$$

$$= \frac{M Z_1 Z_2 + Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + r_d (Z_1 + Z_2 + Z_3)}$$

$$A_v = -\frac{M \cancel{(Z_1 + Z_2 + Z_3)} Z_2 (Z_1 + Z_3)}{Z_1 Z_2 + Z_2 Z_3 + r_d (Z_1 + Z_2 + Z_3)}$$

$\textcircled{3}$ Therefore the loop gain $1 + A\beta$ is given by

$$-A\beta = \left[\frac{-M \cancel{(Z_1 + Z_2 + Z_3)} Z_2 (Z_1 + Z_3)}{Z_1 Z_2 + Z_2 Z_3 + r_d (Z_1 + Z_2 + Z_3)} \right] \times \left[\frac{-Z_1}{Z_1 + Z_3} \right]$$

This should be equal to unity.

$$\therefore + \frac{-M Z_1 \cancel{(Z_1 + Z_2 + Z_3)} Z_2}{(Z_1 + Z_3) [Z_1 Z_2 + Z_2 Z_3 + r_d (Z_1 + Z_2 + Z_3)]} = 1$$

(P.T.O.)

Now substitute $z_1 = jx_1$, $z_2 = jx_2$ and jx_3

$$\therefore \Rightarrow -\frac{M \times j^2 \times x_1 z_2 (\cancel{x_1} \cancel{x_2} \cancel{x_3} + \cancel{x_3})}{-x_1 x_2 - x_2 x_3 + jx_d (x_1 + x_2 + x_3)} = 1$$

$$\Rightarrow -\frac{M \times x_1 z_2 (\cancel{x_1} \cancel{x_2} \cancel{x_3} + \cancel{x_3})}{x_1 x_2 + x_2 x_3 - jx_d (x_1 + x_2 + x_3)} = 1$$

To obtain the oscillations the phase of the LHS should be zero and the loop magnitude should be unity.

$$\therefore \tan^{-1}\left(\frac{jx_d(x_1 + x_2 + x_3)}{x_1 x_2 + x_2 x_3}\right) = 0$$

$$\boxed{\therefore x_1 + x_2 + x_3 = 0} \quad \text{--- I}$$

Therefore the magnitude is given by

$$| -AB | = \frac{| M x_1 x_2 |}{| x_2 (x_1 + x_3) |}$$

$$-AB = \frac{M x_1}{-x_2}$$

$$\therefore \text{loop gain magnitude} = \frac{M x_1}{x_2}$$

$$\boxed{\therefore -AB = \frac{M x_1}{x_2}} \quad \text{--- II}$$

This loop gain should be equal to unity and the therefore x_1 and x_2 reactances should be of same type means both should be either inductors or both should be of capacitors.

Case 1: Colpitts oscillator:

If x_1 and x_2 are capacitors then the circuit is called as Colpitts oscillator. From eqn: I

$$x_3 = -x_1 - x_2$$

$\therefore x_3 = -(x_1 + x_2)$
means x_3 should be inductive type.

Therefore $x_1 = -\frac{1}{WC_1}$; $x_2 = -\frac{1}{WC_2}$ and $x_3 = WL$

$$\begin{aligned} \therefore WL &= \frac{1}{WC_1} + \frac{1}{WC_2} \\ &= \frac{1}{W} \left[\frac{1}{C_1} + \frac{1}{C_2} \right] \\ WL &= \frac{1}{W C_{eq}} \end{aligned}$$

$$\text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\therefore \omega^2 = \frac{1}{LC_{eq}}$$

$$\boxed{\therefore f = \frac{1}{2\pi\sqrt{LC_{eq}}}}$$

Therefore the circuit will oscillate with this frequency.

From equation II we have

$$-AB = \frac{\mu^{x_1}}{x_2} = \frac{\mu C_2}{x_1 C_1} = \frac{\mu C_2}{C_1}$$

To obtain oscillations the magnitude of the loop gain

should be ~~more than unity~~

$$\therefore \frac{\mu C_2}{C_1} \geq 1$$

$$\boxed{\therefore \mu \geq \frac{C_1}{C_2}}$$

Case 2: Hartley oscillator:

If x_1 and x_2 are inductors then the circuit is called as Hartley oscillator. From eqn: I

$$x_3 = -(x_1 + x_2)$$

when x_1 & x_2 are inductors then x_3 should be a capacitor.

Therefore

$$x_1 = \omega L_1^{+WM}; x_2 = \omega L_2^{+WM} \text{ and } x_3 = -\frac{1}{\omega C_2}$$

$$\therefore -\frac{1}{\omega C} = -\omega(L_1 + L_2^{+2M}) \\ = -\omega L_{eq}.$$

$$\omega^2 = \frac{1}{L_{eq}C}$$

$$\text{where } L_{eq} = L_1 + L_2 + 2M$$

$$\therefore f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

The circuit will oscillate with this frequency. And we know that

$$-A\beta = \frac{Mx_1}{x_2}$$


$$= \frac{M\omega(L_1 + M)}{\omega(L_2 + M)} \\ = \frac{M(L_1 + M)}{(L_2 + M)}$$

To obtain oscillations the magnitude of loop gain should be more than unity.


$$\therefore M \frac{L_1 + M}{L_2 + M} \geq 1$$

$$\therefore M \geq \frac{L_2 + M}{L_2 + M}$$

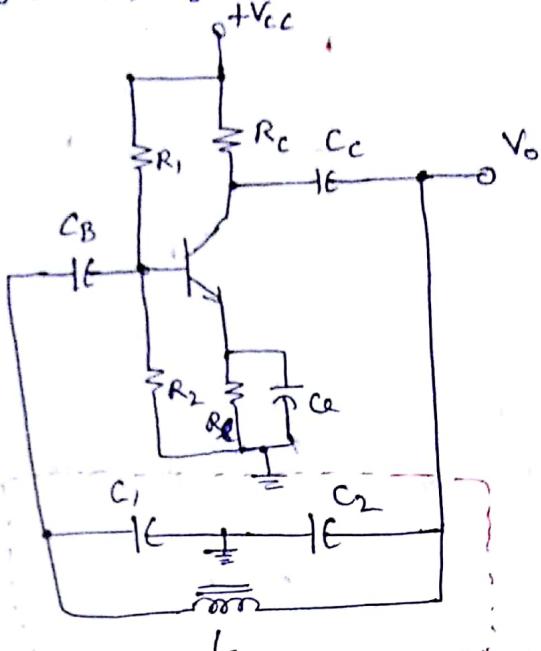
The Hartley and Colpitts oscillators using FET and BJT are as shown below-




① Colpitts oscillator using BJT

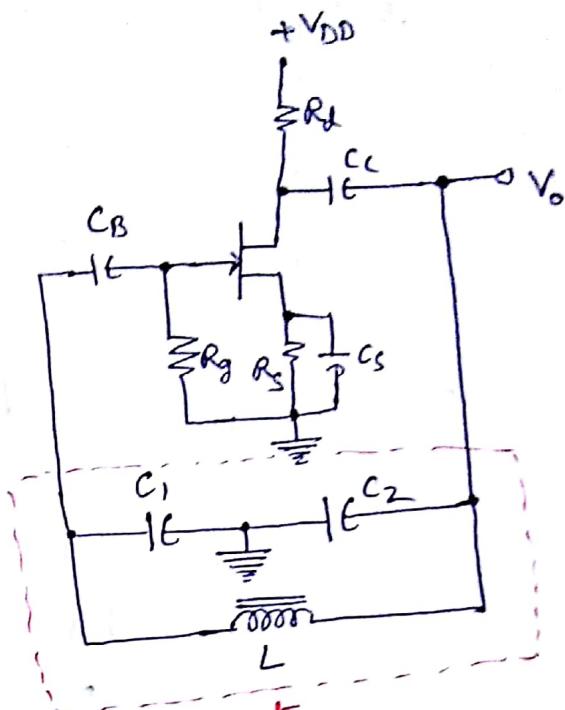

② Colpitts oscillator using FET

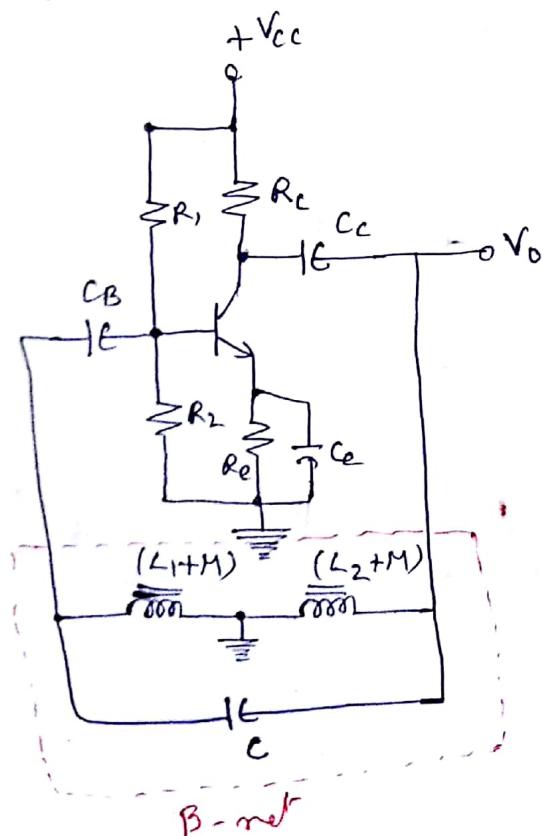


③ Hartley oscillator using BJT

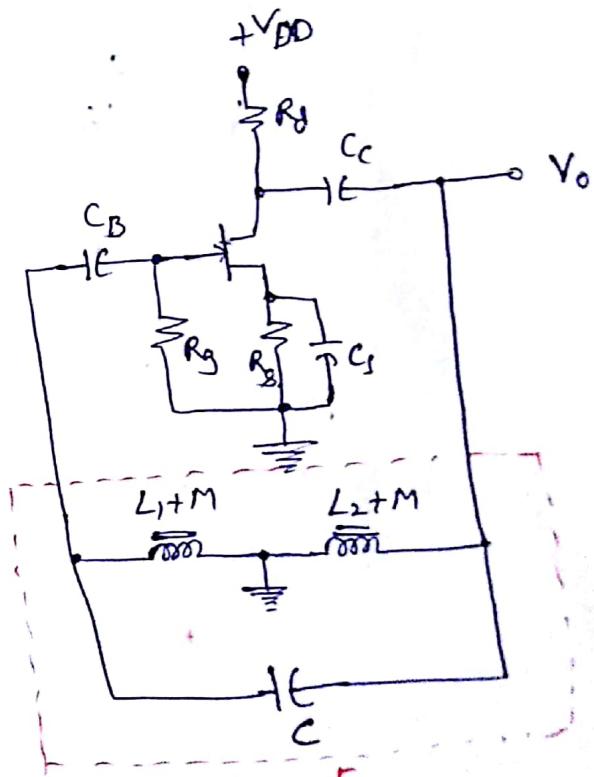

④ Hartley oscillator using FET

- Note:
- ① In the above circuits C_B & C_a behave like short circuit at the frequency of oscillations.
 - ② The frequency of oscillations is given by
- For Hartley oscillator $\rightarrow f = \frac{1}{2\pi\sqrt{L_{eq}C}}$; $L_{eq} = L_1 + L_2 + 2m$
 - For Colpitts oscillator $\rightarrow f = \frac{1}{2\pi\sqrt{LC_{eq}}}$; $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$

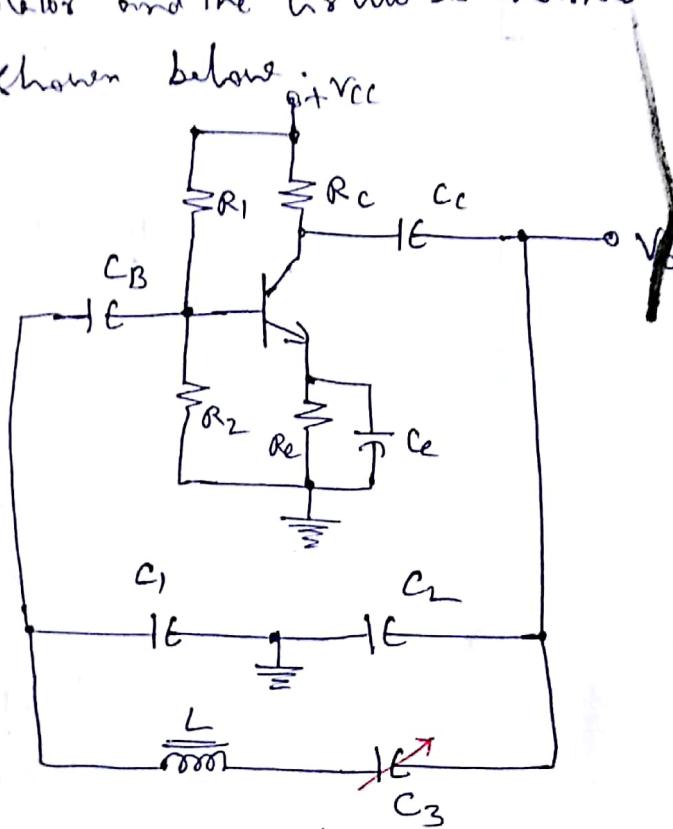- ③ To improve the frequency stability a capacitor C_3 is connected in series with inductor in Colpitts oscillator and the circuit is named as CLAPP oscillator as shown below.



CLAPP oscillator


$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

(7) Wien-Bridge oscillator:

The circuit of Wien-Bridge

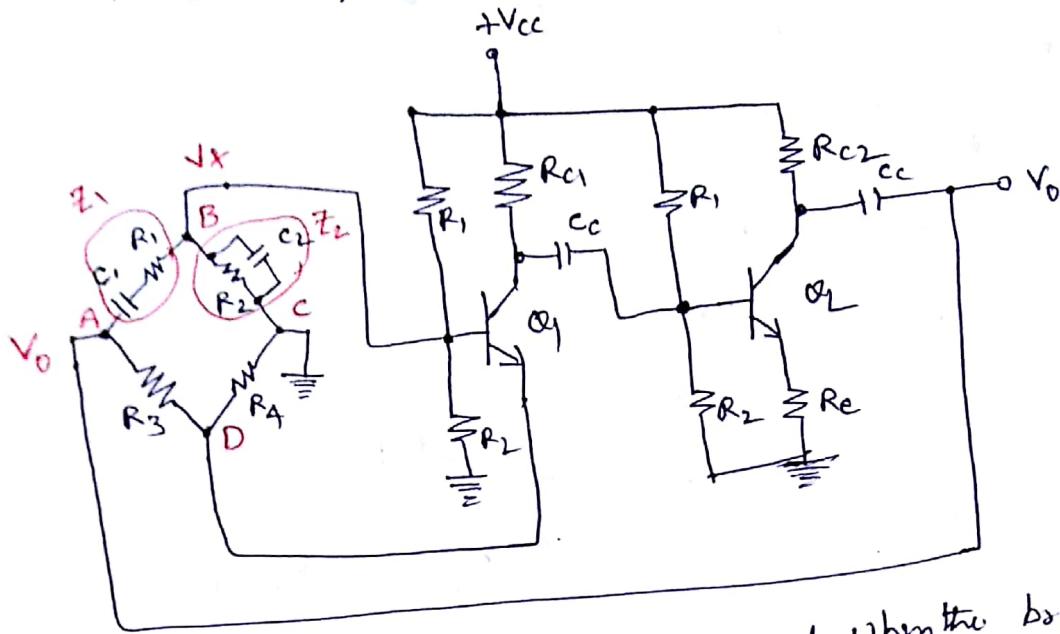

- ① Bridge act behaves as β -network and when the bridge is balanced it does not provide any phase shift and behave as a perfect resistive circuit.
- ② The transistors Q_1 and Q_2 are operated in CE configuration hence the overall voltage gain will be very large and combinedly both stages provide 360° . Hence β -network need not provide any additional phase shift.
- ③ Here β -network provides +ve feedback when it is balanced and R_E provides -ve feedback to reduce the gain.

When the bridge is balanced

$$\frac{R_3}{R_4} = \frac{z_1}{z_2}$$

$$\therefore \frac{z_1}{z_2} = \frac{(R - jX_C)(R - jX_C)}{-jR X_C}$$

$$= \frac{R^2 - X_C^2 - j2X_C R}{-jX_C R}$$

$$\therefore \frac{z_1}{z_2} = 2 + j\left(\frac{R^2 - X_C^2}{X_C R}\right)$$

where $z_1 = R_1 - jX_C$
 $z_2 = \frac{R_2(-jX_C)}{R_2 + jX_C}$

Let $R_1 = R_2 = R_{PA}$; $C_1 = C_2 = C$

$$\therefore z_2 = \frac{-jR X_C}{R - jX_C} = \frac{1}{R + jX_C}$$

$$z_1 = R - jX_C$$

(P.T.O.)

$$\therefore \frac{R_3}{R_4} = 2 + j \left(\frac{R^2 - X_C^2}{X_C R} \right)$$

LHS is real hence RHS should also be real

$$\therefore R^2 - X_C^2 = 0$$

$$\therefore \omega^2 = \frac{1}{X_C^2}$$

$$\therefore \omega^2 = \frac{1}{R^2 C^2}$$

$$\boxed{\therefore f = \frac{1}{2\pi RC}}$$

Therefore the will be balanced only for this frequency f
and at this frequency

$$\frac{R_3}{R_4} = 2 \Rightarrow$$

$$\boxed{R_3 = 2R_4}$$

Analysis of β -network:

$$\beta = \frac{V_f}{V_o}$$

$$\therefore V_f = Z_2 I$$

$$= Z_2 \times \frac{V_o}{Z_1 + Z_2}$$

$$\therefore \beta = \frac{V_f}{V_o} = \frac{Z_2}{Z_1 + Z_2}$$

$$= \frac{-jX_C R / (R - jX_C)}{R - jX_C - \frac{jX_C R}{R - jX_C}}$$

$$= \frac{-jX_C R}{(R - jX_C)^2 - jX_C R} = \frac{-jX_C R}{R^2 - X_C^2 - j2X_C R - jX_C R}$$

$$= \frac{-jX_C R}{R^2 - X_C^2 - j3X_C R}$$

$$= \frac{1}{3 - \left(\frac{R^2 - X_C^2}{-jX_C R} \right)}$$

$$\beta = \frac{1}{3 - j \left(\frac{R^2 - X_C^2}{X_C R} \right)}$$

$V_f \rightarrow$ voltage across Z_2 and
 $V_o \rightarrow$ voltage across $(Z_1 + Z_2)$ because
 $V_o \rightarrow$ voltage across $(Z_1 + Z_2)$ because
the current flowing through
Base is negligibly small and
hence neglected.

But β -network need not provide any phase shift. The imaginary part should be equal to zero

$$R^2 - X_C^2 = 0 \Rightarrow R = X_C \Rightarrow \omega = \frac{1}{RC} \Rightarrow f = \frac{1}{2\pi RC}$$

at this frequency the magnitude of the β -net is given by

$$|\beta| = \frac{1}{3}$$

Thus for the gain of the basic amplifier (2-stage CE amp.) should be greater than or equal to 3, to obtain sustained oscillations.

$$\therefore |A| \geq 3$$

Design Considerations for Variable Frequency Operation: Assume $C_1 = C_2 = C \leq 1 \mu F$

- ① For the given frequency and calculate R using

$$f = \frac{1}{2\pi RC}$$

② Set $R_3 = 2R_4$ by assuming R_4 any value available.

③ Design 2-stage CE amplifiers with voltage gain

④ $A = A_1 \times A_2 = 3$ and take $R_{E1} = R_4$ (as in step 2).

⑤ Draw the full CKT with design values.



For obtaining variable frequency of operation the two capacitors should be ganged together.

Note: Advantages of Wien-Bridge oscillator are on Page 9.0

⑧ Crystal oscillator:

crystal:

- ① The crystal is a thin slice of piezo-electric material such as quartz, tourmaline and rochelle salt which exhibit Piezo-Electric Effect.
 - ② The Piezo-electric effect means the crystal produces electric charge to any mechanical stress and in reverse effect, it produces mechanical strain to an electric field.
 - ③ The natural frequency of a crystal is inversely proportional to the thickness 't' of the crystal. The frequency is given by
- $$f = \frac{P}{2\pi} \sqrt{\frac{Y}{\rho}}$$
- where
- $$P = 1, 2, 3, \dots$$
- t = Thickness of the crystal
- Y = Young's modulus
- ρ = Density of the material
- ④ The crystal symbol, electrical equivalent and reactance graph are given below

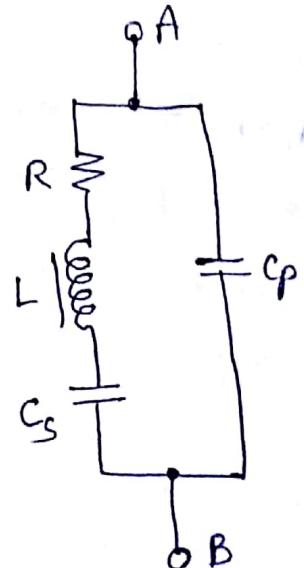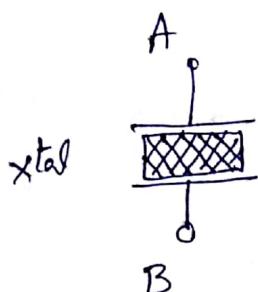


R → resistance of the crystal

L → inductance offered by the crystal

Cs → Series Capacitor

Cp → Parallel capacitor

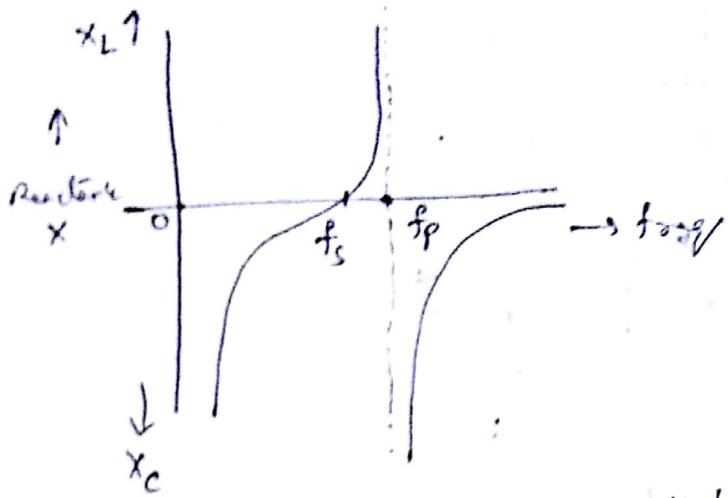

- ⑤ A crystal exhibits two resonant frequencies, series resonant frequency f_s and parallel resonant frequency f_p , given by

$$f_s = \frac{1}{2\pi\sqrt{LC_S}}$$

$$f_p = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

where $\frac{1}{C_{eq}} = \frac{1}{C_S} + \frac{1}{C_P}$

- ⑥ For the frequencies between f_s and f_p crystal exhibits inductive reactance, hence crystal can be used in the place of inductor in a Colpitts oscillator.

- ⑦ For frequencies less than f_s and more than f_p crystal exhibits capacitive reactance, hence it can be used in the place of capacitor in a Hartley oscillator.


- Advantages** ⑧ The Q factor for crystal is more than 100. crystals with Q in the range several thousand to several hundred thousand are available commercially in the frequency range from few kHz to few MHz.

- ⑨ The frequency stability of 1 part in 10^{10} can be obtained in temperature environment.

controlled

(P.T.O.)

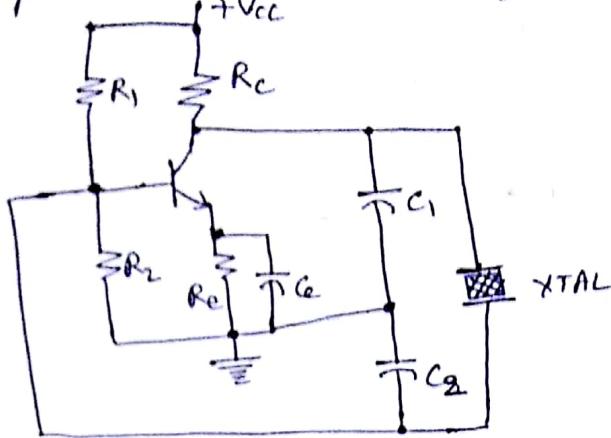- ⑩ The Colpitts oscillator using crystal is shown below.



⑨ Stability of oscillators:

ⓐ Frequency stability:

The frequency stability of an oscillator is a measure of its ability to maintain as nearly a fixed frequency as possible over as long a time interval as possible.

The allowable variation in frequency may be anywhere between 10^{-2} to 10^{10} depending on the area of application.

The deviation (variation) in frequency of an oscillator occurs due to the following reasons:

- ① Due to change in temperature, the values of the frequency-determining components, i.e. resistors, inductor, capacitors, changes.
- ② Due to variation in power supply, unstable transistor parameters, change in climatic conditions and aging.
- ③ the effective resistance of the tank circuit is changed when the load is connected.
- ④ Due to variation in biasing conditions and loading conditions.

The variation in frequency with temperature is given by

$$S_{W,T} = \frac{\Delta W/W_0}{\Delta T/T_0} \text{ ppmc (Parts Per million per } ^\circ\text{C})$$

where W_0 and T_0 are the desired frequency and operating temp. If no temperature control is available then ~~an~~ inductor with positive temperature coefficient and a capacitor with negative temperature coefficient can reasonably maintain frequency stability.

The frequency stability is defined as

$$S_W = \frac{d\theta}{dW}$$

where $d\theta$ is the phase shift introduced for a small frequency change in nominal frequency f_0 . The circuit giving larger value of $\frac{d\theta}{dW}$ is the oscillator with more frequency stability. The circuit with larger θ can provide more frequency stability in oscillators. [i.e., $S_W \propto \theta$]

(b) Amplitude stability:

The amplitude stability of an oscillator is a measure of its ability to maintain as nearly a fixed amplitude as possible over a long or time interval as possible.

In the case of RC oscillators, the amplitude variations, due to aging of transistors and fluctuations in circuit components, can be stabilized by replacing the resistors by resistors which exhibit positive temperature coefficient of resistance.

on LC oscillators, the variation in tank circuit resistance can be compensated by connecting negative resistance devices across tank circuit. The devices like dynatron, transistor, thermistor, UJT and Tunnel diode, can be operated in their negative resistance region and placed across a high Q. tank circuit for maintaining amplitude stability.

(10) Problems:

- ① A FET phase-shift oscillator has $g_m = 5 \text{ mV}$ and $R_d = 50 \text{ k}\Omega$. The β -network resistance is $100 \text{ k}\Omega$ and capacitance is 64.79 pF . Calculate the frequency of oscillations and value of R_d . ($f_o = 10 \text{ kHz}$; $R_d = 7.8 \text{ k}\Omega$)
- ② RC phase shift oscillator using BJT has $R_C = 18 \Omega$, and $R = 6 \Omega$ & $C = 1500 \text{ pF}$ calculate f_o . (4.168 kHz)
- ③ Design an RC phase shift oscillator for 12 kHz . Ignore the effect of R_1, R_2, R_E or C_B, C_E .
- ④ In a Hartley oscillator, calculate L_2 , if $L_1 = 15 \text{ mH}$ & $C = 50 \text{ pF}$ and mutual inductance of $5 \mu\text{H}$ and $f_o = 168 \text{ Hz}$ ($L_2 = 2.939 \text{ A}$)
- ⑤ For a transistorized Hartley oscillator $L_1 = 2 \text{ mH}$ & $L_2 = 20 \mu\text{H}$ while the frequency is to be changed from 950 kHz to 2050 kHz . Calculate the range over which the capacitor is to be varied.
- ⑥ A Colpits oscillator has $C_1C_2 = 0.001 \mu\text{F}$ & $L = 5 \text{ mH}$. What is f_o if L is doubled? What should be inductance to double the frequency?

$$\begin{cases} f = 3.183 \text{ MHz} \\ L = 1.25 \text{ mH} \end{cases}$$

- ⑦ A crystal has $L = 0.1\text{H}$, $C = 0.01\text{pF}$; $R = 10\text{k}\Omega$ and $C_p = 1\text{pF}$. Find series and parallel resonant frequencies and Q factors at both frequencies.

$C_p \rightarrow$ Package or $C_M \rightarrow$ Mounting

- ⑧ A crystal has $L = 2\text{H}$, $C = 0.01\text{pF}$ and $R = 2\text{k}\Omega$, its mounting capacitance is 2pF . Calculate its series and parallel resonant frequencies.

—
END of UNIT - III.

UNIT - III

FEEDBACK AMPLIFIERS

- *① Derive the expression for gain with negative feedback.
- *② Prove the gain stabilizes with negative feedback.
- *③ Explain the general characteristics of negative feedback amplifiers.
- *④ Draw the block diagrams of four negative feedback ~~topologies~~ topologies and explain.
- *⑤ Prove the input impedance decreases for shunt sampling.
- *⑥ Justify the output impedance increases for current sampling.
- *⑦ Define the expressions for A_{vf} , R_{if} and R_{of} for a voltage series feedback amplifier.
- *⑧ Draw the circuit of a current shunt feedback amplifier and derive the expression for A_{if} .
- *⑨ Draw the circuit of a transresistance amplifier and derive the expression for transresistance gain.
- *⑩ Compare the four feedback amplifier topologies.

Anti-Parameter	Topology			
	Voltage-Series	Voltage-Shunt	Current-Series	Current-Shunt
① Gain stabilized	Voltage gain	Transresistance increases	Transconductance increases	Current gain increases
② Bandwidth	increases	increases	increases	decreases.
③ Input resistance (R_i)	increases	Decreases	increases	increases
④ Output resistance (R_o)	Decreases	Decreases	increases	increases
⑤ Harmonic Distortion	Decreases	Decreases	Decreases	Decreases
⑥ Noise	Decreases	Decreases	Decreases	Decreases

(PTO)

OSCILLATORS

- *① Derive the condition for oscillations and state Barkhausen Conditions.
 - *② Prove the minimum h_{fe} required is 44.5, to obtain oscillations using BJT in RC-phase shift oscillator.
 - *③ Derive the expression for frequency of oscillations and gain required for FET amplifier in RC phase-shift circuit.
 - *④ Draw the circuit of a Hartley oscillator and derive the expression for frequency of oscillations.
 - *⑤ Design a Colpitts oscillator for 100 kHz frequency.
 - *⑥ Write short notes on Wien-Bridge oscillator.
 - *⑦ Write short notes on crystal.
 - *⑧ Discuss the stability considerations in oscillators.
 - *⑨ The parameters of a crystal are given as
 $L = 0.33 \text{ H}$, $C = 0.065 \text{ pF}$, $C_p = 1.0 \text{ pF}$ and $R = 5.5 \text{ k}\Omega$
 Find the series resonant frequency and Q-factor.
 - *⑩ Compare the advantages and disadvantages of RC, LC and crystal oscillators.

(P.T.O.)

UNIT - II

A: 05/3/15

(43)

Question Bank on Feedback Amplifiers:

Short questions:

- ① List the advantages and disadvantages of negative feedback in amplifiers.
- ② An amplifier has an open loop gain of 1000, what would be the gain if 1% of the output is fed back in phase opposition.
- ③ For a feedback amplifier the gain is 810 when $\beta = 0.1$, calculate the open loop gain of the amplifier.
- ④ Prove the gain stabilizes with negative feedback.
- ⑤ Define the expression for input impedance of a current-shunt feedback amplifier.
- ⑥ Derive the expression for output impedance of a voltage series feedback amplifier.
- ⑦ Define the expression for o/p impedance of voltage series [Transconductance] amplifier.
- ⑧ Define the expression for o/p impedance of voltage shunt feedback amplifier.
- ⑨ For an amplifier the open loop gain is 100 when the source signal of 50 mV is applied. If $\beta_f = 1\%$ of the o/p is fed back negatively, what will the output voltage be?
- ⑩ An amplifier has an input resistance of $200 k\Omega$ when negative feedback is applied it was found to $20 M\Omega$. Calculate the loop gain and feedback factor if the open loop gain is 1000.




(P.T.O.)

Elbow questions:

define &

- Ques

 - ① Draw the block diagrams of four topologies and explain which gain will be stabilized and how the input and output impedances are affected.
 - ② Derive the expressions for input and o/p Impedance for a Voltage shunt feedback amplifier.
 - ③ Derive the expressions for both cut-off frequencies with feed forward and hence prove the Bandwidth increases with negative feedback.
 - ④ Draw the circuit of C/E amplifier without bypass capacitor and check is there any feedback present, if present identify the topology. Suggest R₁, R₂, biasing resistors and C_B, C_C are neglected the effect of R₁, R₂ & C_B, C_C.
 - ⑤ An amplifier with open-loop voltage gain 1000 ± 100 is available. It is necessary to have an amplifier whose gain varies by no more than ± 0.1 percent with the reverse transmission factor β .
 - (a) Find the reverse transmission factor β .
 - (b) Find the gain with Feedback.
 - (c) For the transistor characteristics shown below $I_{CBO} = 1\text{A}$, $I_{CEO} = 0$, $\beta = 100$, $V_{BE} = 0.7\text{V}$, $V_{CE} = 10\text{V}$. Determine (i) R_{IF} , (ii) R_{OF} , (iii) R_{IF} , (iv) R_{OF} .
 - ⑥ For the transistor characteristics shown below $I_{CBO} = 1\text{A}$, $I_{CEO} = 0$, $\beta = 100$, $V_{BE} = 0.7\text{V}$, $V_{CE} = 10\text{V}$. Determine (i) R_{IF} , (ii) R_{OF} , (iii) R_{IF} , (iv) R_{OF} .

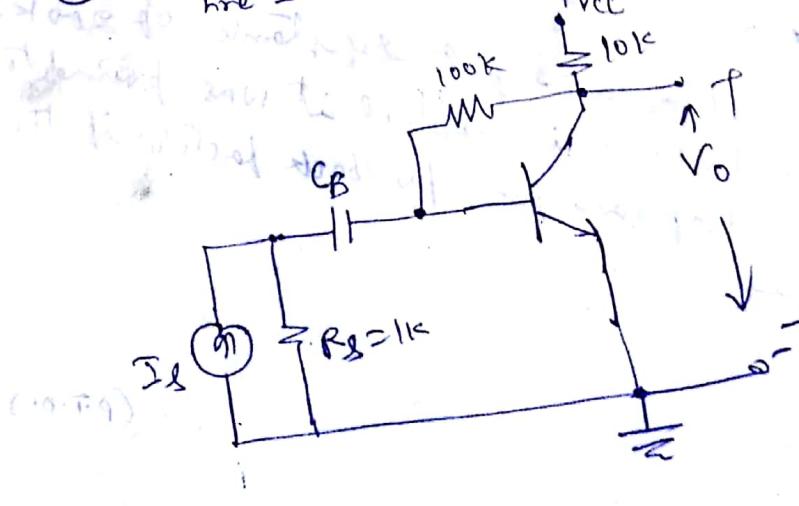

UNIT-II END OF PART-A