

High - Frequency Analysis:


Topics to be covered:-

- 1) Hybrid- π model and typical parameter values.
- 2) Hybrid- π Conductances in terms of h-parameters.
- 3) Short circuit current gains at HFs.
- 4) Definitions of f_p , f_L and f_T .
- 5) Gain Bandwidth Product (Figure of Merit).
- 6) Current gains with load resistance (R_L)

① Hybrid- π model and typical parameter values:

- h-parameter model is not valid at high frequency. At low frequencies it is assumed that the rate of diffusion is large than the rate of change of input voltage or current. But at high frequencies this assumption is not valid. So, a new model, Hybrid- π model, is derived for BJT to predict the use of high frequencies.

GRIACOLETTO model

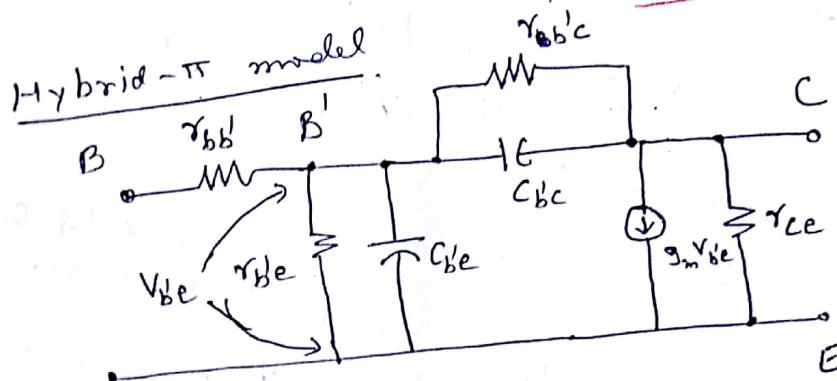

- B' is the Virtual Base terminal, physically cannot be accessible.
- r_{bb}' → Base Spreading Resistance.
- r_{be} → The ~~leakage~~ resistance across Emitter Junction.
- C_{be} → Diffusion Capacitance across Emitter Junction.
- r'_{bc} → Reverse biased collector Junction resistance.
- g_m → Trans or Neutral Conductance
- r_{ce} → Resistance between Collector and Emitter.

(P.T.O.)

Note: Hybrid-II conductances are sensitive to ambient conditions. If I_C changes all conductances changes.

Typical values of Hybrid-II model

for $I_C = 1.3 \text{ mA}$ at room temperature

$$g_m = 50 \text{ mA/V} ; r_{bb'} = 100 \text{ k}\Omega$$

$$r_{be} = 11 \text{ k}\Omega ; r_{bc} = 4 \text{ M}\Omega$$

$$r_{ce} = 80 \text{ k}\Omega ; C_c = 3 \text{ pF}$$

$$C_e = 100 \text{ pF}$$

② Hybrid-II Conductances in terms of h-parameters:

① Transconductance (g_m)

it is defined as

$$g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{CE} = 0}$$

we know that

$$I_C = I_{CO} - \alpha I_E$$

[From Transistor Current Components
in CB Configuration]

$$\therefore g_m = -\alpha \frac{\partial I_E}{\partial V_{BE}}$$

($\because I_{CO}$ is constant and α is independent of V_{BE} .)

$$g_m = +\alpha \frac{\partial I_E}{\partial V_E}$$

[\because for p-n-p transistor $V_E = -V_{BE}$ and
for n-p-n transistor $V_E = +V_{BE}$]

$$\therefore g_m = \alpha \times \frac{1}{r_e}$$

[$r_e = \frac{\partial V_E}{\partial I_E}$ is the dynamic
resistance of the Emitter
Junction.]

but we know that $\gamma_e = \frac{\gamma V_T}{I}$ for a given diode

$\therefore \gamma_e = \frac{V_T}{I_E}$ for emitter junction with $\gamma = 1$.

$$\therefore g_m = \frac{\partial I_E}{V_T}$$

$$g_m = \frac{I_{CO} - I_C}{V_T}$$

$$g_m = \frac{-I_C}{V_T}$$

$$\therefore |I_{CO}| \ll |I_C|$$

but for p-n-p transistor I_C is negative hence the collector terminal.

$$\therefore g_m = \frac{I_C}{V_T} \quad \text{for p-n-p}$$

for n-p-n transistor I_C is positive but

$$V_E = +V_B'E$$

$$\therefore g_m = \frac{I_C}{V_T} \quad \text{for n-p-n}$$

in general for any transistor

$$g_m = \frac{|I_C|}{V_T}$$

(P.T.O.)

(b) Input Conductance (g'_{be}) ($= \frac{1}{r'_{be}}$)

The Hybrid- π model at low frequencies can be obtained as [∴ at low frequencies all capacitors are open]

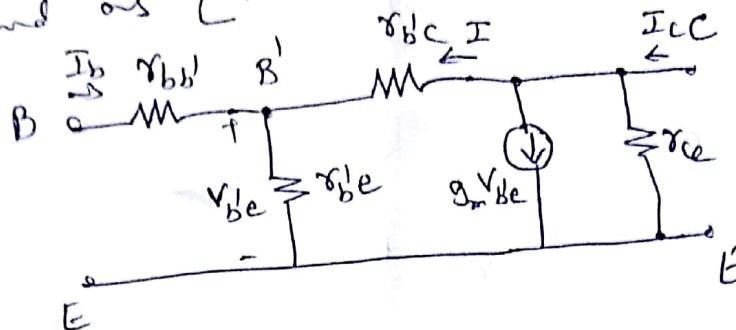


Fig: 1

and the h-parameter model valid for low frequencies is given below.

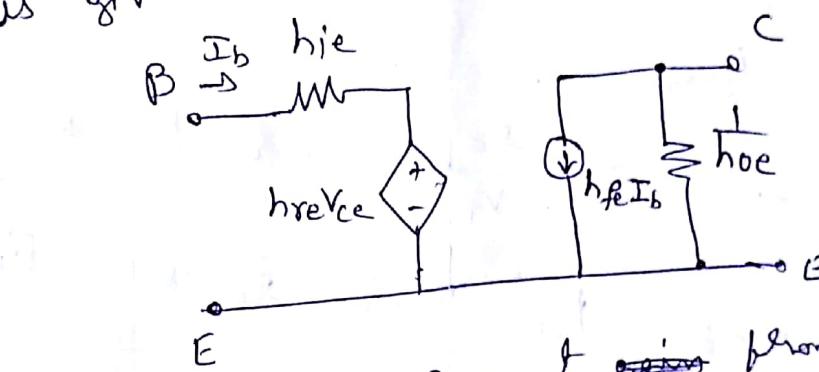


Fig: 2

The short circuit current from Fig: 1 is given by $-g_m V_{be}$ and the same from Fig: 2 is given by $-h_{fe} I_b$

$$\therefore h_{fe} I_b$$

$$\therefore h_{fe} I_b = g_m V_{be}$$

$$\text{but } V_{be} \approx I_b r'_{be}$$

$$\therefore h_{fe} I_b = g_m I_b r'_{be}$$

$$\therefore r'_{be} = \frac{h_{fe}}{g_m}$$

$$\text{or } \text{g}'_{be} = \frac{g_m}{h_{fe}}$$

$$\text{Note: Since } g_m = \frac{|I_C|}{V_T} \text{ & } V_T = \frac{T}{11,600}$$

$r'_{be} \propto T$ and

$$\propto \frac{1}{|I_C|}$$

(c) Feed back Conductance (g_{bc}') ($= \frac{1}{r_{bc}'}$)

On Fig: 2~~00~~, hre is defined as

$$hre = \left. \frac{\text{o/p voltage}}{\text{o/p voltage}} \right|_{I_b=0} = \frac{V_{be}}{V_{ce}}$$

From Fig: 1

$$V_{ce} = (r_{be} + r_{bc}') I \quad \checkmark$$

$$V_{be} = r_{be} I$$

$$\therefore hre = \frac{r_{be}}{r_{be} + r_{bc}'}$$

$$\therefore hre r_{bc}' = (1 - hre) r_{be}$$

$$\approx r_{be}$$

$$\left. \begin{array}{l} hre \ll 1 \\ hre = 10^4 \end{array} \right\}$$

$$\boxed{\therefore r_{bc}' = \frac{r_{be}}{hre}}$$

$$\boxed{\therefore g_{bc}' = hre g_{be}}$$

Base - Spreading resistance (r_{bb}')

(d)

From Fig: 2 the o/p resistance with o/p short ckted then

short ckt is hie.

From Fig: 1 when o/p short ckted then
o/p impedance is given by $r_{bb}' + (r_{be} \parallel r_{bc}')$

$$\therefore hie = r_{bb}' + (r_{be} \parallel r_{bc}')$$

$$hie = r_{bb}' + r_{be}$$

$$\left(\because r_{bc}' \gg r_{be} \right)$$

$$\boxed{\therefore r_{bb}' = hie - r_{be}}$$

(P.T.O.)

(e)

The Output Conductance g_{ce} ($= \frac{1}{r_{ce}}$)

on Fig: 2 o/p conductance, is when s_{10} is open-circuited
(i.e. $I_b = 0$)

is defined as hoe

From Fig: 1 when $I_b = 0$

$$I_c = \frac{V_{ce}}{r_{ce}} + \frac{V_{ce}}{r_{bc} + r_{be}} + g_m V_{be}$$

but $V_{be} = \frac{V_{ce} r_{be}}{r_{bc} + r_{be}}$

and $r_{bc} \gg r_{be}$

$$\therefore I_c = \frac{V_{ce}}{r_{ce}} + \frac{V_{ce}}{r_{bc}} + \frac{g_m V_{ce} r_{be}}{r_{bc}}$$

$$\therefore \frac{I_c}{V_{ce}} = \frac{1}{r_{ce}} + \frac{1}{r_{bc}} (1 + h_{fe})$$

$$\therefore hoe = g_{ce} + g_{bc} (1 + h_{fe})$$

$$\boxed{\therefore g_{ce} = hoe - g_{bc} (1 + h_{fe})}$$

SUMMARY:

$$\textcircled{1} \quad g_m = \frac{|I_c|}{V_T}$$

$$\textcircled{2} \quad g_{be} = \frac{g_m}{h_{fe}}$$


$$\textcircled{3} \quad r_{bb} = h_{ie} - r_{be}$$

$$\textcircled{4} \quad g_{bc} = h_{re} g_{be}$$

$$\textcircled{5} \quad g_{ce} = hoe - (1 + h_{fe}) g_{bc}$$


(P.T.O.) ⑥

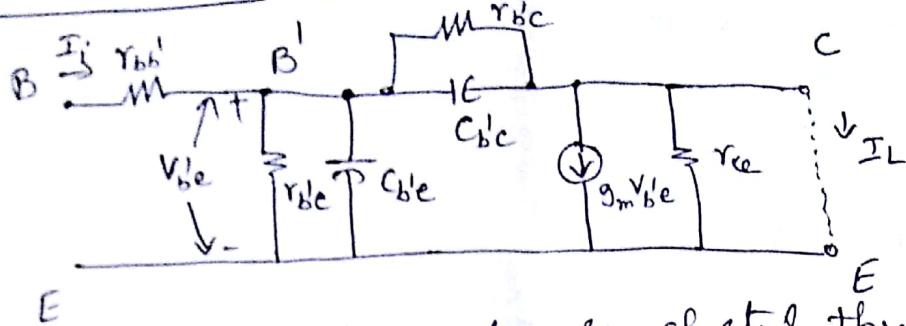③ Short circuit Current Gain at High Frequencies:



when o/p terminals are shorted then

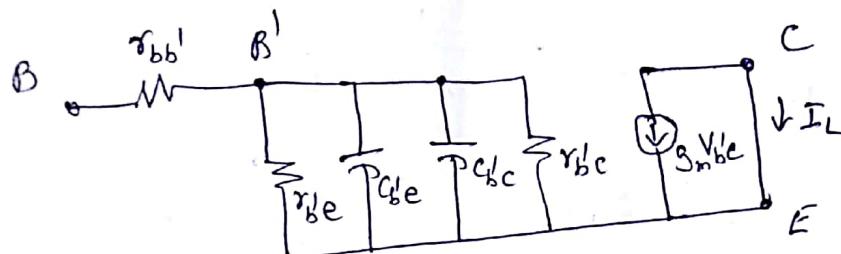
$I_L = -g_m V_{be}$
and the circuit can be represented as follows:



Since $r_{bc} \gg r_{be}$, r_{bc} can be ignored.

and $C_T = C_{be} + C_{bc} = C_e + C_c$

Now the circuit can be represented as

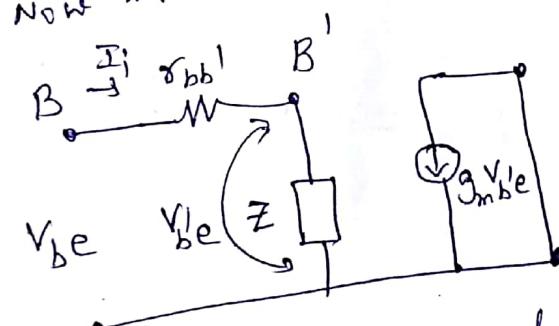

$$\therefore V_{be} = I_i Z \quad \text{where}$$

$$Z = r_{be} \parallel j \times C_T$$

$$= \frac{r_{be} \frac{1}{j \omega C_T}}{r_{be} + \frac{1}{j \omega C_T}} = \frac{r_{be}}{1 + j \omega r_{be} C_T}$$

where

$$f_H = \frac{1}{2\pi r_{be} C_T}$$

$$Z = \frac{r_{be}}{1 + j \frac{f}{f_H}} \quad (\text{P.T.O.})$$

$$\therefore I_L = -g_m V_B'e$$

$$= -g_m I_i Z$$

$$\therefore A_{ISC} = -g_m Z$$

$$= \frac{-g_m \gamma_B'e}{1 + j \frac{f}{f_H}}$$

$$|A_{ISC}| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \quad \boxed{180 - \tan^{-1}\left(\frac{f}{f_H}\right)}$$

$$\therefore A_{ISC} = \frac{-h_{fe}}{1 + j \frac{f}{f_H}}$$

$$\text{where } f_H = \frac{1}{2\pi \gamma_B'e (C_e + C_c)}$$


Mid Band Region

$$\text{at } f < f_H \Rightarrow A_{ISC} = -h_{fe} \text{ and } \varphi = 180^\circ$$

$$\text{at } f = f_H \Rightarrow A_{ISC} = \frac{-h_{fe}}{\sqrt{2}} \quad \begin{cases} \varphi = 135^\circ \\ \text{i.e., } 3 \text{ dB frequency} \end{cases}$$

$$\text{at } f > f_H \Rightarrow A_{ISC} \approx 0 \quad \begin{cases} \text{with } f_B, \text{ called as} \\ \text{this } f_H \text{ is represented} \\ \text{B - cut off frequency} \end{cases} \quad \begin{cases} \text{in CE configuration} \end{cases}$$
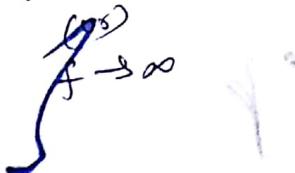
$$\text{for } f > f_H \Rightarrow A_{ISC} \approx 0 \quad \varphi = 90^\circ.$$



Band Width: The frequency range upto f_B is referred to as the band width of the ckt. (P.T.O.)

① & ⑤ Figure of Merit (f_T) or Threshold Frequency:

f_T is defined as the frequency at which the short-circuit Common Emitter Current Gains attains unity magnitude.

$$\therefore \frac{h_{FE}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} = 1$$

$$\therefore h_{FE} = 1 + \left(\frac{f}{f_H}\right)^2$$

$$\therefore \left(\frac{f}{f_H}\right)^2 = \frac{h_{FE}^2 - 1}{h_{FE}}$$

$$\left(\because h_{FE} \gg 1\right)$$

$$\boxed{\therefore f_T = f_H h_{FE}}$$

G.B.P.

this f is called as f_T
 for CE Configuration $f_H = f_\beta \therefore f_T = f_\beta^{h_{FE}}$
 for CB Configuration $f_H = f_\alpha \therefore f_T = f_\alpha^{h_{FB}}$
 for CC Configuration $f_H = f_g \therefore f_T = f_g^{h_{FC}}$

for a given transistor, hence

Note: f_T is a constant for a given transistor, hence
 $f_\alpha h_{FB} = f_\beta h_{FE} = f_g h_{FC}$. From this we can say

$$\boxed{f_\beta \approx f_T}$$

$$\therefore h_{FC} = 1 + h_{FE} \approx h_{FE}$$


$$\boxed{f_\alpha \gg f_\beta}$$

and

Large f_E makes CB as a video Amplifier.

Carry Forward
(P.T.O.)

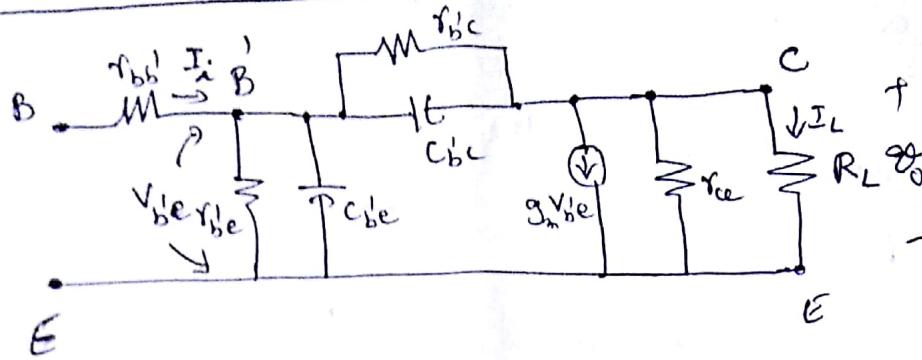⑥ Current gain at HF with load resistance (R_L):



Brought
Forward


$$\text{We know that } f_B = \frac{1}{2\pi r_{be}(C_e + C_c)}$$

$$\therefore f_T = \frac{h_{fe}}{2\pi r_{be}(C_e + C_c)}$$

$$\boxed{\therefore f_T = \frac{g_m}{2\pi C_e}}$$

$$\therefore g_m = \frac{h_{fe}}{r_{be}} \quad \text{if } C_e \gg C_c$$

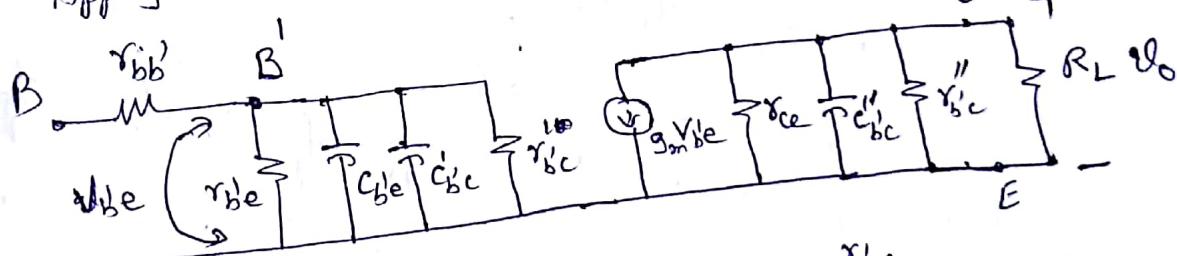Step : 2 Apply Miller's theorem on r_{bc}' and C_{bc}'



$$\text{where } C_{bc}' = C_{bc}(1 - A_v) \quad ; \quad r_{bc}'' = \frac{r_{bc}'}{1 - A_v}$$

$$C_{bc}'' = C_{bc}\left(1 - \frac{1}{A_v}\right) \quad ; \quad r_{bc}'' = \frac{r_{bc}'}{1 - \frac{1}{A_v}}$$

~~but we know~~ $A_v = \frac{a_{ce}}{r_{be}}$


~~we know that~~ $r_{bc}' > r_{be}$

$$R_L \ll r_{ce} \quad \text{and} \quad C_{bc}'' \approx 0 \quad \therefore A_v \gg 1$$

$$R_L \ll r_{bc}'' \quad \text{and hence neglected.}$$

hence neglect r_{ce} , r_{bc}'' , C_{bc}'' and r_{bc}' , then the circuit becomes

(P.T.O.)

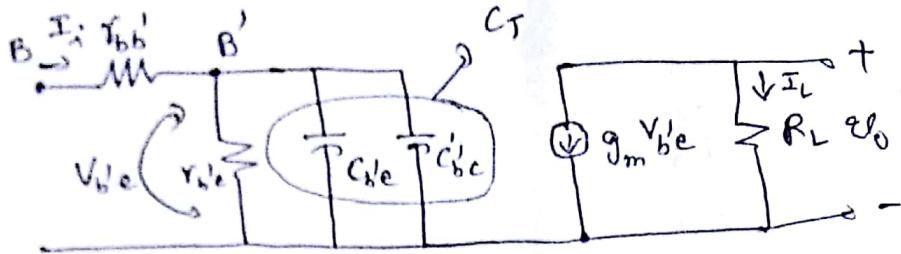


$$\therefore v_o = -g_m V'_be R_L$$

$$\therefore A_v = \frac{v_o}{V_{be}} = -g_m R_L$$

hence $C'_bc = C_{bc}(1 + g_m R_L)$ this is called Miller's capacitance.
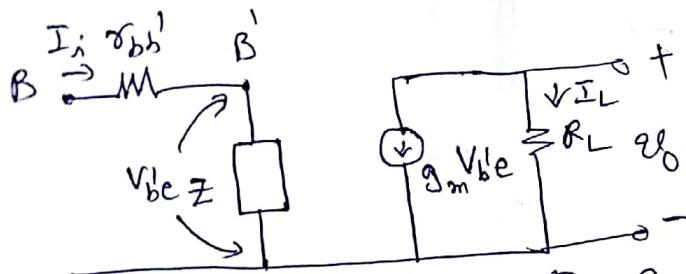
$$\therefore \text{Total input capacitance } C_T = C_{be} + C_{bc}(1 + g_m R_L) \\ = C_{be} + C_{bc}(1 + g_m R_L)$$



The current gain with R_L can be obtained as

$$A_{IHF} = \frac{I_L}{I_i} = \frac{-g_m V'_be}{\frac{V_{be}}{Z}} = -g_m Z$$

where $Z = (\gamma_{be}) || (x_{CT})$

$$= \frac{\gamma_{be} + \frac{1}{j\omega C_T}}{\gamma_{be} + \frac{1}{j\omega C_T}}$$

$$= \frac{\gamma_{be}}{1 + j\omega \gamma_{be} C_T}$$

$$Z = \frac{\gamma_{be}}{1 + j \left(\frac{f_H}{f_M} \right)}$$

where $f_H = \frac{1}{2\pi \gamma_{be} C_T}$

(P.T.O.)

$$\begin{aligned} \therefore A_{IHF} &= -g_m Z \\ &= -\frac{g_m r_{be}}{1 + j \left(\frac{f}{f_H} \right)} \\ A_{IHF} &= \frac{-h_{fe}}{1 + j \left(\frac{f}{f_H} \right)} \end{aligned}$$

where $f_H = \frac{1}{2\pi r_{be} C_T}$

it can be observed that $f_H < f_\beta$

$$f_\beta = \frac{1}{2\pi r_{be} (C_e + C_C)}$$

Grain Band Width Product:

(a) $|G_{BP}| = |A_{mid}| \times BW$

$$A_{mid} = -h_{fe}$$

$$BW = f_H = \frac{1}{2\pi r_{be} C_T}$$

$$\therefore |G_{BP}| = \frac{h_{fe}}{2\pi r_{be} C_T} = \frac{g_m}{2\pi C_T}$$

including R_L $|G_{BP}| = \frac{g_m R_L}{2\pi C_T (R_L + r_{bb}')$

(b) $\frac{\text{Voltage } G_{BP}}{|G_{BP}|} = |A_{mid}| \times BW$

$$A_{mid} = -h_{fe} \times \frac{R_L}{R_L + r_{bb}'}$$

(including R_S)

$$\therefore |G_{BP}| = \frac{h_{fe}}{2\pi r_{be} C_T} \times \frac{R_L}{(R_L + r_{bb}')}$$

$$|G_{BP}| = \frac{g_m}{2\pi C_T} \times \frac{R_L}{R_L + r_{bb}'}$$

(P.T.O.) → 9

Problems From Unit-II.

- (a) For an amplifier mid band gain is 100 and lower cut off frequency is 1KHz. (b) Find the gain of the amplifier at 20Hz
 (b) Find the frequency at which the gain is 10% smaller than its mid band gain.

Sol: given data $A_{mid} = 100$; $f_L = 1\text{KHz}$
 (b) calculate gain at $f = 20\text{Hz}$ i.e. $A_v = ?$ at $f = 20\text{Hz}$

$$\text{we know } \left| A_v \right| = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_L} \right)^2}} \quad \left[180 + \tan^{-1} \left(\frac{f}{f_L} \right) \right]$$

$$\therefore A_v = \frac{100}{\sqrt{1 + \left(\frac{1000}{20} \right)^2}} \quad \left[180 + \tan^{-1}(50) \right]$$

$$= 2 \quad \left[180 + 88.85^\circ \right]$$

$$\boxed{\therefore A_v = 2 \quad \left[268.85^\circ \right]}$$

$$(b) \text{ calculate } f = ? \text{ at which } A_v = \left[A_{mid} - \cancel{A_{mid}} \times \frac{10}{100} \times 100 \right]$$

$$A_v = 90$$

we know

$$A_v = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f} \right)^2}}$$

$$\therefore \left(1 + \left(\frac{f_L}{f} \right)^2 \right) = \left(\frac{A_{mid}}{A_v} \right)^2 = \frac{100}{90} = \left(\frac{10}{9} \right)^2$$

$$\therefore \left(\frac{f_L}{f} \right)^2 = \frac{100-81}{81} = \frac{19}{81} \quad \therefore \frac{f_L}{f} = \frac{4.36}{9}$$

$$\therefore f = \cancel{f_L} \times \frac{9}{4.36} \times f_L = \underline{\underline{2.065\text{KHz}}} \quad (\text{P.T.O.})$$

- ② The 3dB gain of an amplifier is given as 200 and the higher cut-off frequency is 20 kHz. Find the gain of the amplifier at $f = 100 \text{ kHz}$.

Sol: Given data $A_{VHF}|_{3\text{dB}} = 200$
 $f_H = 20 \text{ kHz}$

Determine $A_{VHF}|_f = 100 \text{ kHz}$

We know

$$A_{VHF} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$\text{at } f = f_H \Rightarrow A_{VHF} = 200$$

$$\therefore A_{mid} = A_{VHF}|_{3\text{dB}} \times \sqrt{2}$$

$$= 200 \times 1.414$$

$$A_{mid} = 282.4$$

$$\therefore A_{VHF} = \frac{282.4}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$\therefore \text{at } f = 100 \text{ kHz}$$

$$A_{VHF} = \frac{282.4}{\sqrt{1 + \left(\frac{100 \text{ K}}{20 \text{ K}}\right)^2}} = \frac{282.4}{\sqrt{26}}$$

$$\boxed{\therefore A_{VHF}|_{100\text{K}} = 55.46}$$

(P.T.O.)

- ③ At $I_C = 1 \text{ mA}$ and $V_{CE} = 10 \text{ V}$ a certain transistor data shows $C_{bc}' = 3 \text{ pF}$, $h_{fe} = 200$ and $\omega_T = 50 \text{ M rad/sec}$. Calculate g_m , r_{be} , C_{be}' and $\omega_B(f_B)$.

Sol: Given data $I_C = 1 \text{ mA}$, $V_{CE} = 10 \text{ V} (\text{not useful})$

$$C_{bc}' = 3 \text{ pF}, h_{fe} = 200 \text{ and } \omega_T = 50 \text{ M rad/sec}$$

$$\therefore f_T = \frac{50}{2\pi} \text{ MHz.}$$

We know that

$$g_m = \frac{|I_C|}{V_T} \quad \text{where } V_T = \frac{T}{11,600} \text{ at room temp.}$$

$$V_T = 26 \text{ mV.}$$

$$\therefore g_m = \frac{1 \text{ mA}}{26 \text{ mV}}$$

$$= \frac{1}{26} \approx$$

$$g_m = 38.46 \text{ mV}$$

$$f_B = \frac{f_T}{h_{fe}}$$

$$\therefore \omega_B = \frac{\omega_T}{h_{fe}}$$
 ~~$= \frac{50}{200} \text{ M rad/sec}$~~
 ~~$= 0.25 \text{ M rad/sec}$~~

$$\omega_B = 250 \text{ rad/sec}$$

$$f_B = \frac{1}{2\pi r_{be}(C_{be} + C_{bc}')}}$$

$$= 2.5 \text{ M rad/sec}$$

We know that

$$r_{be} = \frac{h_{fe}}{g_m} = \frac{200}{38.46} \text{ k}\Omega$$

$$r_{be} = 5.2 \text{ k}\Omega$$

$$\therefore C_{be} = 77.92 - 3$$

$$\underline{\underline{C_{be} = 74.92 \text{ pF.}}}$$

$$f_T = \frac{h_{fe}}{2\pi r_{be}(C_{be} + C_{bc}')}$$

$$\therefore (C_{be} + C_{bc}') = \frac{h_{fe}}{2\pi r_{be} f_T}$$

$$= \frac{h_{fe}}{2\pi \times 5.2 \times 10^3 \times \frac{50}{2\pi} \times 10^6}$$

$$= \frac{200}{260 \times 10^9} = 779.7 \text{ pF.}$$

$$= 3.846 \text{ pF} \rightarrow 200$$

(P.T.O.)

- Q) short circuit CE current gain of transistor is 25 at a frequency of 2 MHz . If $f_B = 200 \text{ kHz}$, calculate
 i) f_T , ii) h_{FE} , iii) A_I at $f = 10 \text{ MHz}$ and 100 MHz .

Sol: We know that CE short circuit current gain at HF is given by

$$|A_{VSC}| = \frac{+h_{FE}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \quad \text{here } f_H = f_B.$$

given data; $A_{VSC} = 25$, $f = 2 \text{ MHz}$ & $f_B = 200 \text{ kHz}$

$$(i) \therefore h_{FE} = |A_{VSC}| \sqrt{1 + \left(\frac{f}{f_H}\right)^2}$$

$$= 25 \times 10$$

$$(ii) h_{FE} = 250$$

$$(ii) \therefore f_T \approx f_B \quad h_{FE} = 250 \times 200 \text{ kHz} \\ = 500 \text{ MHz.}$$

(iii) A_I at $f = 10 \text{ MHz}$ is

$$A_I|_{10 \text{ MHz}} = \frac{h_{FE} 250 \times 10^6}{\sqrt{1 + \left(\frac{10 \times 10^6}{200 \times 10^3}\right)^2}} \approx \frac{250}{\sqrt{(50)^2}}$$

$$\underline{A_I = 0.5}$$

A_I at $f = 100 \text{ MHz}$

$$A_I|_{100 \text{ MHz}} = \frac{250}{\sqrt{1 + \left(\frac{100 \times 10^6}{200 \times 10^3}\right)^2}} = \frac{250}{500}$$

$$\underline{A_I|_{100 \text{ MHz}} = 0.5}$$

(P.T.O.)

5

A BJT has the following parameters measured at $I_C = 10mA$,
 $h_{ie} = 3k\Omega$, $h_{fe} = 100$, $f_T = 4MHz$, $C_C = 2pF$ & $C_E = 18pF$.
Find r_{be} , $r_{bb'}$, g_m , f_H for $R_L = 1k\Omega$.

Sol: we know that where $V_T = 26mV$ at Room Temp.

$$\text{i)} \quad g_m = \frac{|I_C|}{V_T}$$

$$\therefore g_m = \frac{1 \times 10^{-3}}{26 \times 10^3}$$

$$= 0.0385 \text{ mV}$$

$$\boxed{\therefore g_m = 38.5 \text{ mV}}$$

ii) we know

$$r_{be} = \frac{h_{fe}}{g_m} = \frac{100}{38.5 \times 10^3} = 2600 \Omega$$

$$\boxed{r_{be} = 2.6 k\Omega}$$

iii) we know that

$$r_{bb'} = h_{ie} - r_{be}$$

$$= 3000 - 2600$$

$$\boxed{\therefore r_{bb'} = 400 \Omega}$$

iv) we know that

$$f_H = \frac{1}{2 \pi r_{be} C_T}$$

where C_T is the ~~Miller's~~ capacitance given by

$$C_T = C_{be} + C_{bc}(1 + g_m R_L)$$

$$= 18pF + 2pF \left(1 + \frac{38.5}{39.5} \right)$$

$$= 18 + 7.079$$

$$\therefore C_T = 97 pF$$


(P.T.O.)

$$\therefore f_H = \frac{1}{2\pi \times 2.6 \times 10^3 \times 97 \times 10^{-12}} \text{ Hz}$$


$$= \frac{10^9}{2\pi \times 2.6 \times 97}$$

$\therefore f_H = 631 \text{ kHz}$

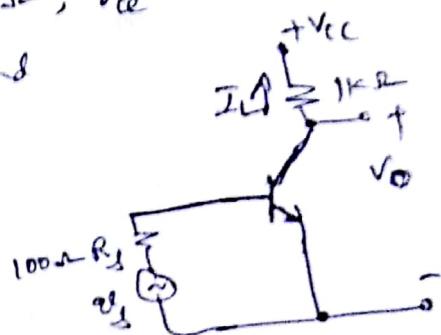
- ⑥ The Hybrid- π parameters of the transistor used in the circuit shown are $I_{m0} = 50 \text{ mA/V}$, $r_{be} = 1 \text{ k}\Omega$, $r'_{bc} = 4 \text{ M}\Omega$, $r_{ce} = 80 \text{ k}\Omega$, $C_c = 3 \text{ pF}$, $C_e = 100 \text{ pF}$ and $r_{bb} = 100 \text{ }\Omega$, find
 i) Upper 3dB frequency of A_I
 ii) the voltage gain A_v at midband



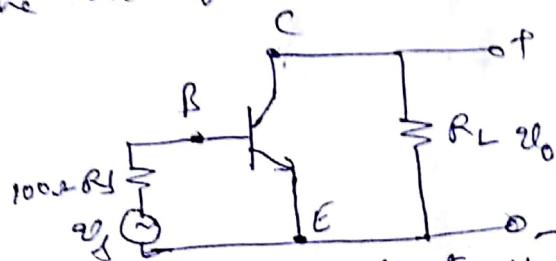Sol: The ac equivalent circuit is obtained as



Replace BJT with its Hybrid- π model

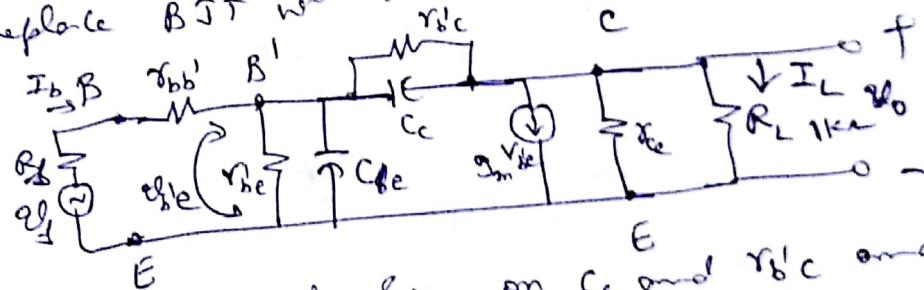

Apply Miller theorem on C_c and r'_{bc} and then neglect r_{ce} , r'_{bc} because $r_{ce} \gg R_L$ and $r'_{bc} \gg R_L$ on o/p side. On o/p side neglect r'_{bc} as

$$\frac{1}{r'_{bc}} \gg \frac{1}{r_{be}} \text{ and } C_i = C_e + C_c(1 + g_m R_L)$$


$$= 100 + 3(1 + 51)$$

$$= 100 + 156$$

$$C_i = 256 \text{ pF}$$

(P.T.O.)

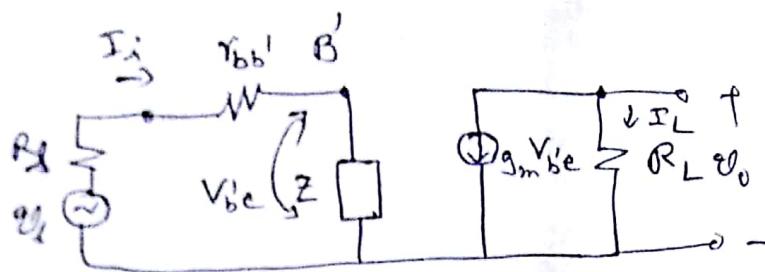The simplified equivalent circuit becomes



where C_c is neglected and

$$Z = r_{be} \parallel X_{ci}$$

$$= \frac{r_{be}}{r_{be} + \frac{1}{j\omega C_i}}$$

$$= \frac{r_{be}}{1 + j\omega r_{be} C_i}$$

$$\therefore Z = \frac{r_{be}}{1 + j\frac{f}{f_H}}$$

$$\text{where } f_H = \frac{1}{2\pi r_{be} C_i}$$

$$\therefore A_I = \frac{I_L}{I_i} = \frac{-B_m V_{be}}{I_i} = \frac{-B_m Z}{f_H} = -B_m Z$$

$$\therefore A_I = \frac{-B_m r_{be}}{1 + j\left(\frac{f}{f_H}\right)} = \frac{-h_{fe}}{1 + j\frac{f}{f_H}}$$

$$\text{where } f_H = \frac{1}{2\pi r_{be} C_i}$$

$$\therefore f_H = \frac{1}{2\pi \times 1 \times 10^3 \times 256 \times 10^{-12}}$$

$$= \frac{10^9}{2\pi \times 256} \text{ Hz}$$

$\therefore f_H = 621.7 \text{ kHz}$

(P.T.O.)

iii) The voltage gain A_{VS} is given by

$$A_{VS} = \frac{V_O}{V_S} = \frac{-g_m V_B e R_L}{R_S}$$

$$A_{VS} = \frac{-g_m I_f R_L}{I_f (1.2) \times 10^3} = \frac{-50 \times 10^3 \times 10^3}{1.2 \times 10^3} = -41.667$$

Write KVL to 2dp loop

$$V_S - I_A (100 + \frac{r_b'}{Z} + r_{bb'}) = 0$$

$$\therefore V_S = I_A (200 + \frac{1}{Z}) = 1.2 I_A \times 10^3$$

$$\therefore A_{VS} = \frac{-g_m I_f Z R_L}{R_f I_f (200 + Z)} = \frac{-g_m R_L}{1 + \frac{200}{Z}} = \frac{-g_m R_L}{1 + \frac{200}{r_b' e}} = \frac{-g_m R_L}{200 (1 + j \frac{f}{f_H})} = \frac{-g_m R_L}{r_b' e}$$

$$A_{VS} = \frac{-g_m R_L}{\sqrt{1 + (\frac{200}{Z})^2}}$$

$$|Z| = \frac{r_b' e}{\sqrt{2}} = 1k$$

$$\therefore A_{VS} = \frac{-g_m R_L}{\sqrt{1 + \left(\frac{200 \times 50}{1 \times 10^3}\right)^2}} = \frac{-50}{\sqrt{1 + 0.16}} = -50$$

$$\begin{aligned} & 2+2 \\ & (0.4)^2 \\ & 0.16 \end{aligned}$$

$$A_{VS} = \frac{-g_m R_L}{1 + 0.2 + j \frac{0.2 f}{f_H}}$$

$$A_{VS} = \frac{-50}{1.2 + j \frac{0.2 f}{f_H}}$$

$$\therefore A_{VS \text{ mid}} = \frac{+50}{1.2} = 41.67$$

$$A_{VS \text{ 3dB}} = 41.10$$


Cascading of Amplifiers:

- 1) Overall gain expression (Linear and in dB)
- 2) Effect of cascading, ~~n~~-stages, on f_L
- 3) Effect of cascading, n-stages, on f_H
- 4) Effect of cascading on BW

Gain of n-stage cascaded amplifier:

Assumptions made:

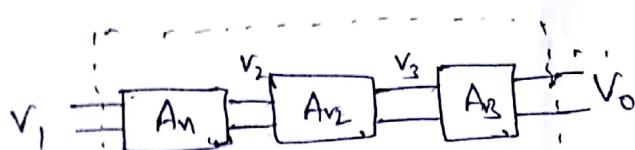- ① All individual stages are identical
- ② All stages are non-interacting stages



The overall voltage gain A_v is given by,

$$A_v = \frac{V_0}{V_1} = \frac{V_0}{V_3} \times \frac{V_3}{V_2} \times \frac{V_2}{V_1}$$

$\therefore A_v = A_{v1} \times A_{v2} \times A_{v3}$

If it is converted into dB scale

$$20 \log_{10} A_v = 20 \log_{10} A_{v1} + 20 \log_{10} A_{v2} + 20 \log_{10} A_{v3} \dots$$

The overall gain is the sum of individual gains

in dB.

$f_L = f_{L1}$

Adapted from



(P.T.O.)

② Effect of Cas Coding on f_L .

We know the gain of n -stage cascade comp is given by

$$A_v = A_{v1} \times A_{v2} \times A_{v3} \dots \text{ } n \text{ stages}$$

assume that all stages identical

$$\therefore A_v = A_{v1}$$

but we know at low frequencies

$$|A_v| = \sqrt{\frac{A_{mid}}{1 + j \frac{f_L}{f}}} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$\therefore A_{v\otimes} = \left[\frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} \right]^n$$

the lower 3dB frequency f_L^* is defined as the frequency at which the ~~the~~ gain reduced by $\frac{1}{\sqrt{2}}$ times of its maximum gain i.e. A_{mid}

$$\therefore \left[\frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f_L^*}\right)^2}} \right]^n = \frac{[A_{mid}]^n}{\sqrt{2}}$$


$$\therefore \left[1 + \left(\frac{f_L}{f_L^*} \right)^2 \right]^{\frac{n}{2}} = 2^{1/2}$$

$$\therefore 1 + \left(\frac{f_L}{f_L^*} \right)^2 = 2^{\frac{1}{n}}$$

$$\therefore \frac{f_L}{f_L^*} = \sqrt{2^{\frac{1}{n}} - 1}$$

$$\therefore f_L^* = \frac{f_L}{\sqrt{2^{\frac{1}{n}} - 1}}$$

for $n=1$, $f_L^* = f_L$.

for any higher value of n ,

$f_L^* > f_L$

③ Effect of cascading on f_H :

The overall voltage gain of n-stage amplifier is

$A_v = A_{v1}^n$

At high frequencies we know that

$$|A_{v1}| = \left| \frac{A_{mid}}{1 + j \frac{f}{f_H}} \right| = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

∴ for n-stages

$$A_v = \left[\frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \right]^n$$

The upper 3dB frequency f_H^* for of the n-stage amplifier is defined as the frequency at which the gain reduces by $\sqrt{2}$ times of its mid band gains.

$$\therefore \left[\frac{A_{mid}}{\sqrt{1 + \left(\frac{f_H^*}{f_H}\right)^2}} \right]^n = \frac{A_{mid}}{\sqrt{2}}$$

$$\therefore 1 + \left(\frac{f_H^*}{f_H} \right)^2 = 2^{1/n}$$

$$\therefore \frac{f_H^*}{f_H} = \sqrt{2^{1/n}-1}$$

$$\therefore f_H^* = f_H \left(\sqrt{2^{1/n}-1} \right)$$

$$\text{for } n=1 \Rightarrow f_H^* = f_H : \text{for } n>1 \quad f_H^* \ll f_H$$

(P.T.O.)

(A) Effect of cascading on B.W:

We know that f_L^* and f_H^* are given by

$$f_L^* = \frac{f_L}{\sqrt{2^{1/n}-1}} \quad \text{and} \quad f_H^* = f_H \sqrt{2^{1/n}-1}$$

for $n > 1$,

$$f_L^* > f \quad \text{and} \quad f_H^* < f_H$$

Therefore

$$\text{B.W.}_{\text{n-stage}} = f_H^* - f_L^*$$

$$= f_H \sqrt{2^{1/n}-1} - \frac{f_L}{\sqrt{2^{1/n}-1}}$$


$$\approx f_H \sqrt{2^{1/n}-1}$$

$$\therefore \text{B.W.}_{\text{n-stage}} = \text{B.W.}_{\text{single stage}} \times \sqrt{2^{1/n}-1}$$

for $n > 1$; $\sqrt{2^{1/n}-1} < 1$

$$\therefore \text{B.W.}_{\text{n-stage}} < \text{B.W.}_{\text{single stage}}$$
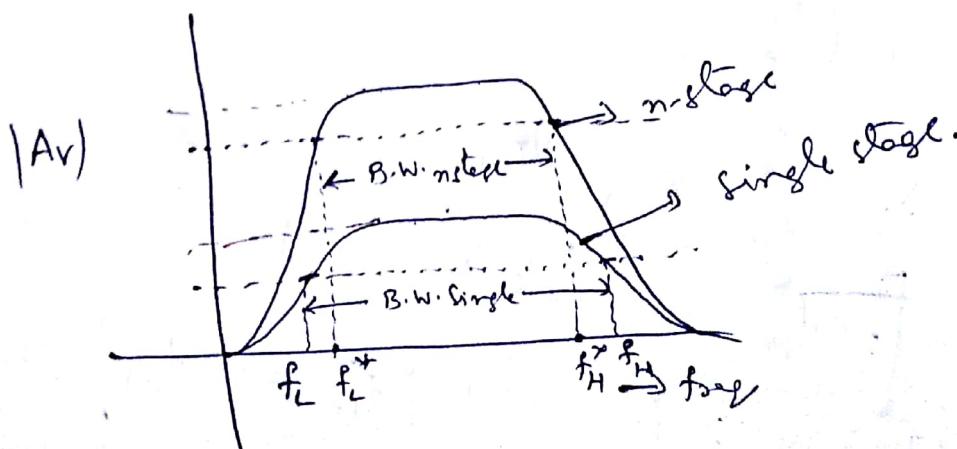
$$\therefore \text{B.W.}_{\text{n-stage}} = f_H \sqrt{2^{1/n}-1}$$



Problem

- ① For an amplifier mid band gain is 100 and lower cut-off frequency is 1kHz. Find
 a) gain at $f = 20\text{Hz}$
 b) midband gain and f_L^* if three such stages are cascaded.

Sol: given that
 $A_{\text{mid}} = 100$ and $f_L = 1\text{kHz}$

② we know that

$$|A_{\text{VLF}}| = \frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$\therefore A_{\text{VLF}} \Big|_{f=20\text{Hz}} = \frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{1 \times 10^3}{20}\right)^2}} = \frac{100}{\sqrt{2501}}$$

$$\therefore A_{\text{VLF}} \Big|_{20\text{Hz}} \approx 2$$

③ when 3 stages are cascaded the overall gain is given by

$$A_{\text{VLF}} \Big|_{n=3} = \left[\frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{f_L^*}{f}\right)^2}} \right]^3 = A_{\text{mid}}^3$$

$$\therefore A_{\text{VLF}} \Big|_{n=3} = \frac{100 \times 100 \times 100}{6} = 10$$

we know that

$$f_L^* = \frac{f_L}{\sqrt{\frac{n}{2}-1}} = \frac{1000}{\sqrt{\frac{3}{2}-1}} \text{ Hz}$$

$$\underline{f_L^* = 1.962 \text{ kHz}}$$

(P.T.O.)

Q) For an amplifier, the upper dB frequency is given as 20 kHz and the gain at this frequency is 200. Find

a) The gain at $f = 100 \text{ kHz}$

b) If n such stages are cascaded determine the maximum gain and upper 3 dB frequency.

Sol: a) It is given. $f_H = 20 \text{ kHz}$ and $A_v|_{f_H} = 200$

We know that

$$A_{VHF} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

at 3 dB frequency

$$A_v = \frac{A_{mid}}{\sqrt{2}} = 200$$

$$\therefore A_{mid} = \sqrt{2} \times 200$$

$$\underline{A_{mid} = 282.8}$$

$$\therefore A_{VHF} = \frac{282.8}{\sqrt{1 + \left(\frac{f}{20 \times 10^3}\right)^2}}$$

$$\therefore A_{VHF}|_{f=100 \text{ k}} = \frac{282.8}{\sqrt{1 + \left(\frac{100 \text{ k}}{20 \text{ k}}\right)^2}} \\ = \frac{282.8}{\sqrt{26}}$$

$\therefore A_v|_{f=100 \text{ k}} = 55.46$

(P.T.O.)

(b) when 2 stages are cascaded

$$A_v|_{n=2} = A_{mid}$$

$$= (2.82, 8)^2$$

$$A_v|_{n=2} = 79975.84$$

$$A_v|_{n=2 \text{ in dB}} = 98.06 \text{ dB}$$

we know

$$f_H^* = f_H \left(\sqrt{2^{1/n-1}} \right)$$

$$= 20 \times 10^3 \left(\sqrt{2^{1/2}-1} \right) \text{ Hz}$$

$$\therefore f_H^* = 12.87 \text{ kHz}$$

(3) if 4 identical amplifiers are cascaded each having $f_L = 100 \text{ Hz}$, determine the overall lower 3dB frequency f_L^*

Sol: given $f_L = 100 \text{ Hz}$, $n = 4$, we know

$$f_L^* = \frac{f_L}{\sqrt{2^{1/n-1}}} = \frac{100}{\sqrt{2^{1/4}-1}} = 229.9 \text{ Hz}$$

(4) if 4 identical amplifiers are cascaded each having $f_H = 100 \text{ kHz}$, determine the overall upper 3dB frequency f_H^* .


Sol: given $f_H = 100 \text{ kHz}$, $n = 4$ we know

$$f_H^* = f_H \left(\sqrt{2^{1/n-1}} \right) = 100 \times \left(\sqrt{2^{1/4}-1} \right) \text{ kHz}$$

$$\therefore f_H^* = 43.5 \text{ kHz}$$


SINGLE STAGE CE AMPLIFIER RESPONSE:

CE amplifier circuit is as shown below

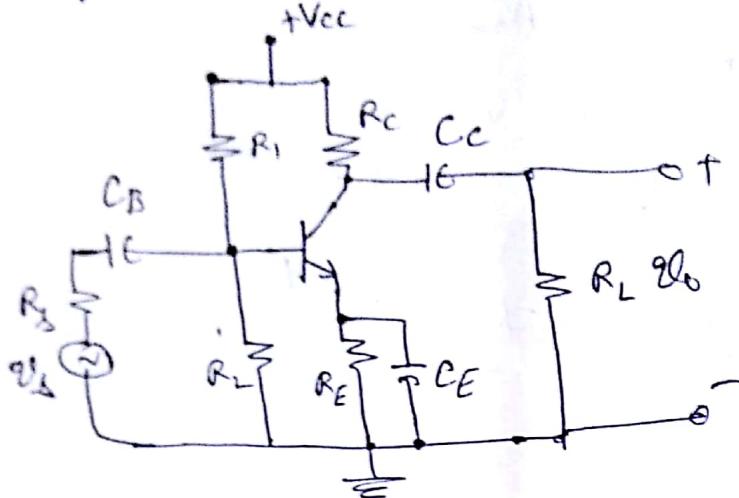

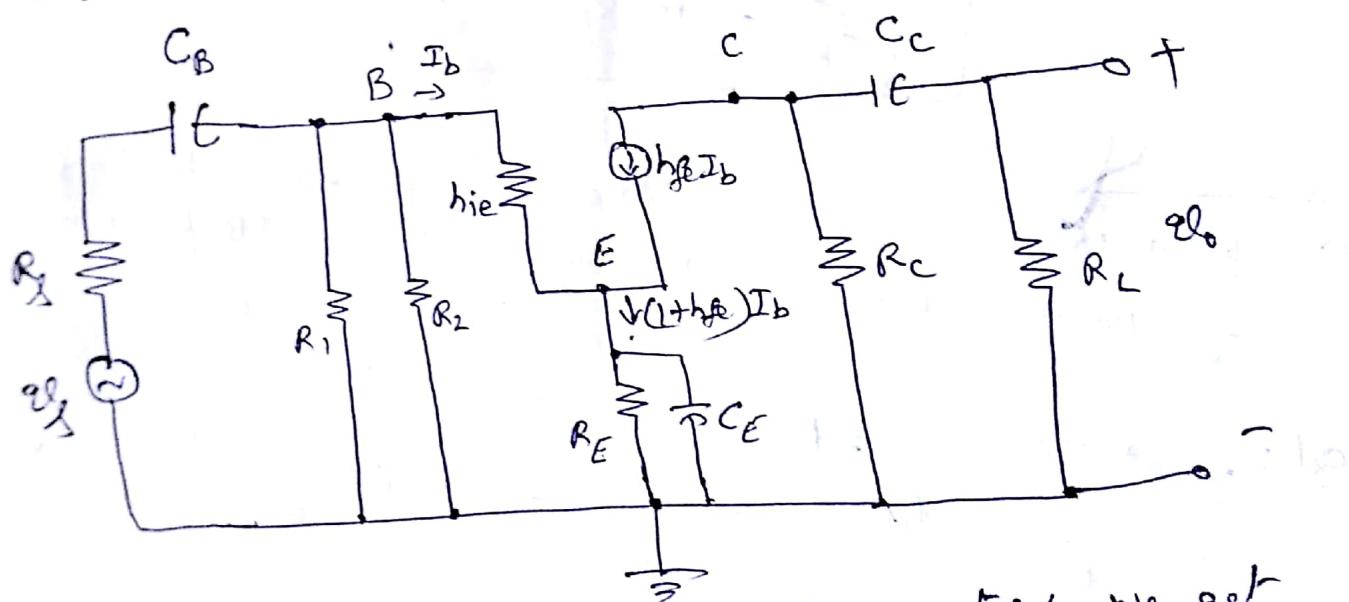a) Low Frequency Analysis:

The one equivalent circuit using approximate ~~h~~ h parameters model, by considering all external capacitances is given below



Since there are 3 external capacitors we get 3 time constant and hence 3 cut off frequencies in Low Frequency region. Each cut off frequency can be exactly obtained as follows:

① Cut off frequency due to \$C_B\$

(P90.)

17


Note: while Considering one, other two capacitances are to be short circuited.

① Considering C_B alone:

the Time Constant τ for an RC circuit is given by the product of RC and the cut off frequency is given by

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}$$

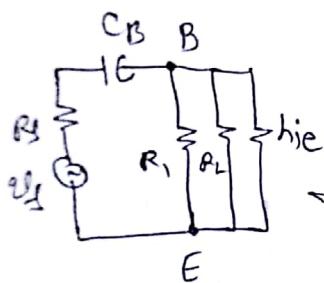while
 C \rightarrow The capacitor under consideration
 R \rightarrow the equivalent resistance associated with that capacitor C. (the resistance seen by the capacitor)



Therefore

$$f_{CB} = \frac{1}{2\pi R_1 C_B}$$

Note: R₁ can be obtained by setting $h_{fe} = \infty$.


where $R_1 = R_S + (R_1 || R_2 || h_{ie})$

if $R_1 > h_{ie}$ and $R_2 > h_{ie}$ then

$$R_1 = R_S + h_{ie}$$

$$\therefore f_{CB} = \frac{1}{2\pi(R_S + h_{ie}) C_B}$$

$$\textcircled{1} \quad \frac{1}{C}$$

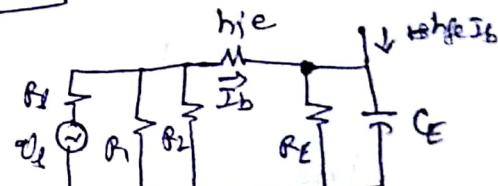

② Considering C_E alone:

$$f_{CE} = \frac{1}{2\pi R_2 C_E}$$

where

$$R_2 = R_E || \left[\frac{h_{ie} + (R_1 || R_2 || R_S)}{(1+h_{fe})} \right]$$

(P.T.O.)

if $R_1 > R_S$, $R_2 > R_S$ then

$$R_1 \parallel R_2 \parallel R_S = R_S$$

$$\therefore R_2 = R_E \parallel \left(\frac{R_S + h_{ie}}{1+h_{fe}} \right)$$

$$\text{if } R_E \gg \left(\frac{R_S + h_{ie}}{1+h_{fe}} \right)$$

$\therefore h_{fe}$ very large.

then

$$R_2 \approx \frac{R_S + h_{ie}}{1+h_{fe}}$$


$$\therefore f_{CE} = \frac{1}{2\pi \frac{(R_S + h_{ie}) \cdot C_E}{1+h_{fe}}}$$

$$\therefore f_{CE} = \frac{1+h_{fe}}{2\pi (R_S + h_{ie}) C_E}$$

— (2)

(3) Considering C_C alone:


$$f_{CC} = \frac{1}{2\pi R_3 C_C}$$

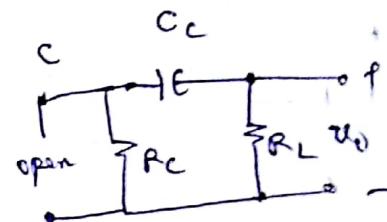

while $R_3 = R_C + R_L$

$$\therefore f_{CC} = \frac{1}{2\pi (R_C + R_L) C_C}$$


— (3)

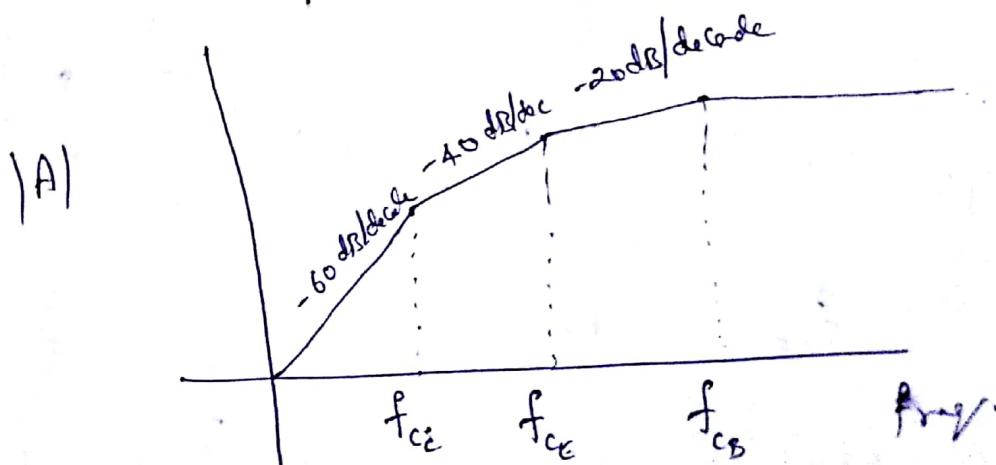

(P.T.O.)

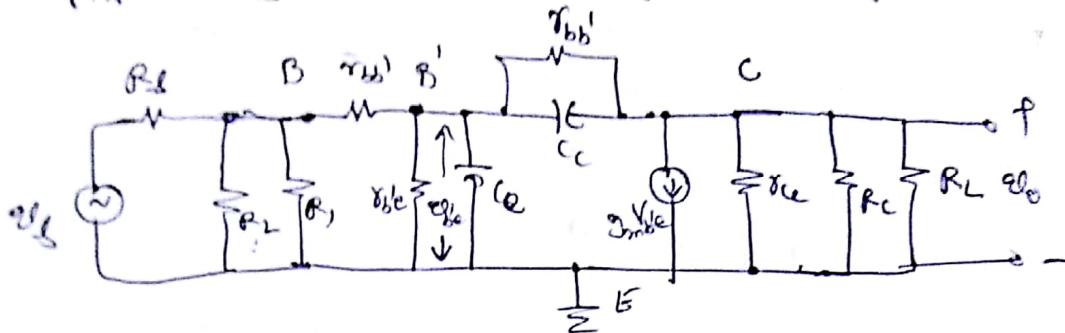(b) High Frequency Analysis:

The AC equivalent circuit using Hybrid-II model by shorting all external capacitances.




Applying Miller's Theorem on r_{bb}' & C_c results in

$$\frac{1}{r_{bb}'} = \frac{r_{bb}'}{1-Av} \quad \times \quad r_{bb}'' = \frac{r_{bb}'}{1 - \frac{1}{Av}}$$

$$c'_c = c_c(1-Av) \quad \times \quad c''_c = c_c\left(1 - \frac{1}{Av}\right)$$

The equivalent circuit now becomes

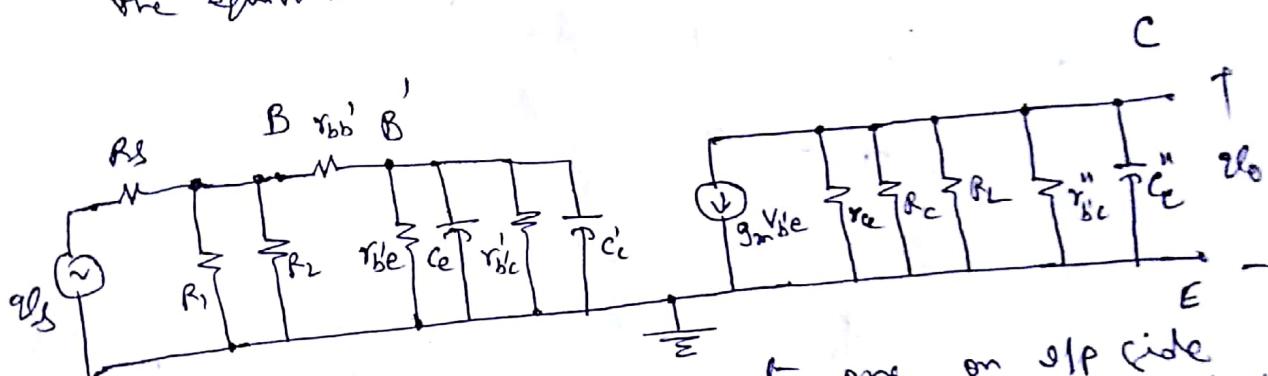

This circuit has 2 RC parts one on o/p side and other on o/p side. So we get 2 cut off frequencies in High frequency region.

Considering the o/p RC network;

$$f_{(o/p)C_i} = \frac{1}{2\pi R_{in} C_i} ; \quad r'_i = R_{in} C_i$$

$$\text{where } C_i = C_c + c_c(1-Av)$$

$$C_i = C_c + c_c(1+g_m R'_L)$$

$$\text{where } R'_L = r_{ce} || R_c || R_L || r'_{bc} . \quad (\text{P.T.O.})$$

and

$$R_{in} = r_{be} \parallel r'_{bc} \parallel \left[r_{bb}' + (R_s \parallel R_1 \parallel R_2) \right]$$

$$\therefore f_{ci} \approx \frac{1}{2\pi R_{in} C_i} \quad - \textcircled{A}$$

(b) Considering o/p network.

$$f_{co} = \frac{1}{2\pi R_o C_o} ; \gamma_o = R_o C_o$$

$$\text{where } C_o = C_c = C_c \left(\frac{1 + g_m R_L}{g_m} \right)$$

$$R_o = r_{ce} \parallel R_C \parallel R_L \parallel r'_{bc}$$


By considering the typical values

$$\gamma_o \gg \gamma_i$$

Therefore

$$f_{ci} \ll f_{co}$$

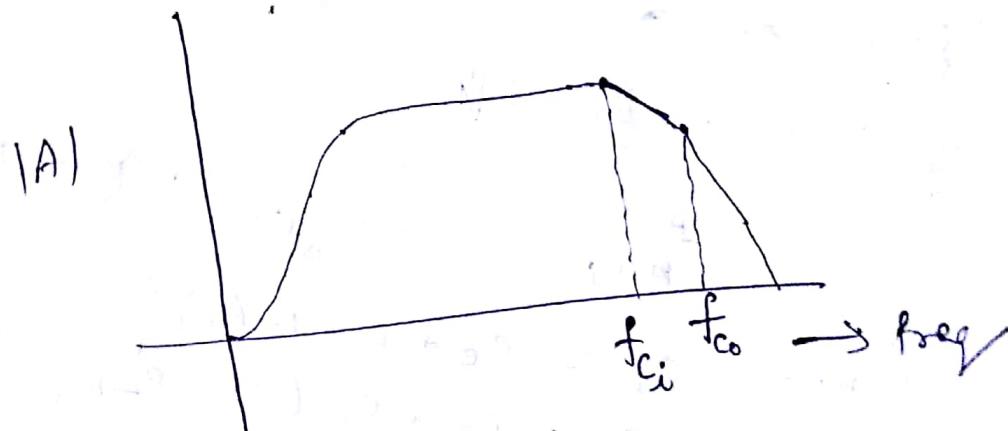Hence the High frequency response is mainly decided by f_{ci} alone.



(P.T.O.)

(19)

Logarithmic scale for Expressing gains:

① In most of the cases, used in practice, the gain is a very large number. So, it is difficult to represent & reproduce. Hence logarithmic scale is used to express gains in Engineering applications.

Very large numbers can be represented as
Very large numbers in log scale.
Small numbers in log scale.

③ Example:

Linear Ratio/no.	\log_{10} (no.)	Value
1	$\log_{10} 1 = 0$	
10	$\log_{10} 10 = 1$	
100	$\log_{10} 100 = 2$	
1000	$\log_{10} 1000 = 3$	
:	⋮	⋮
1000000	$\log_{10} 10^6 = 6$	6

check for every 10 times linear value only one increment is there in \log_{10} scale with base 10.

— So, logarithmic scales are very useful in expressing gains (or) any ratios.

(P.T.O.)

Decibel dB

- ① 'Bel' is defined from the Telephone inventor, Alexander Graham Bell. The unit 'Bel' is defined relating two power levels P_1 and P_2 as

$$G_B = \log_{10} \left(\frac{P_2}{P_1} \right) \text{ Bel}$$

- ② But, in practice, it was found that Bel is a very large unit for measurement. Hence "decibel" (dB) is defined where

$$\boxed{10 \text{ decibels} = 1 \text{ Bel}}$$

$$\therefore G_{dB} = 10 \log_{10} \left(\frac{P_2}{P_1} \right) \text{ dB}$$

where P_2 & P_1 are the output and I/P powers of a given circuit.

- ③ Often we express gain as a ratio of voltage or current.
- ④ Often the input power is normalized/standardized or kept constant at 1 milliwatt then the gain is represented as dBm

$$\therefore G_{dBm} = 10 \log \left(\frac{P_2}{1mW} \right) \text{ dBm}$$

- ⑤ If the gain is expressed in terms of voltage or current

$$G_{dB} = 10 \log \left(\frac{V_o^2 / R_o}{V_i^2 / R_i} \right) \text{ dB}$$

when it is set ~~A~~,
 $R_i = R_o = \text{units}$

$$\boxed{G_{dB} = 20 \log \left(\frac{V_o}{V_i} \right) \text{ dB} \text{ or } = 20 \log \left(\frac{I_o}{I_i} \right) \text{ dB}}$$

For n -stage cascaded amplifier the gains in dB is as below

$$\text{Av} = \text{Av}_1 \times \text{Av}_2 \times \text{Av}_3 \times \dots \times \text{Av}_n$$

$$\therefore 20 \log_{10} \text{Av} = 20 \log_{10} \text{Av}_1 + 20 \log_{10} \text{Av}_2 + \dots + 20 \log_{10} \text{Av}_n$$

$\therefore T_{dB}$ is sum of all gains in dB.


if $\text{Av} = 1$ then

$$20 \log_{10} 1 = 0 \text{ dB}$$

if $\text{Av} = 0.1$ i.e. $V_o = 0.1 \times V_i$ means o/p is smaller than input such a ckt is called as an attenuator, then the gain dB is

$$20 \log_{10} \text{Av} = 20 \log_{10} 0.1 = -1 \text{ dB}$$

the gain in dB is negative

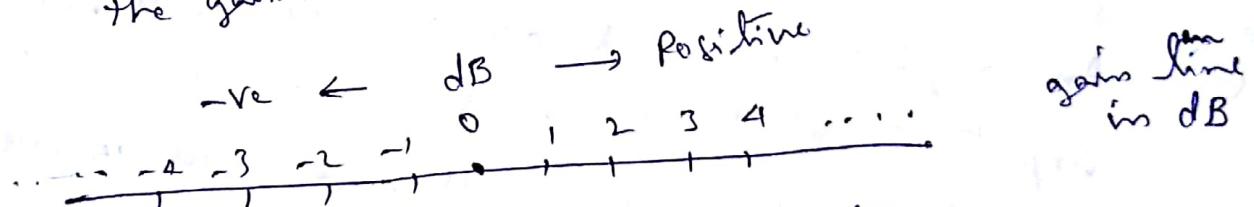

Amplification \rightarrow
i.e. $A > 1 \Rightarrow O/P > I/P$
Attenuation \leftarrow
 $A < 1 \Rightarrow O/P < I/P$

At 3dB frequency the gain is $\frac{1}{\sqrt{2}}$ of maximum gain

$$\therefore 20 \log_{10} \frac{\text{Av}}{3\text{dB}} = -2$$

$$A \Big|_{3\text{dB freq}} = \frac{A_{\text{max}}}{\sqrt{2}}$$

(P.T.O.)

$$\therefore 20 \log_{10} A_{\text{at } 3\text{dB freq}} = 20 \log_{10} \frac{A_{\text{max}}}{\sqrt{2}}$$

$$= 20 \log_{10} A_{\text{max}} - 20 \log_{10} \sqrt{2}$$

$$= (A_{\text{max}} \text{ in dB}) - 10 \log 2$$

$$= (A_{\text{max}} \text{ in dB}) - 3.010 \text{ dB}$$

∴ At 3 dB frequency the gain is 3 dB smaller than that of the maximum gain in dB.

Prob: ① Determine the linear gain if gain is 1 dB.

Sol: $20 \log_{10} A = 1 \text{ dB}$

$$\therefore \log_{10} A = \frac{1}{20} = 0.05$$

$$\therefore A = 10^{0.05}$$

$$\boxed{\therefore A = 1.12}$$

- ② An amplifier has a voltage gain of 15 dB. If the input signal voltage is 0.8V determine the o/p voltage. we know that gain in dB is given as 15 dB

Sol: we know

$$\therefore 20 \log_{10} \frac{V_o}{V_i} = 15$$

$$\therefore \log_{10} \frac{V_o}{V_i} = \frac{15}{20} = \frac{3}{4} = 0.75$$

$$\therefore \frac{V_o}{V_i} = 10^{0.75} = 5.6234$$

$$\therefore V_o = 4.5 \text{ V}$$

End

(P.T.O.)

Note ⑥ Validity of Hybrid- π model.

- ② The Hybrid- π model is valid for ~~small~~ and base incremental current I_B is small compared with collector incremental current I_C .
- ③ The Hybrid- π model is valid for frequencies upto approximately $\frac{f_T}{3}$.

**Question Bank on
ANALOG CIRCUITS AND APPLICATIONS.**

Questions for 2 marks.

- ✓ 1. The absolute gain of an amplifier is 30; find its decibel in gain.
- ✓ 2. The absolute gain of an amplifier is 40; find its decibel in gain.
3. The input power to an amplifier is 10 mw while output power is 1.5 W. Find the gain of the amplifier.
4. The input power to an amplifier is 20 mw while output power is 2.5 W. Find the gain of the amplifier.
5. A multistage amplifier employs 4 stages each of which has a power gain of 20. What is the total gain of the amplifier in db?
6. A multistage amplifier employs 3 stages each of which has a power gain of 30. What is the total gain of the amplifier in db?
7. The gain of the second amplifier in case of two-stage amplifier is low. Comment.
8. What do you understand by multistage transistor amplifier?
9. What is need to of multistage transistor amplifier?
10. Explain the term frequency response with respect to two-stage transformer-coupled amplifier.
11. What are the advantages of frequency with respect to two-stage amplifier?
12. What are the disadvantages of frequency with respect to two-stage transformer-coupled amplifier?
13. Explain the term gain.
14. What is the application of two stage RC coupled amplifier?
15. Draw the block diagram of multistage amplifier.
16. Why do we prefer to express the gain in db?

Questions for 3 marks.

1. We are to match a $16\ \Omega$ speaker load to an amplifier so that the effective load resistance is $10K\Omega$. What should be the transformer turn ratio?
2. We are to match a $24\ \Omega$ speaker load to an amplifier so that the effective load resistance is $12\ K\Omega$. What should be the transformer turn ratio?
3. A single stage amplifier has collector load $R_c=10K\Omega$, input resistance $R_{in}=1K\Omega$ and $\beta=100$. If $R_L=100\Omega$ find the voltage gain.
4. A single stage amplifier has collector load $R_c=20K\Omega$, input resistance $R_{in}=2K\Omega$ and $\beta=100$. If $R_L=75\Omega$ find the voltage gain.
5. A multistage amplifier consists of three stages; the voltage gain of the stages are 60, 100 and 160 calculate the overall gain.
6. With the neat diagram explain the application of two-stage transformer-coupled amplifier
7. Explain the term frequency response.
8. Explain the term decibel gain.
9. Explain the term bandwidth.
10. Why does transformer coupling give poor frequency response?

Questions for 4 marks.

1. A multistage amplifier consists of four stages; the voltage gain of the stages are 60,80, 100 and 160 calculate the overall gain.
2. Explain the terms of amplifier I) frequency response and II) decibel gain.
3. Explain the terms of amplifier I) frequency response and II) bandwidth.
4. Explain the terms of amplifier I) decibel gain and II) bandwidth.
5. Explain the frequency response of two-stage RC coupled amplifier.
6. A multistage amplifier consists of three stages; the voltage gain of the stages are 60,100 and 160 calculate the overall gain.
7. How will you achieve impedance matching with transformer coupling?
8. What are the merits of two-stage transformer coupled amplifier over RC coupled amplifier?
9. Draw the neat-labeled diagram of two-stage RC coupled amplifier and two-stage transformer coupled amplifier.

Questions for 6 marks.

1. With the neat diagram explain the working of two-stage RC coupled amplifier
2. Explain the terms of amplifier I) frequency response II) decibel gain and III) bandwidth.
3. Explain RC coupled transistor amplifier with special reference to frequency response, advantages, disadvantages and application.
4. With neat diagram explain the working of transformer coupled transistor amplifier.